

UNIT-1, Numericals

Ques 1. A Si diode has a saturation current of 5 mA at 25°C. What is saturation current at 100°C.

Soln. We know

$$I_D = I_0 \left[e^{\frac{V}{\eta V_T}} - 1 \right]$$

$$\Rightarrow \frac{V}{T} = \frac{T \text{ in Kelvin}}{11,600} = \frac{25+273}{11,600} \Rightarrow \frac{V}{T} = 25.68 \text{ mV}$$

$$\Rightarrow \text{For Si, } \begin{cases} V = 0.7 \text{ V} \\ \eta = 2 \end{cases}, I_0 = 5 \text{ mA} = 5 \times 10^{-9} \text{ Amp.}$$

$$\therefore I_D = 5 \times 10^{-9} \left[e^{\frac{0.7}{2 \times 25.68 \times 10^{-3}}} - 1 \right]$$

$$\boxed{I_D = 4.15 \text{ mA}}$$

$$\Rightarrow \text{At } 100^\circ \text{C : } I_D = I_0 \left[e^{\frac{V}{\eta V_T}} - 1 \right]$$

$$\frac{V}{T} = \frac{T}{11,600} = \frac{100+273}{11,600}, \boxed{V = 32.15 \text{ mV}}$$

$$\begin{cases} \eta = 2 \\ V = 0.7V \end{cases}$$

$$\Rightarrow \therefore 4.15 \times 10^{-3} = \frac{I}{I_0} \left[e^{\frac{0.7}{2 \times 32.15 \times 10^{-3}}} - 1 \right]$$

$$\Rightarrow I_0 = \frac{4.15 \times 10^{-3}}{53422.17}$$

$$I_0 = 77.68 \text{ mA}$$

Ans

Imp
* Q2) At what Voltage, the Current flowing through Ge diode will reach 80% of its saturation value at room temp.

$$\text{Soln: Given } \eta = 1 \text{ for Ge} \quad \left| \begin{array}{l} \frac{V}{T} = \frac{T}{11,600} = \frac{27+273}{11,600} \\ I_D = 0.8 I_0 \quad \boxed{V_T = 25.8 \text{ mV}} \end{array} \right.$$

We know

$$I_D = I_0 \left[e^{\frac{V}{\eta T}} - 1 \right]$$

$$\Rightarrow 1.8 \frac{I}{I_0} = \frac{V}{I_0} \left[e^{\frac{V}{25.8 \times 10^{-3}}} - 1 \right]$$

$$\Rightarrow 1.8 = e^{\frac{V}{25.8 \times 10^{-3}}} - 1$$

$$\Rightarrow 1.8 = e^{\frac{V}{25.8 \times 10^{-3}}}$$

\Rightarrow Take \log_e on both sides :-

$$\Rightarrow \log_e 1.8 = \log_e e^{\frac{V}{25.8 \times 10^{-3}}}$$

$$\log_e 1.8 = \frac{V}{25.8 \times 10^{-3}}$$

$$\boxed{V = 15.16 \text{ mV}} \quad \underline{\text{Ans}}$$

Q No 3 The diode Current and reverse saturation Current of a Si diode at room temp are 3.4 mA

and 5 nA respectively. Calculate the value of voltage drop across the diode at room temp.

Soln

We know

$$I_D = I_0 \left[e^{\frac{V}{25.8 \times 10^{-3}}} - 1 \right]$$

$$\Rightarrow \frac{V}{T} = \frac{T}{11,600} = \frac{27+273}{11,600} \Rightarrow \boxed{V = 25.8 \text{ mV}}$$

$$3.4 \times 10^{-3} = 5 \times 10^{-9} \left[e^{\frac{V}{2 \times 25.8 \times 10^{-3}}} - 1 \right]$$

⇒ After solving and taking \log_e on both sides -

$$V = 6.94 \text{ mV}$$

QNo4 I_0 at $350K = 5mA$

$$V_0$$
 at $350K = 0.6V$

Find I_D at $350K$ for si diode.

Sol 4

$$I_D = I_0 \left[e^{\frac{V_D}{\eta V_T}} - 1 \right]$$

$$\Rightarrow V_T = \frac{T}{11,600} = \frac{350}{11,600} = \underline{\underline{30.18 \text{ mV}}}$$

$$\therefore I_D = 5 \times 10^{-9} \left[e^{\frac{0.6}{2 \times 30.18 \times 10^{-3}}} - 1 \right]$$

$$= 5 \times 10^{-9} \left[e^{9.94035} - 1 \right]$$

$$\left. \begin{array}{l} (P, N) \rightarrow (N, P) \\ (D, N) \rightarrow (N, D) \end{array} \right\}$$

$$I_D = 0.103 \text{ mA}$$

Ans

- QN05) Find the dynamic resistance of a p-n junction diode at a forward current of 2 mA. Assume

$$\frac{k'T}{e} = 25 \text{ mV.}$$

Soln. Given $I = 2 \text{ mA}$, $\eta = 1$ (For Ge) Assume

$$V_T = \frac{k'T}{e} = 25 \text{ mV}$$

$$\Rightarrow \text{Dynamic Resistance } R = \frac{\eta V_T}{I} = \frac{1 \times 25 \times 10^{-3}}{2 \times 10^{-3}}$$

$$R = 12.5 \Omega \quad \underline{\text{Ans}}$$

Imp -

- * QN06 Calculate the dynamic forward resistance and reverse resistance of a p-n junction diode

When the applied voltage is 0.25V at temp of

$$\# T = 300K. \text{ Given } I_0 = 2 \text{ mA}$$

Q1 :- We know Dynamic forward Resistance

$$\boxed{r = \frac{\eta V}{T} e^{\frac{V}{\eta V_T}}}$$

⇒ Assume $\eta = 1$, For Ge

$$\Rightarrow \frac{V}{T} = \frac{T}{11,600} = \frac{300}{11,600} = 25.86 \text{ mV}$$

$$\Rightarrow V = .25V \quad I_0 = 2 \mu A$$

$$r = \frac{1 \times 25.86 \times 10^{-3}}{2 \times 10^{-6} e^{.25 / 1 \times 25.86 \times 10^{-3}}}$$

$$\boxed{r = 0.8167 \Omega}$$

$$\Rightarrow \text{Reverse Resistance} = \frac{V}{I_0} = \frac{.25}{2 \times 10^{-6}}$$

$$= 125 \text{ k}\Omega$$

Ans

QNO7

A diode Current is 0.6 mA when applied Voltage is 400 mV and 20 mA when applied Voltage is 500 mV . Find η . Assume $V_T = 26 \text{ mV}$.

Soln.

$$I_D = I_0 \left[e^{\frac{V}{\eta V_T}} - 1 \right]$$

$$\Rightarrow I_D = I_0 e^{\frac{V}{\eta V_T}}, \text{ put the values, we get: -}$$

$$0.6 \text{ mA} = I_0 e^{\frac{400}{26 \text{ mV} \eta}} \rightarrow ①$$

$$\Rightarrow \text{Similarly } 20 \text{ mA} = I_0 e^{\frac{500}{26 \eta}} \rightarrow ②$$

\Rightarrow Divide eqn ② by eqn ①, we get

$$\frac{e^{\frac{500}{26 \eta}}}{e^{\frac{400}{26 \eta}}} = \frac{20}{0.6}$$

$$\Rightarrow e^{\frac{100}{26 \eta}} = \frac{20}{0.6} \quad \Rightarrow e^{\frac{100}{26 \eta}} = 33.33$$

$$\Rightarrow \text{Take loge on both sides: - } \frac{100}{26 \eta} = \log_e 33.33$$

$$\eta = \frac{100}{26 \times \log_e 33.33} \Rightarrow \boxed{\eta = 1.097} \quad \underline{\text{Ans}}$$

Ques What is the ratio of Current for forward

bias mode with Voltage $0.05V$ to the Current

with same magnitude of reverse bias.

Ans

We know

$$I = I_0 \left[e^{\frac{V}{\eta V_T} - 1} \right]$$

When Forward Bias

$$I_F = I_0 \left[e^{\frac{0.05}{\eta V_T} - 1} \right]$$

Assume $\eta = 1$, For Ge

$$2 \frac{V}{T} = \frac{T}{11,600} = \frac{27+273}{11,600} \text{ at room temp.}$$

$$\frac{V}{T} = 25.8 \text{ mV} \approx \underline{\underline{26 \text{ mV}}}$$

$$\therefore I_F = I_0 \left[e^{\frac{0.05}{26 \times 10^{-3}} - 1} \right] \rightarrow ①$$

Similarly

When Reverse bias :

$$V = -0.05V$$



$$I_R = I_0 \left[e^{\frac{-0.05}{26 \times 10^{-3}} - 1} \right] \rightarrow$$

Divide (i) by (ii), we get -

$$\Rightarrow \frac{\frac{I_F}{I_R}}{\frac{I_F}{R}} = \frac{e^{0.05/26 \times 10^{-3}} - 1}{e^{-0.05/26 \times 10^{-3}} - 1} = \frac{5.842}{-0.8538}$$

$$\Rightarrow \left[\frac{I_F}{I_R} = -6.84 \right] \text{ Ans}$$

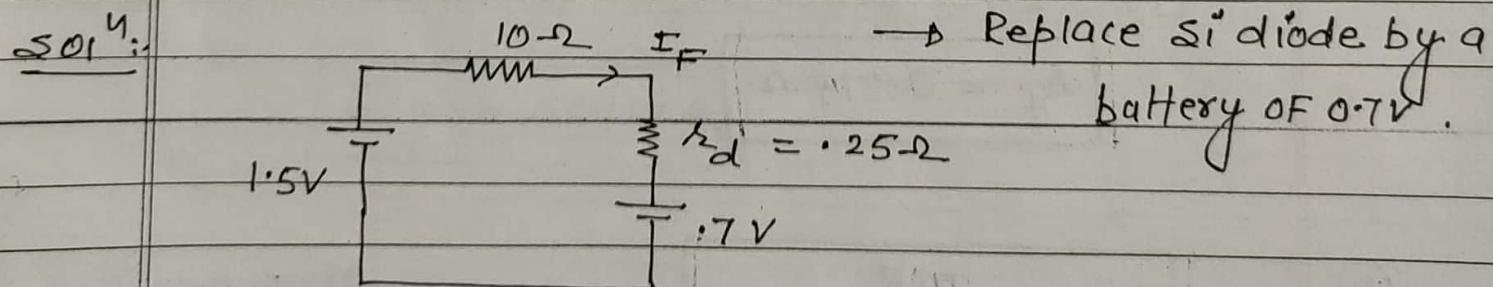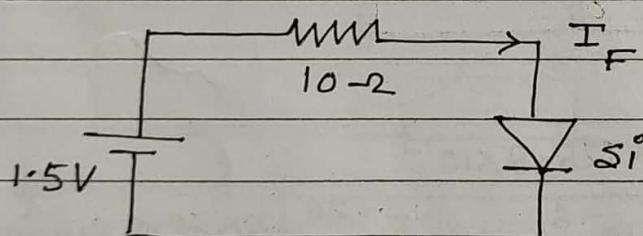QNo9 Calculate forward Current I_F for si diode with dynamic resistance $r_d = 0.25\Omega$



$$\Rightarrow \text{Apply KVL} \quad 1.5 - 10I_F - 0.25I_F - 0.7 = 0$$

$$\therefore I_F = \frac{1.5 - 0.7}{10 + 0.25} \Rightarrow I_F = 87.8 \text{ mA}$$

Ans

Q10 For a Ge diode, the reverse saturation current is $2 \mu A$ at reverse voltage of $0.26 V$.

Calculate the forward and reverse dynamic resistance, if the forward biased voltage is $0.26 V$ at room temp.

Q11 Given

$$I_0 = 2 \mu A$$

$$\eta = \pm \text{ for Ge}$$

$$V_{\text{reverse}} = -0.26 V$$

$$V_{\text{forward}} = 0.26 V$$

At Room Temp

$$\frac{V}{T} = \frac{T}{11,600} = \frac{27+273}{11,600}$$

$$\boxed{\frac{V}{T} = 25.8 \text{ mV}}$$

We know

$$\boxed{r_d = \frac{nV_T}{I_0 e^{-V/nV_T}}}$$

$$\Rightarrow ① r_f = \frac{2 \times 25.8 \times 10^{-3}}{\frac{2 \times 10^{-6}}{e^{+0.26}} \mid 2 \times 25.8 \times 10^{-3}}$$

$$\boxed{r_f = 0.519 \Omega}$$

②


$$\boxed{r_s = \frac{nV_T}{I_0 e^{-V/nV_T}}}$$

$$\Rightarrow r_s = \frac{2 \times 25.8 \times 10^{-3}}{\frac{2 \times 10^{-6}}{e^{-0.26}} \mid 2 \times 25.8 \times 10^{-3}}$$

$$\boxed{r_s = 310.34 \text{ M}\Omega}$$

⇒ Numericals based on Series And parallel of diodes.


QNo 1)

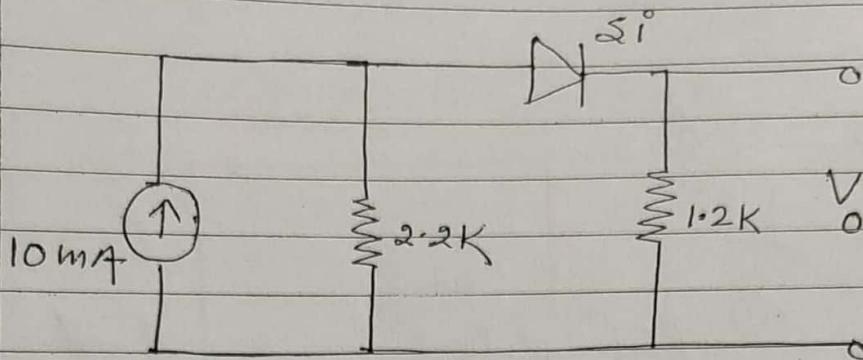

Find V_0 .

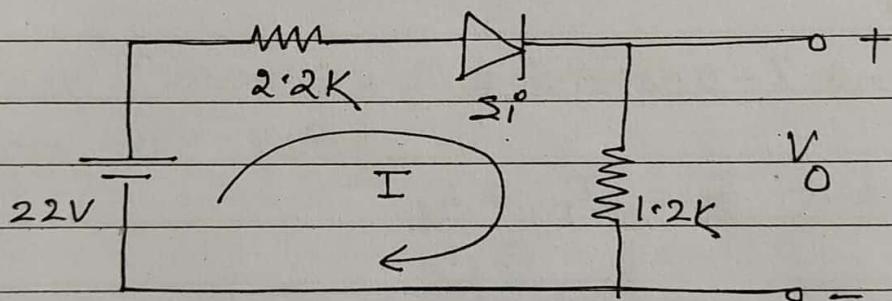Q1)

Converting Current Source into Voltage Source.



⇒ Apply KVL

$$22 - 2.2I - 0.7 - 1.2I = 0$$


$$I = 6.264 \text{ mA}$$

$$\therefore V_0 = 6.264 \text{ mA} \times 1.2K$$

$$V_0 = 7.52V$$

Ans

• QN02 Find I_1 , I_2 and I_{D2} .

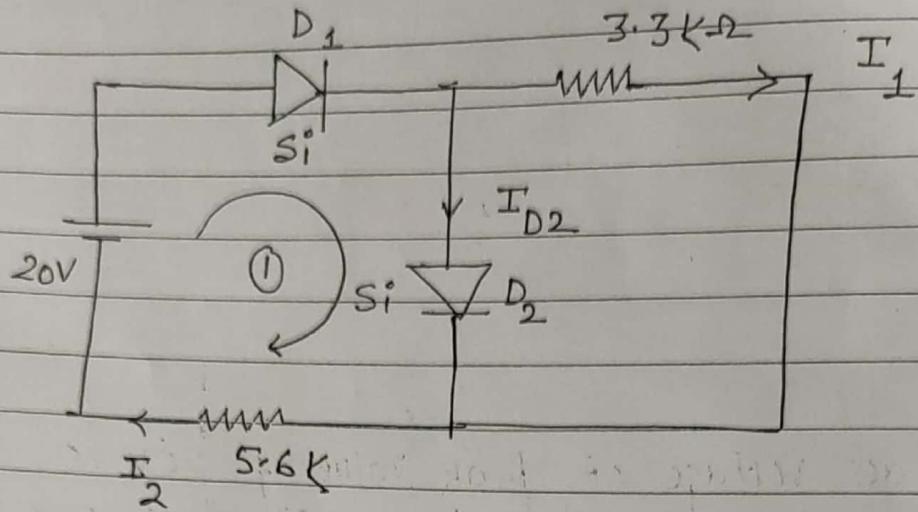

⇒ Apply KVL in Loop 1

$$20 - 0.7 - 0.7 - 5.6 I_2 = 0$$

$$\text{but } I_2 = I_{D2} + I_1$$

$$20 - 0.7 - 0.7 - 5.6 (I_{D2} + I_1) = 0$$

$$\therefore I_{D2} + I_1 = 3.32 \rightarrow ①$$

⇒ Apply KVL in Loop 2

$$-3.3 I_1 + 0.7 = 0$$

$$I_1 = 0.212 \text{ mA}, \text{ put in eqn } ①$$

$$I_{D2} = 3.108 \text{ mA}$$

$$I_2 = I_{D2} + I_1$$

$$= 3.11 + .212$$

$$I_2 = 3.32 \text{ mA}$$


Ans

QNo3

An ac voltage of peak value of 20V is connected in series with a Si diode and load resistance of $1\text{ k}\Omega$. If the forward resistance of diode is 15Ω . Find -

- ① Peak Current through diode
- ② Peak O/P voltage.

so1^h

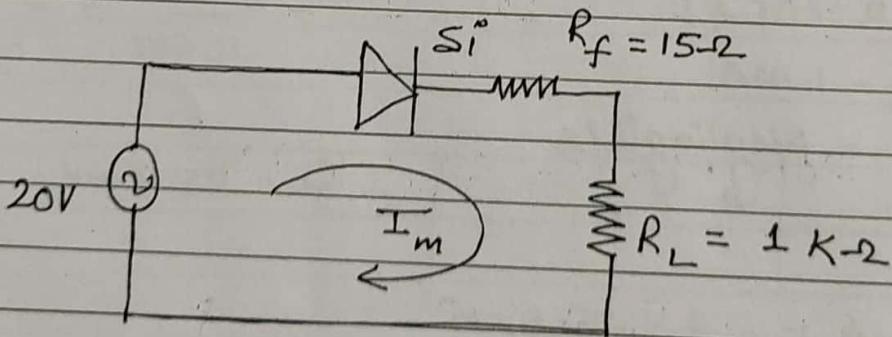

⇒ Apply KVL

$$20 - 0.7 - \frac{I_m \times 15\Omega}{m} - \frac{I_m \times 1\text{ k}\Omega}{m} = 0$$

$$I_m = \frac{20 - 0.7}{15\Omega + 1000\Omega} = \frac{19.3}{1015\Omega}$$

①

$$I_m = 19 \text{ mA}$$

②

$$\begin{aligned} \text{Peak O/P Voltage} - V_{O(\max)} &= I_m \times R_L \\ &= 19 \text{ mA} \times 1 \text{ k}\Omega \\ &= 19 \text{ V } \underline{\underline{\text{Ans}}} \end{aligned}$$

QNo4

What is the magnitude of λ for Si p-n junction diode at room temp and for dc current of 1 mA

Sol4

We know

$$\lambda = \frac{\eta V_T}{I_D + I_0}$$

$$\eta = 2 \text{ For Si}$$

$$I_D = 1 \text{ mA}$$

$$I_0 = \text{Negligible}$$

Room temp
↑

$$V_T = \frac{T}{11,600} = \frac{27+273}{11,600} = \frac{300}{11,600} \text{ mV}$$

$$V_T = 25.8 \text{ mV}$$

∴

$$\lambda = \frac{2 \times 25.8 \times 10^{-3}}{1 \times 10^{-3}}$$

$$\lambda = 51.6 \Omega \quad \underline{\underline{\text{Ans}}}$$

Imp

* QN05

[Page No. _____
Date / /]

A diode operating at 300K at a forward voltage of 0.4V carries a current of 10 mA.

When the voltage is changed to 0.42 V, the current becomes twice.

Calculate the value of I_0 and η for diode.

Q014

Given $T = 300K$

$$V_1 = 0.4V$$

$$\frac{V}{T} = \frac{T}{11,600} = \frac{300}{11,600}$$

$$I_1 = 10 \text{ mA}$$

$$V_2 = 0.42V$$

$$\boxed{\frac{V}{T} = 25.8 \text{ mV}}$$

$$I_2 = 20 \text{ mA}$$

We know

$$I_1 = I_0 \left[e^{\frac{V_1}{\eta V_T}} - 1 \right]$$

$$10 = I_0 \left[e^{\frac{0.4}{\eta V_T}} - 1 \right] \rightarrow ①$$

Similarly

$$I_2 = I_0 \left[e^{\frac{V_2}{\eta V_T}} - 1 \right]$$

$$20 = I_0 \left[e^{\frac{0.42}{\eta V_T}} - 1 \right] \rightarrow ②$$

Divide eqn (1) by (2) :-

$$\frac{10}{20} = \frac{e^{\frac{0.4}{\eta V_T}} - 1}{e^{\frac{0.42}{\eta V_T}} - 1}$$

$$\Rightarrow \frac{1}{2} = \frac{e^{\frac{0.4}{\eta V_T}} - 1}{e^{\frac{0.42}{\eta V_T}} - 1}$$

\Rightarrow As diode is forward biased $\therefore e^x \gg 1$, Neglect

$$\Rightarrow \frac{1}{2} = \frac{e^{\frac{0.4}{\eta V_T}}}{e^{\frac{0.42}{\eta V_T}}} \Rightarrow \text{Taking Loge on both sides}$$

$$\Rightarrow \log_e 0.5 = \log_e e^{\frac{0.4}{\eta V_T}} - \log_e e^{\frac{0.42}{\eta V_T}}$$

$$\Rightarrow -0.693 = \frac{0.4}{\eta V_T} - \frac{0.42}{\eta V_T}$$



$$\Rightarrow \eta V_T = \frac{-0.02}{-0.693} \Rightarrow \eta V_T = 0.0289$$

$$\therefore \eta = \frac{0.0289}{25.8 \times 10^{-3}} \Rightarrow \boxed{\eta = 1.11}$$

$$\therefore I_o = \frac{I_i}{e^{\frac{V_i - V_T}{25.8}} - 1}$$

$$= \frac{10 \times 10^{-3}}{e^{\frac{0.4}{1.11 \times 25.8 \times 10^{-3}} - 1}}$$

$$I_o = 9.066 \text{ mA} \quad \underline{\text{Ans}}$$

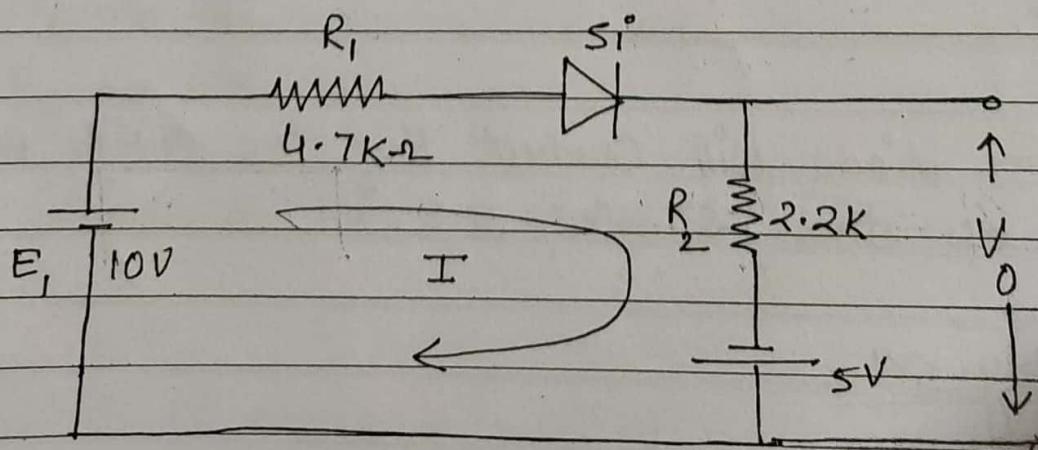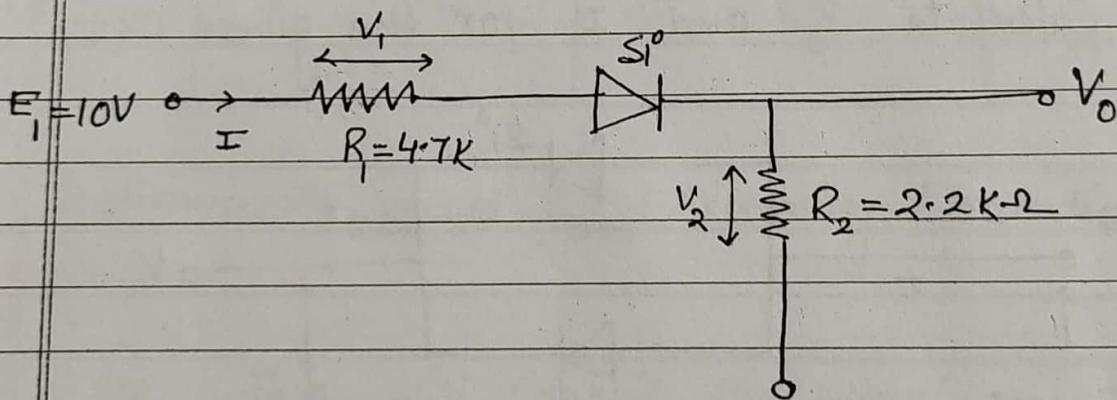QuesDetermine I , V_1 , V_2 and V_o .

$$\Rightarrow \text{Apply KVL : } 10 - I \times 4.7 - 0.7 - I \times 2.2 + 5 = 0$$

$$I = 2.07 \text{ mA}$$


$$\textcircled{1} \quad \therefore V_1 = IR_1 = 2.07 \times 4.7 \text{ k} = 9.73 \text{ V}$$

$$\textcircled{2} \quad V_2 = IR_2 = 2.07 \text{ mA} \times 2.2 \text{ k} \Omega = 4.55 \text{ V}$$

$$\textcircled{3} \quad V_0 = IR_2 - 5 \\ = 4.55 - 5$$

$$V_0 = -0.446 \text{ V} \quad \underline{\text{Ans}}$$

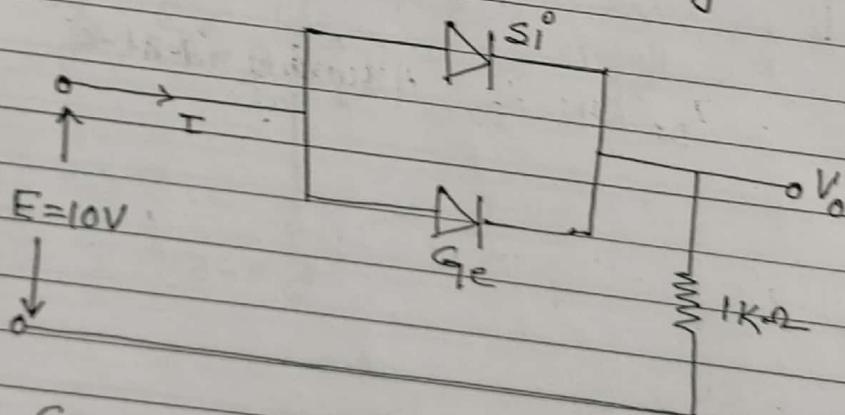QNO7 Calculate V_0 and I for the given ckt.



Soln Ge diode will conduct b'coz its cut-in Voltage is less than Si diode.

\Rightarrow Apply KVL


$$\Rightarrow 10 - 0.3 - I \times 1\text{K}\Omega = 0$$

$$I = 9.7 \text{ mA}$$

$$\therefore V_o = I \times 1\text{K}\Omega$$

$$= 9.7 \text{ mA} \times 1\text{K}\Omega$$

$$V_o = 9.7 \text{ V} \quad \underline{\text{Ans}}$$

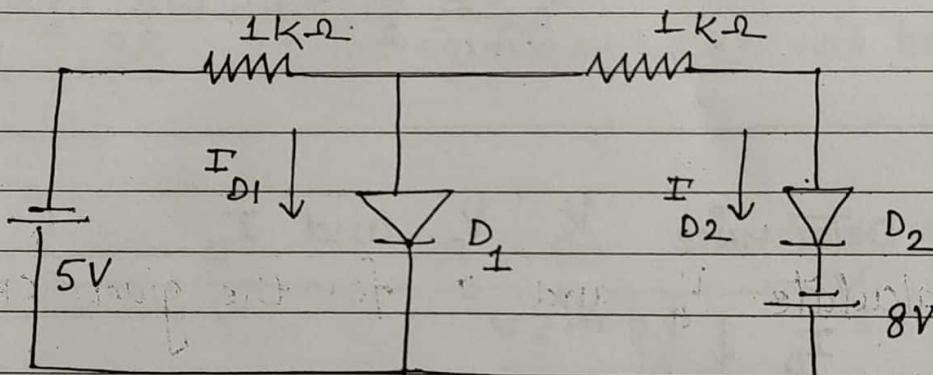Qn 8


Determine I_{D1} and I_{D2} , Assuming ideal diode.

Soln 8V battery will control the working.

$D_1 \rightarrow RB$

$D_2 \rightarrow FB$

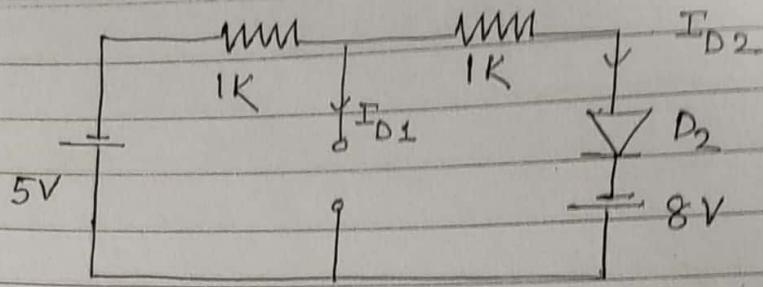\therefore Diode D_1 will be open circuited.




$$\textcircled{1} \quad I_{D1} = 0$$

$$\textcircled{2} \quad \text{Apply KVL} \quad -5 - I_{D2} - I_{D2} + 8 = 0$$

$$I_{D2} = \frac{3}{2} = 1.5 \text{ mA} \quad \underline{\text{Ans}}$$

Ques Determine V_D , V_R and I_D .

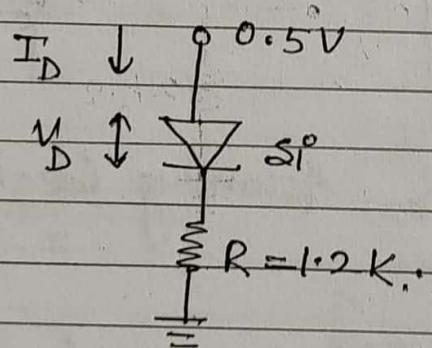

Soln Since the input voltage is insufficient to turn the silicon diode 'ON', therefore equivalent ckt will be -


$$I_D \downarrow \quad 0.5V \quad \textcircled{1} \quad \therefore I_D = 0$$

$$V_D \quad \textcircled{2} \quad V_D = 0.5V$$

$$R = 1.2k \quad \textcircled{3} \quad V_R = I_D \times R$$

$$V_R = 0 \quad \underline{\text{Ans}}$$

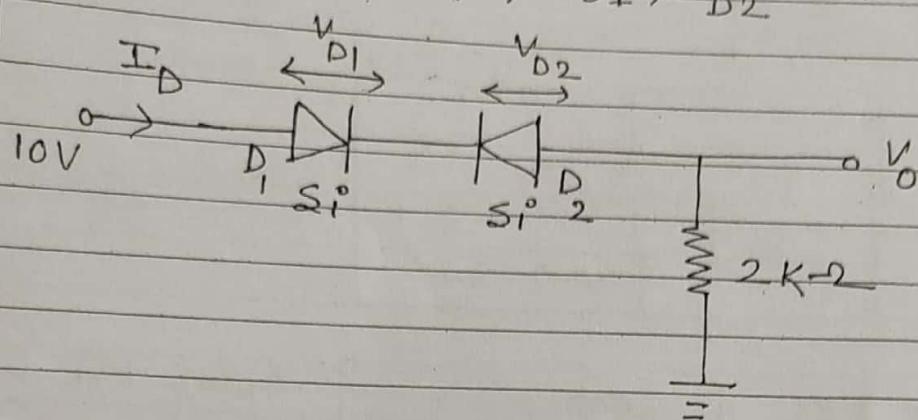
QNO 10 Calculate the V_o , V_{D1} , V_{D2} and I_D .



Soln

D₁ — FB

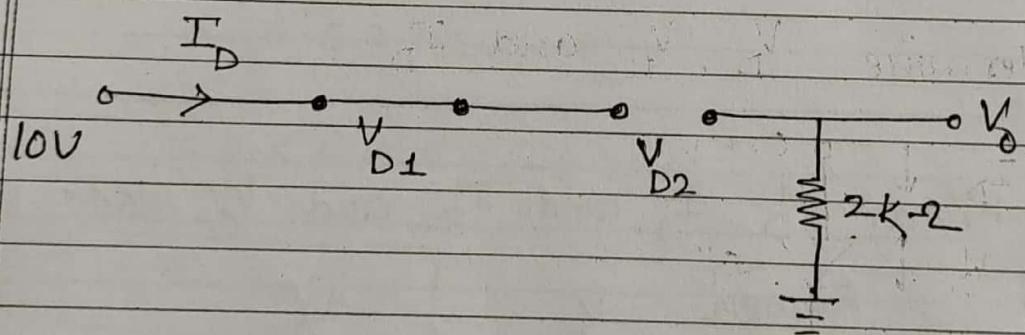D₂ — RB \therefore The equivalent ckt will be —



\therefore

$$\boxed{I_D = 0}$$

$$\boxed{V_{D1} = 10V}$$


$$\boxed{V_{D2} = 10V}$$

$$\& \quad V_o = I_D \times 2k\Omega$$

$$\boxed{V_o = 0V}$$

Ans
=

QNO11 Determine I for the given ckt.

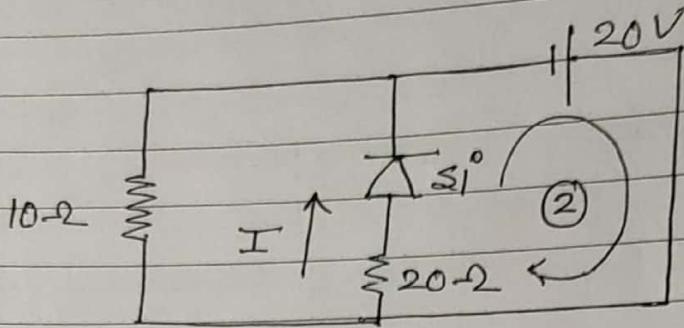

⇒ Apply KVL in Loop 2

$$20 - 20I - 0.7 = 0 \quad \boxed{\text{OR}}$$


$$\boxed{I = 0.965A} \quad \underline{\text{Ans}}$$

Apply KVL in Loop 1

$$-20I - 0.7 - 10I = 0$$

$$I =$$

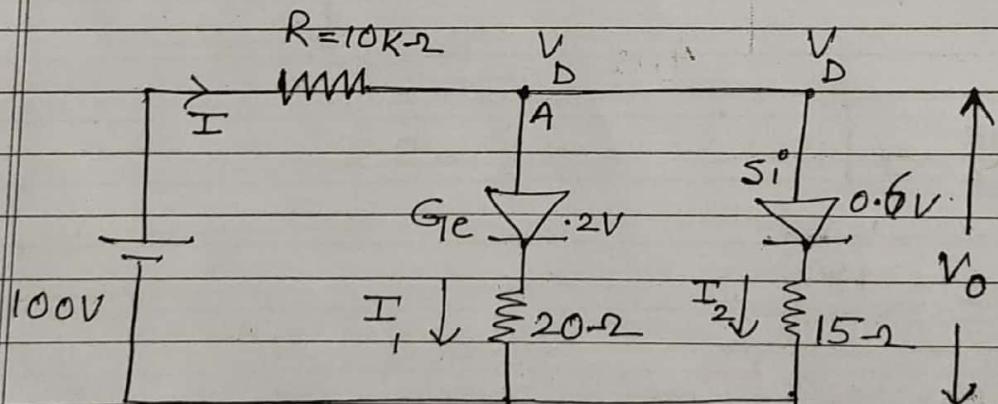QNO12 Find V_D , I , and I_2 , and V_o also.



⇒ Apply KCL at point A.

$$\Rightarrow I = I_1 + I_2$$

$$\Rightarrow \frac{100 - V_D}{10 \times 10^3} = \frac{V_D - 0.9}{20} + \frac{V_D - 0.6}{15 - 2}$$

By solving

$$V_D = 0.5138V$$

$$\Rightarrow I_1 = \frac{V_D - 0.9}{20} = 15.69 \text{ mA}$$

$$I_2 = \frac{V_D - 0.6}{15} = -5.7466 \text{ mA}$$

Ans


$$V_o = 0.6 + 15 - 2 \times I_2$$

$$= 0.6 + 15 - 2 \times (-5.7466 \text{ mA})$$

$$V_o = 0.51 \text{ V}$$

Ans

QNO13 Find V_o , I , I_{D1} and I_{D2} .

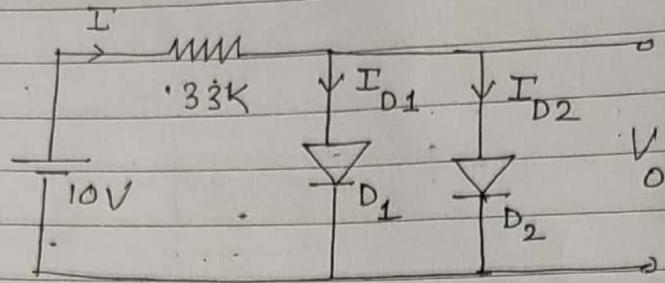


Soln.: D_1 & D_2 will be F.Biased.

$$I = \frac{10V}{33K} = 30.3 \text{ mA}$$

$$\therefore I_{D1} = I_{D2} = I/2 = 15.15 \text{ mA} \quad \underline{\text{Ans}}$$

$$\Rightarrow V_o = 10 - I \times 33K = 0.001V$$

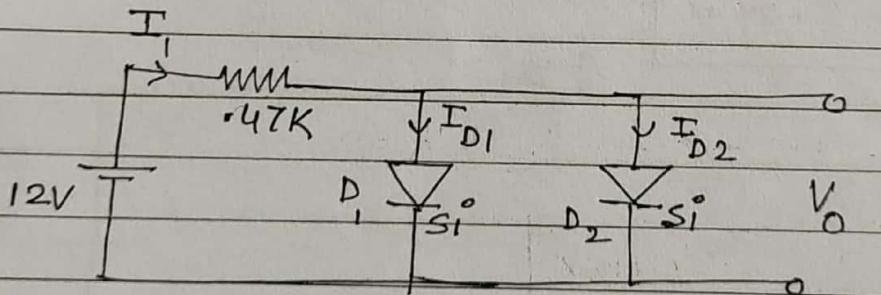QNO14 Find I_i , I_{D1} , I_{D2} and V_o .



Soln: D_1 and D_2 will be Forward biased.

$$\text{Apply KVL} \quad 12 - 47 I_i - 0.7 = 0$$

$$I_i = 24 \text{ mA}$$


$$I_{D1} = I_{D2} = I_i/2 = 12 \text{ mA}, \quad V_o = 0.7V$$

Imp

Page No.

Date: / /

Q NO 15

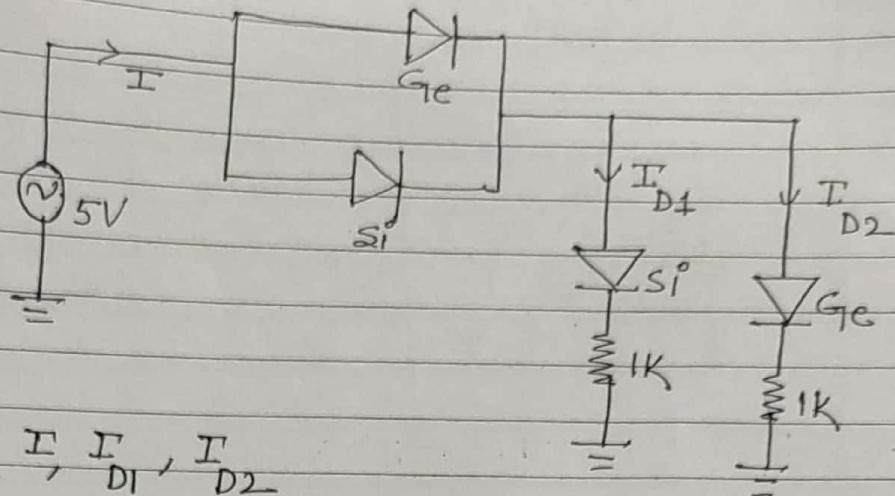

$$\text{Find } I, I_{D1}, I_{D2}$$

Sol: Ge diode will be FB.

\Rightarrow Apply KVL

$$5 - 0.3 - 0.7 - \frac{I}{1k} = 0$$

$$\boxed{I_{D1} = 4 \text{ mA}}$$

Similarly

$$5 - 0.3 - 0.3 - \frac{I_{D2}}{1k} = 0$$

$$\boxed{I_{D2} = 4.4 \text{ mA}}$$


$$\therefore I = I_{D1} + I_{D2}$$

$$= 4 + 4.4$$

$$\boxed{I = 8.4 \text{ mA}} \quad \text{Ans}$$

MINT

QNO16 Find V_{O1} , V_{O2} , I_1 and I .

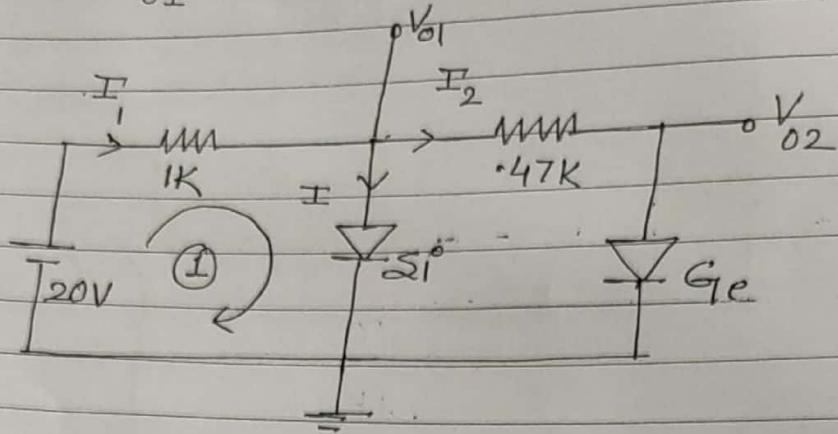

\underline{SOLY}

$$V_{O1} = 0.7V$$

$$\therefore V_{O2} = 0.3V$$

\Rightarrow Apply KVL in Loop 1 :-

$$20 - I_1 - 0.7 = 0$$

$$\boxed{I_1 = 19.3 \text{ mA}}$$

\Rightarrow Now apply KVL in Loop 2 :-

$$-0.47 I_2 - 0.3 + 0.7 = 0$$




$$\boxed{I_2 = .85 \text{ mA}}$$

$$I = I_1 - I_2$$

$$= 19.3 - .85$$

$$\Rightarrow \boxed{I = 18.45 \text{ mA}}$$

Ans

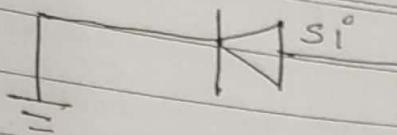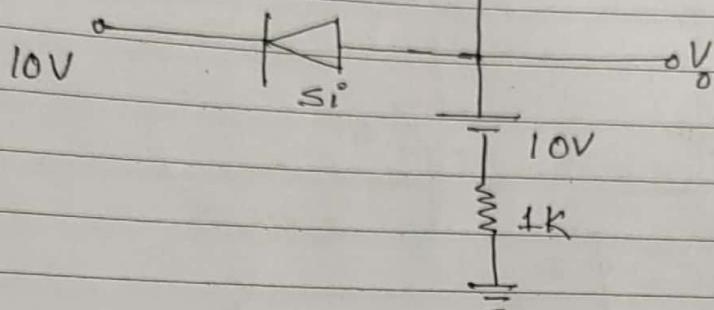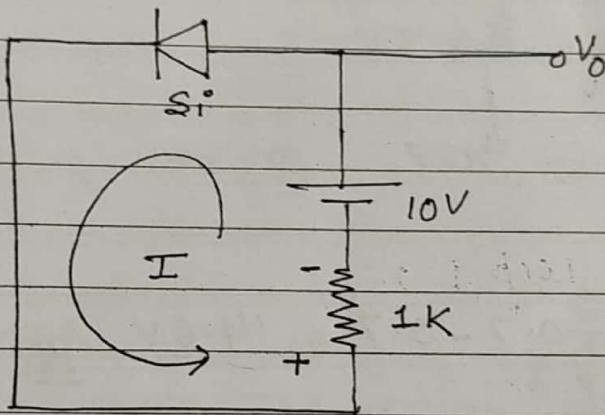QNo17Find V_o QNo14

$$\Rightarrow \underline{\text{KVL}} : 10 - 0.7 - I \times 1k = 0$$


$$I = 9.3 \text{ mA}$$

$$\therefore V_o = 10 - 9.3 \text{ mA} \times 1k\Omega$$

$$V_o = 0.7 \text{ V}$$

Ans

QNo 18

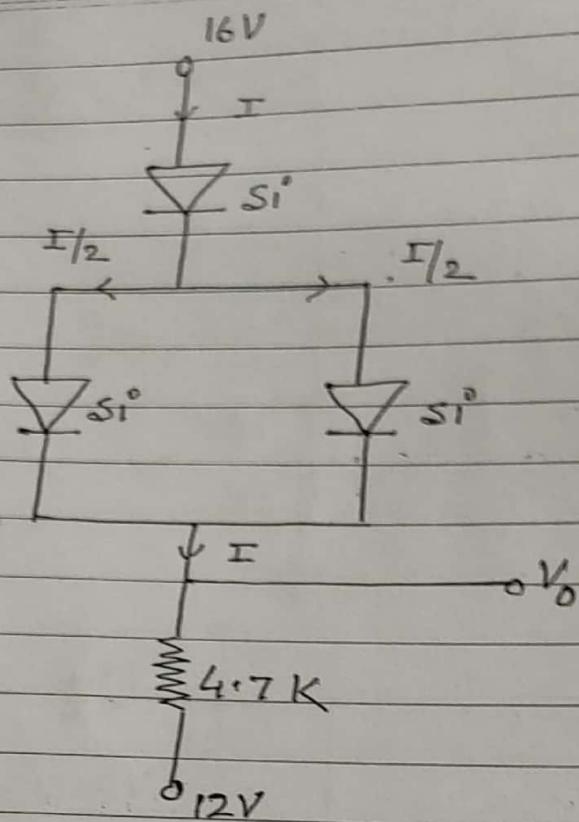Find V_o

Soln.

$$V_o = 16 - 0.7 - 0.7 = 14.6 \text{ V} \quad \underline{\text{Ans}}$$

OR

⇒ Apply KVL

$$16 - 0.7 - 0.7 - IX4.7 - 12 = 0$$


$$I = 0.55 \text{ mA}$$

$$\begin{aligned} \therefore V_o &= 4.7K \times 0.55 \text{ mA} + 12 \\ &= 2.585 + 12 \end{aligned}$$


$$V_o = 14.6 \text{ V}$$

Ans

QN019

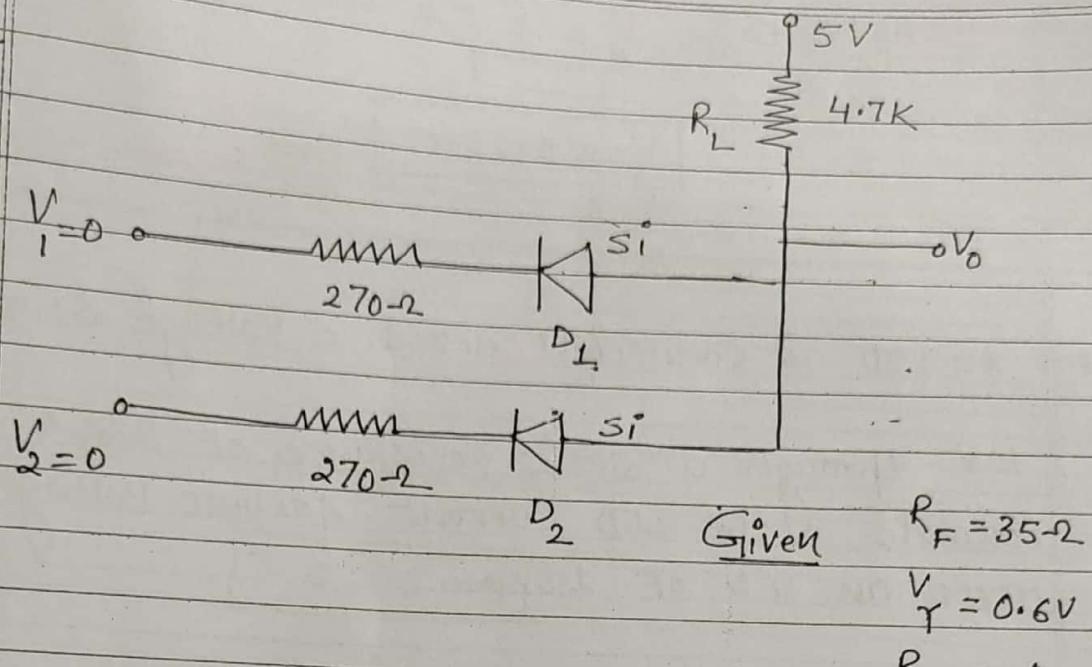

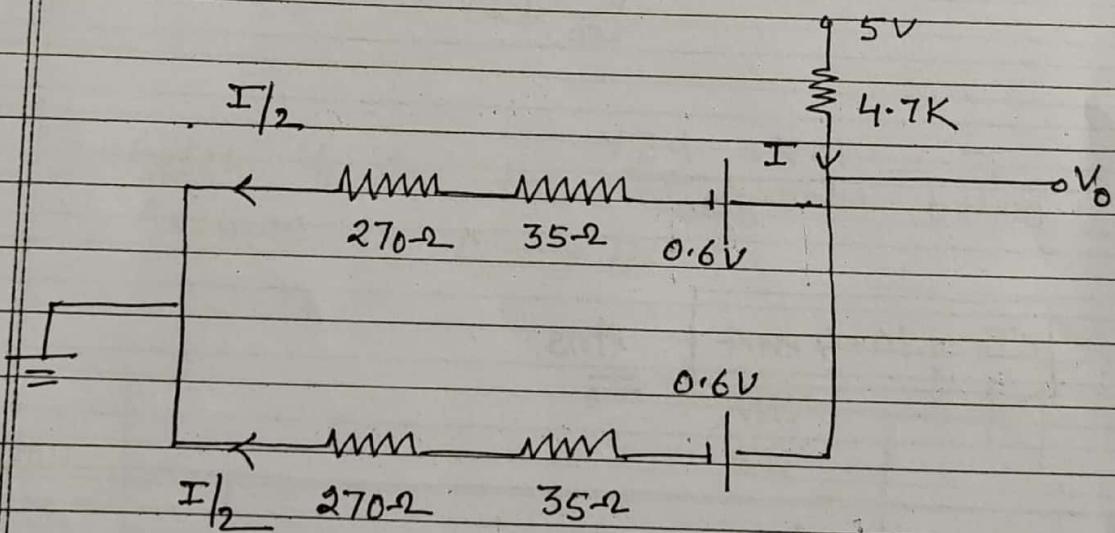Diodes D_1 and $D_2 \rightarrow$ F.B; Equivalent ckt will be -



⇒ Apply KVL in any L path:-


$$5 - 4.7I - 0.6 - 35 \times I_{1/2} - 270 \times I_{1/2} = 0$$

$$\boxed{I = 9 \times 10^{-4} A}$$

$$\therefore \text{O/p voltage } V_o = 5 - 4.7 \times 9 \times 10^{-4} \times 10^3$$

$$V_o = 0.738V \quad \underline{\text{Ans}}$$

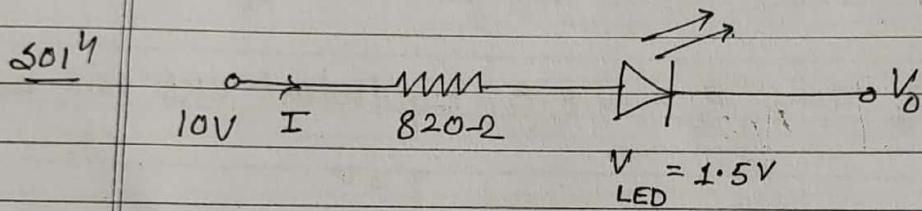
QNo20 An LED is connected across a voltage source of 10V through a series resistance of 820Ω. Calculate the LED current. Assume voltage drop across an LED of 1.5V.



$$I = \frac{10V - 1.5V}{820}$$

$$I = 10.4 \text{ mA} \quad \underline{\text{Ans}}$$


QNo21

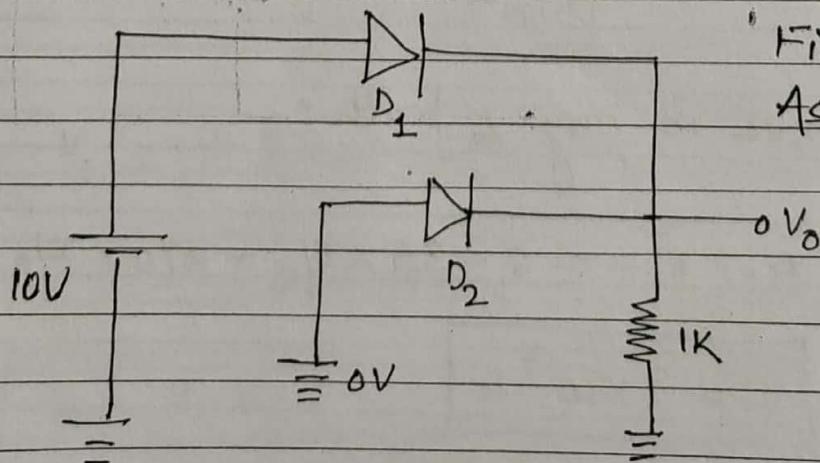

Find I.

Assume diode to be practical.

Q01

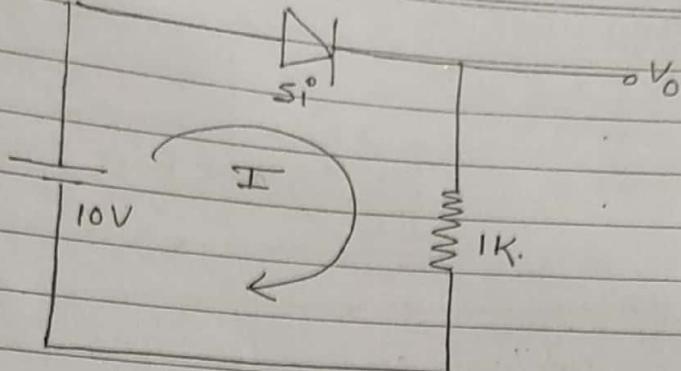

$$\Rightarrow \text{KVL} \quad 10 - 0.7 - I = 0$$

$$I = 9.3 \text{ mA}$$

$$\therefore V_o = 9.3 \text{ mA} \times 1\text{k}$$


$$V_o = 9.3 \text{ V}$$

Ans

QNO 22

Sketch V_o for the ckt shown below.

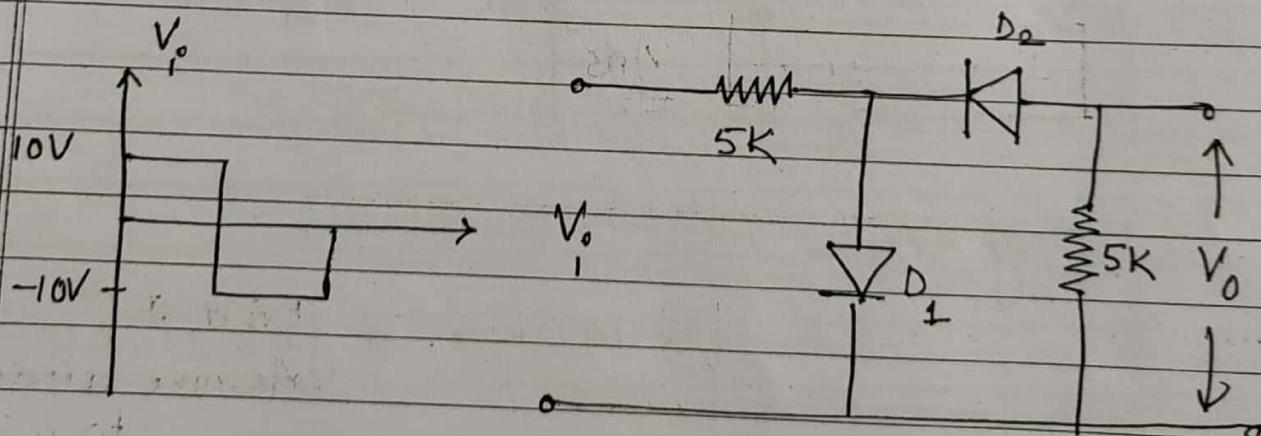
Assume $D_1, D_2 \rightarrow \text{Ideal}$.




Ques 1 During (+ve) Half cycle

$D_1 \rightarrow FB$

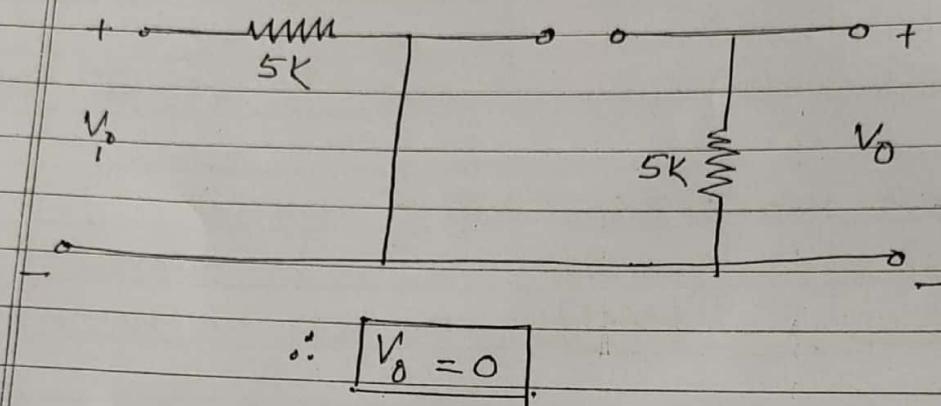$D_2 \rightarrow RB$ \therefore No current will flow through R_1



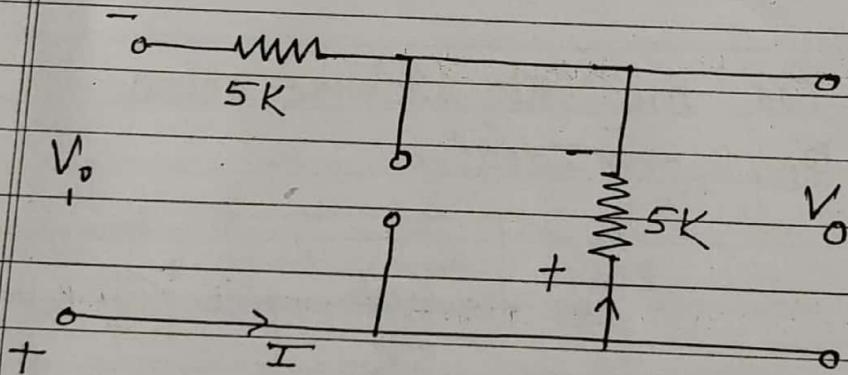\Rightarrow During (-ve) Half cycle :- $D_1 - RB$
 $D_2 \rightarrow FB$




\Rightarrow Apply KVL :- $V_i - 5I - 5I = 0$

$$10 - 10I = 0 \Rightarrow I = 1mA$$

$$\therefore V_o = -5 \times 1mA$$

$$[V_o = -5V]$$

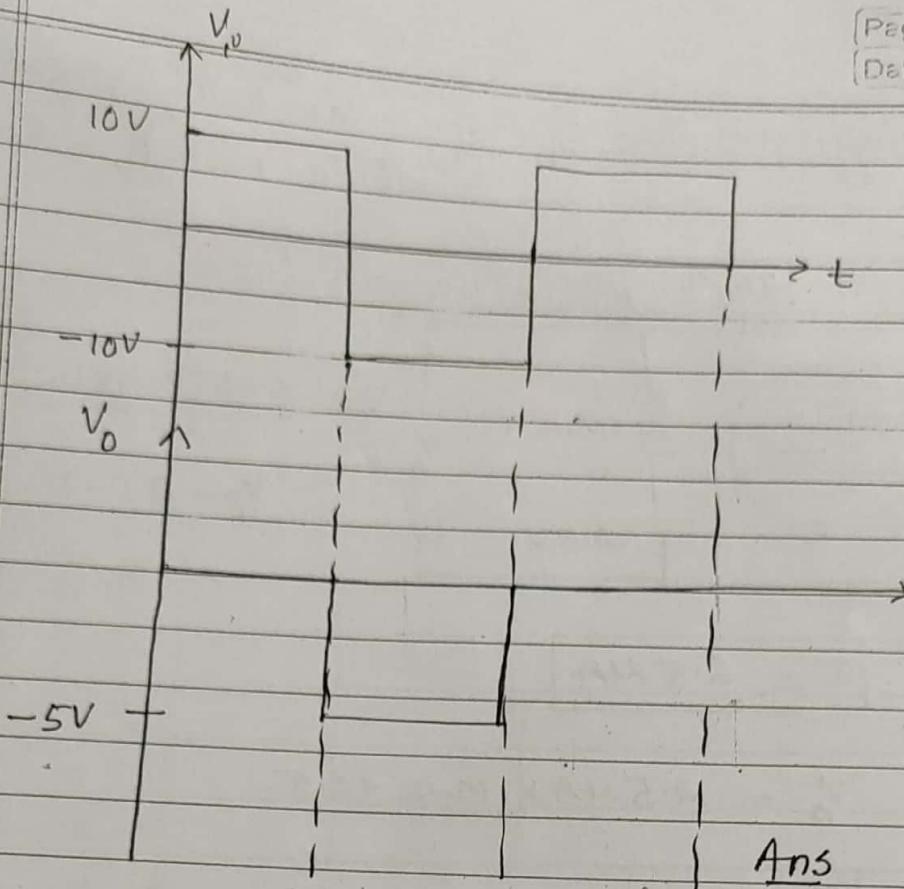


Ans

QNo23 Sketch V_o For the given ckt.


Given $\frac{V_o}{V_i} = 0$

R_S (Resistance of diode when it is R.B) = $2 \text{ M}\Omega$

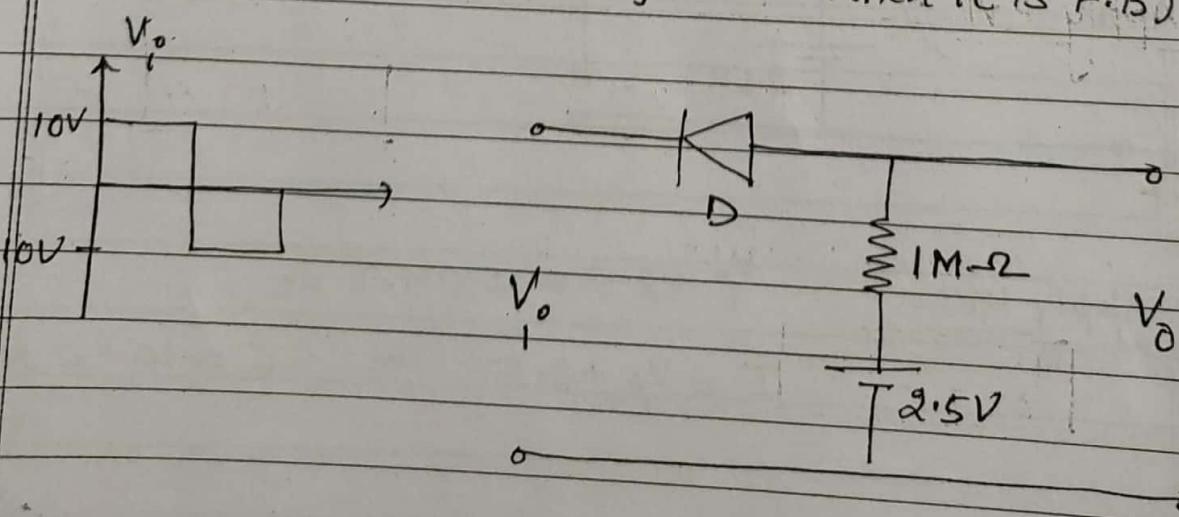R_F (Resistance of diode when it is F.B) = 0



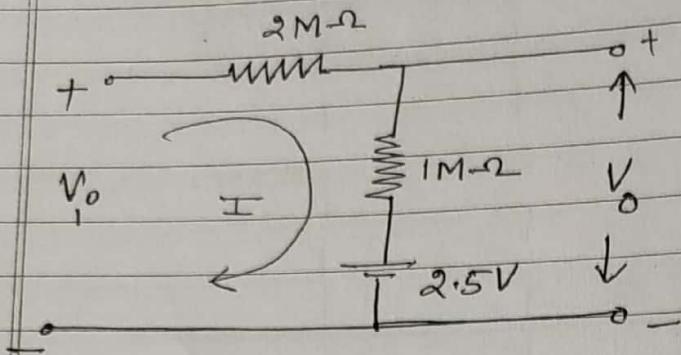Q1 During (+ve) Half cycle :- D - R.B., \therefore Replace diode with $R_d = 2M\Omega$



Apply KVL


$$V_i - 2I - I - 2.5 = 0$$

$$\Rightarrow I = 2.5 \text{ mA}$$

$$\Rightarrow \therefore V_o = 2.5 \text{ mA} \times 1M\Omega + 2.5$$

$$\boxed{V_o = 5V}$$

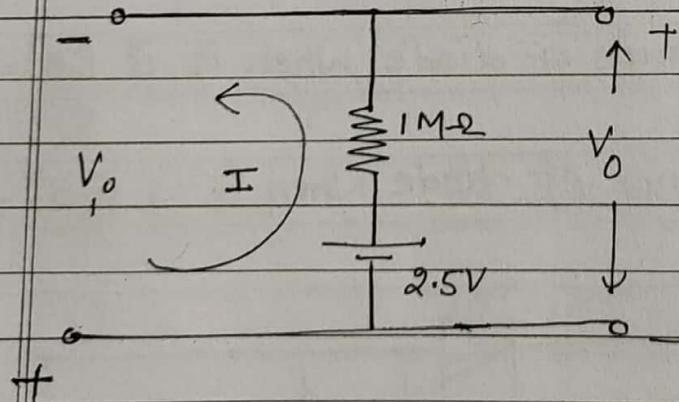During (-ve) Half cycle :- D - FB
Replace diode with $R_F = 0$



Apply KVL


$$V_i + 2.5 - I \times 1M\Omega = 0$$

$$I = V_i + 2.5 \Rightarrow I = 10 + 2.5$$

$$I = 12.5 \text{ mA}$$


$$\therefore V_o = -(1M - 2 \times 12.5 \text{ mA}) + 2.5V$$

$$V_o = -10V$$

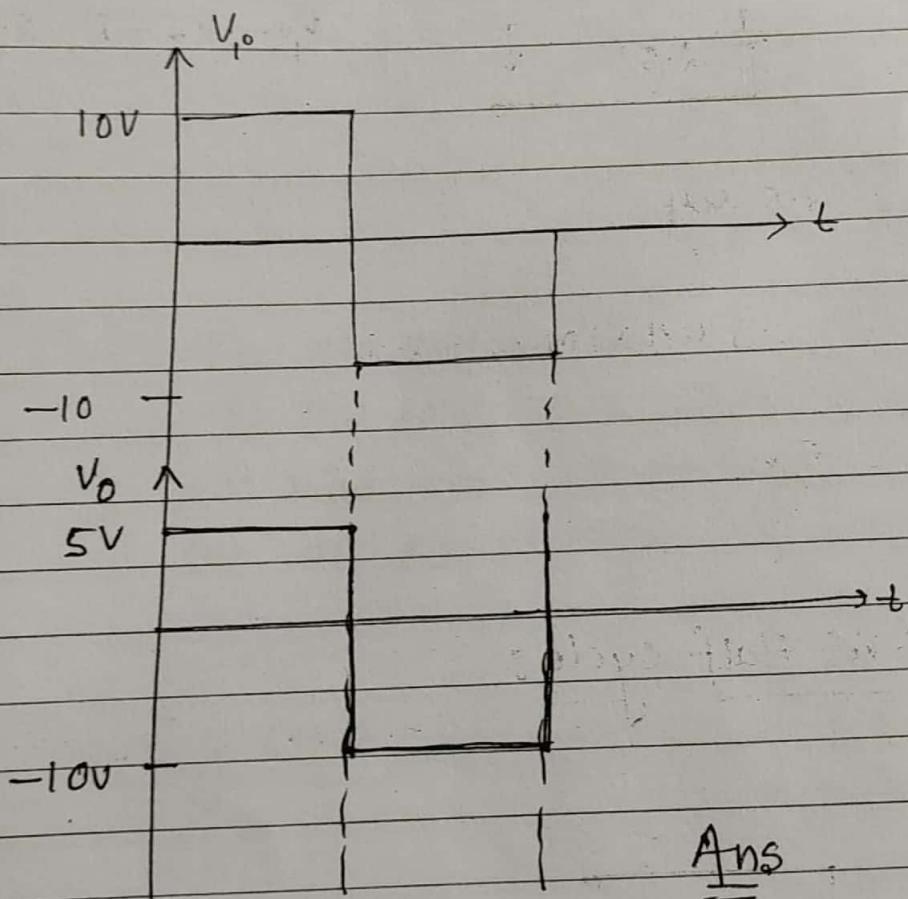

Numericals Based on Rectifiers

QNO1:

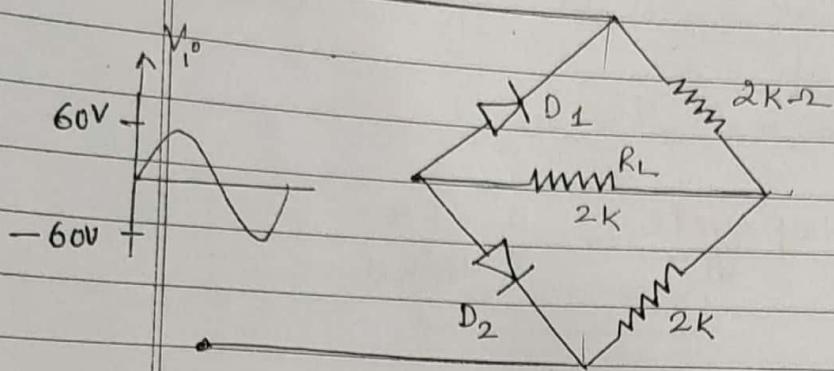


- Find -
- (1) O/P Voltage V_0
 - (2) PIV of each diode
 - (3) Find rms o/p voltage
 - (4) DC o/p voltage

Q01:


During (+ve) Half cycle :- $D_1 \rightarrow RB$

$D_2 \rightarrow FB$

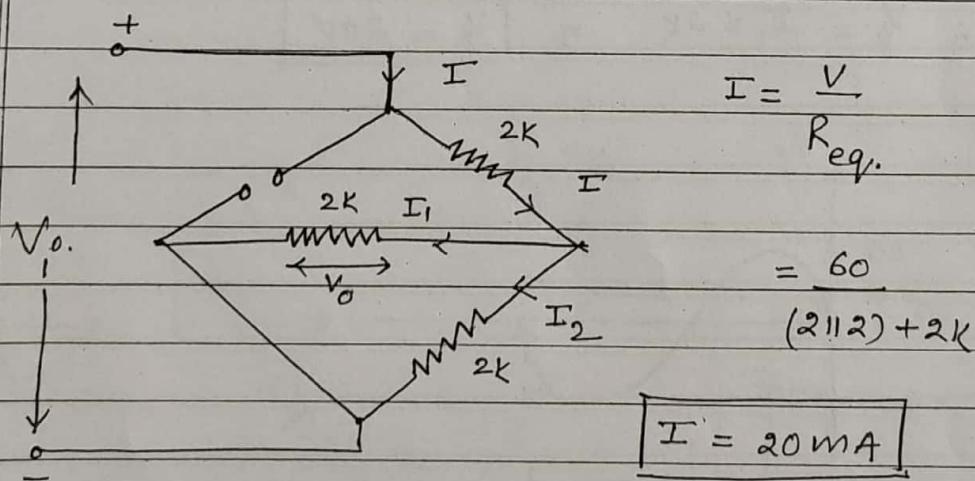


Find - V_o

Q1 The given ckt can be re-drawn as :-

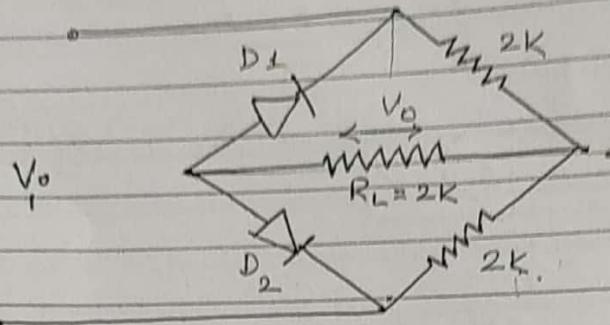

⇒ This is same as QNO-1

QNO3

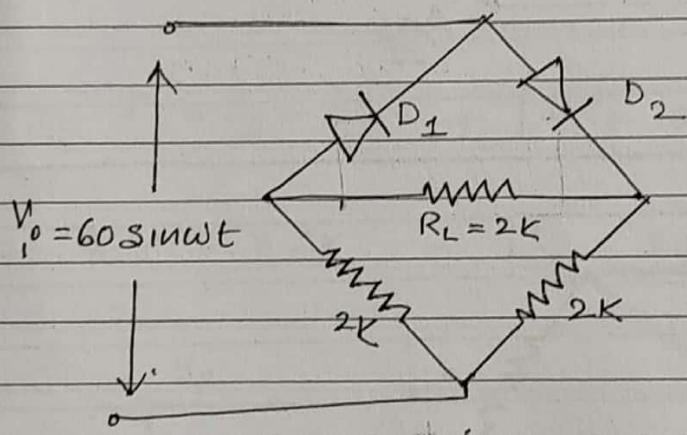

Find :- (1) sketch V_o

(2) PIV of each diode

(3) V_{dc}


(4) V_{rms}

Step 1 During (+ve) Half cycle :-

$D_1 \rightarrow RB$

$D_2 \rightarrow FB$

$$I = \frac{V}{R_{eq}}$$

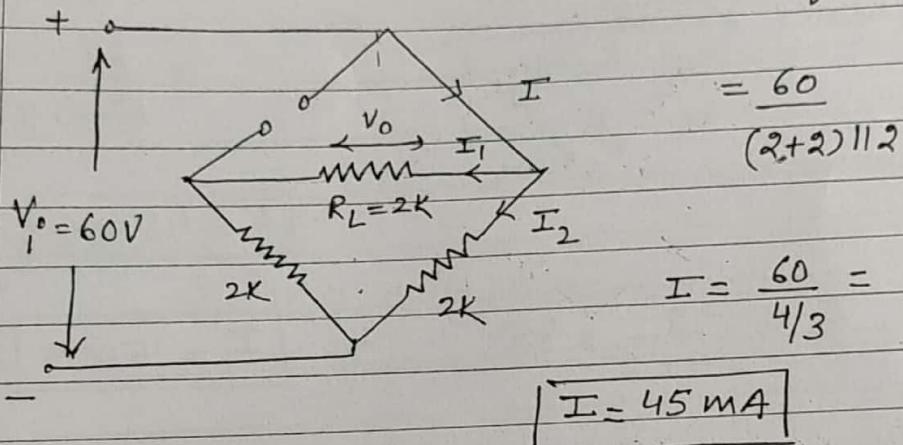

$$= \frac{60}{(2+2)/2}$$

$$I = \frac{60}{4/3} = \frac{60 \times 3}{4}$$

$$\boxed{I = 45 \text{ mA}}$$


$$\Rightarrow I_1 = \frac{2}{2+2} \times 45 \quad (\text{using current divider Rule})$$

$$\boxed{I_1 = 15 \text{ mA}}$$

$$\therefore V_o = I_1 \times R_L$$

$$= 2 \times 15 \text{ mA}$$


$$\boxed{V_o = 30 \text{ V}}$$

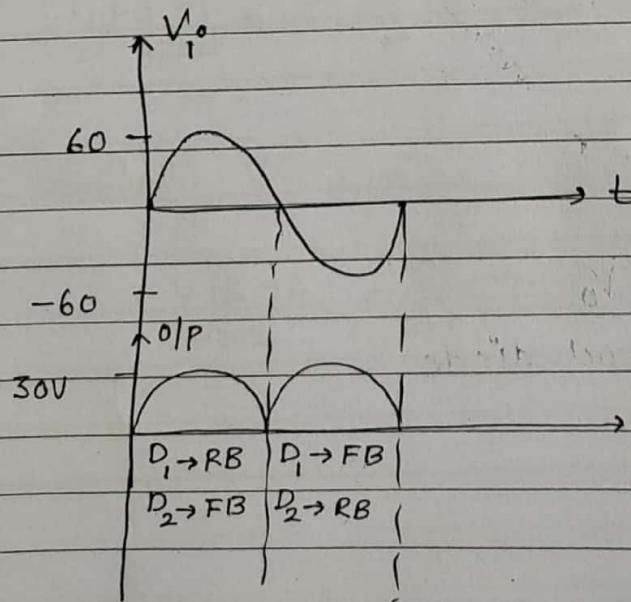

step 2 During (-ve) Half cycle :-

$D_1 \rightarrow FB$

$D_2 \rightarrow RB$

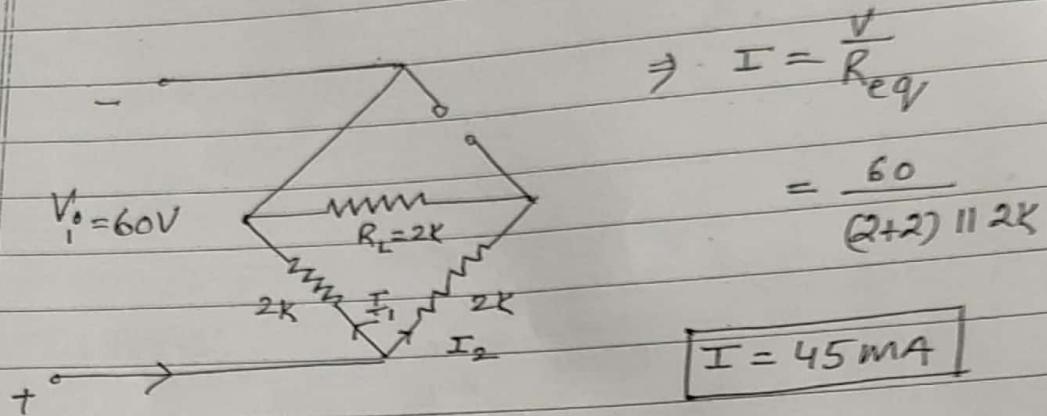

$$\therefore I_1 = \frac{2}{4+2} \times 45 \Rightarrow I_1 = 15 \text{ mA}$$

$$\therefore V_o = 15 \text{ mA} \times 2k$$

$$V_o = 30 \text{ V}$$

② PIV :- PIV of each diode =

$$③ V_{dc} \therefore V_{dc} = \frac{2V_m}{\pi} = \frac{2 \times 30}{\pi} = 19.09 \text{ V}$$


$$④ V_{rms} \therefore V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{30}{\sqrt{2}} = 21.21 \text{ V}$$

Ans

QN04


Page No.

Date: / /

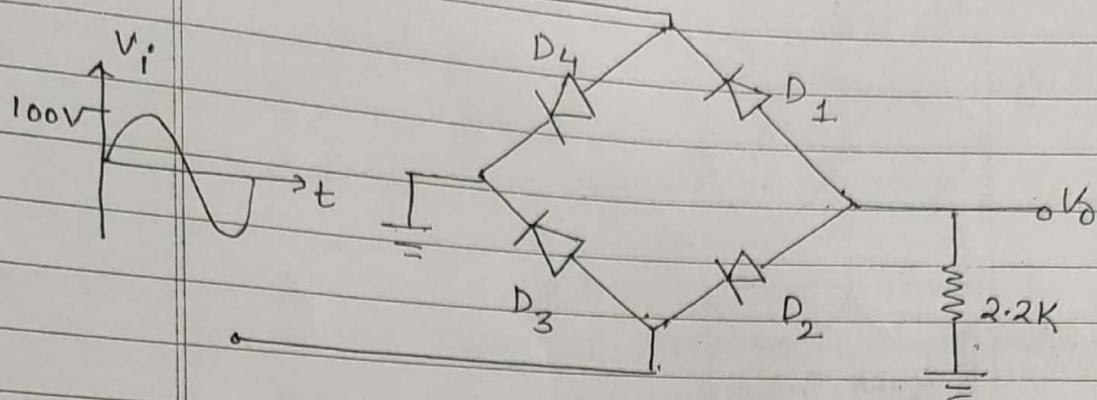


Find - ① V_o
② PIV of each diode.

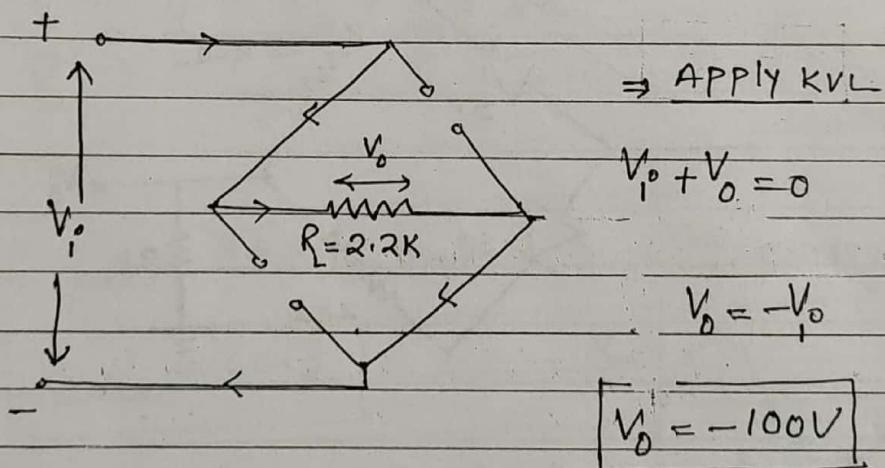Ans:- During (+ve) Half cycle: $D_1 \rightarrow RB$ $D_2 \rightarrow FB$
 $D_3 \rightarrow RB$ $D_4 \rightarrow FB$




\Rightarrow Similarly V_o , during (-ve) Half cycle

$$V_o = -100V$$

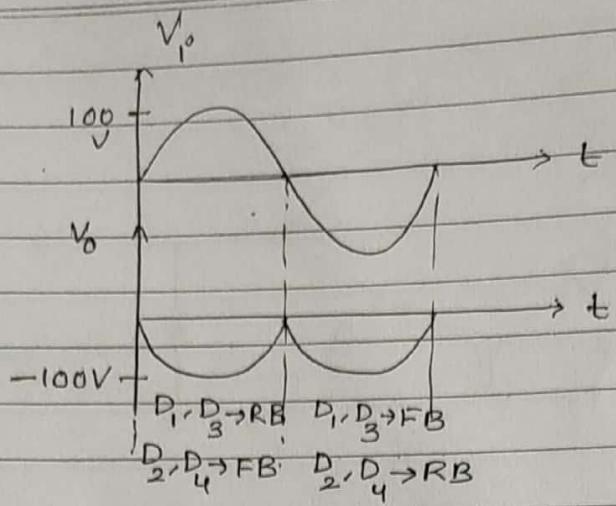

\Rightarrow PIV of each diode = $V_m = 100V$ Ans

Q N 05

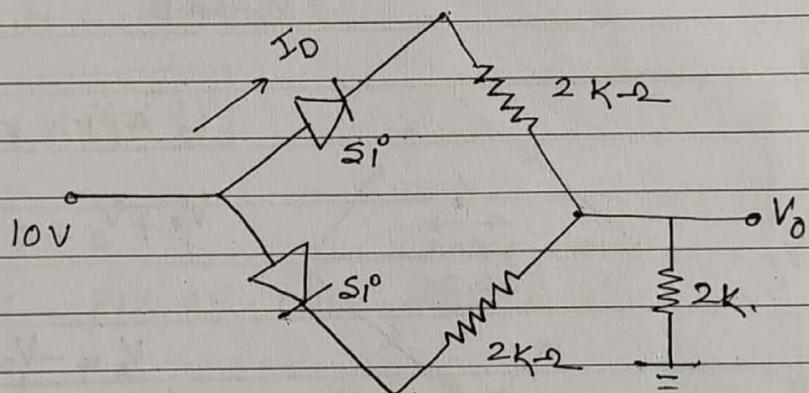


Find ① V_o

② I_D

Soln: The given ckt can be Re-drawn As :-

QNo6

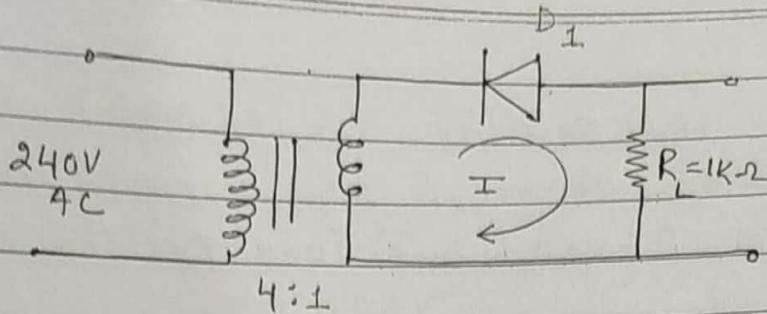

Find the Value of Average Load Voltage (V_{Ldc}) and sketch o/p Waveform.

Solⁿ: We know

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

Where V_1 → Input AC voltage
 V_2 → rms value of Secondary Voltage

$$\Rightarrow \frac{V_1}{V_2} = \frac{4}{1} \Rightarrow \frac{240}{V_2} = \frac{4}{1} \Rightarrow V_2 = 60V$$


\downarrow
rms value

$$\Rightarrow V_{2(\max)} = \sqrt{2} \times V_{2(\text{rms})}$$

$$V_{2(\max)} = 60\sqrt{2}$$

$$\therefore V_{Ldc} = -\frac{V_m}{\pi}$$

$$= -\frac{60\sqrt{2}}{\pi}$$

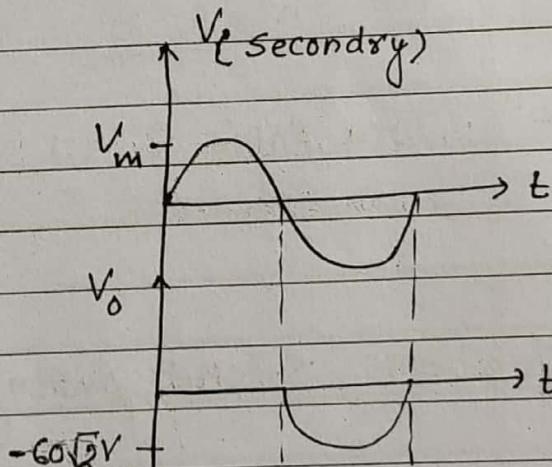

$$V_{Ldc} = -27V$$

Ans

Ques


For Half Wave Rectifier, the Resistance of transformer secondary is 5Ω , forward resistance of diode $R_F = 50\Omega$ and Load Resistance is $1k\Omega$.

Calculate - ① Average load current and load Voltage

② RMS load current and load Voltage

③ DC Load Power and AC Input power

④ Rectification Efficiency

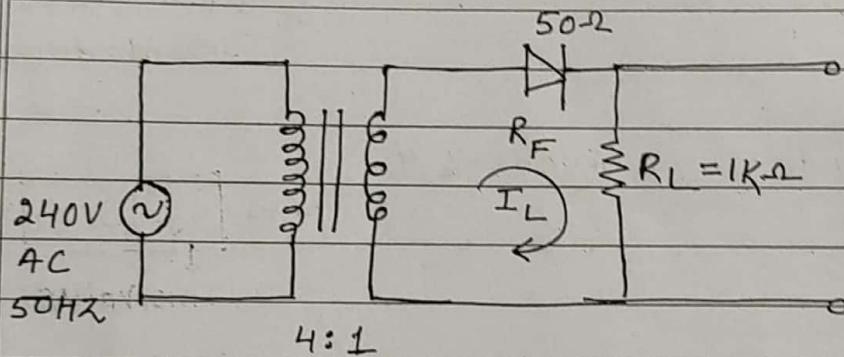

Sol: Turn Ratio is 4:1, therefore it is a stepdown transformer.

Given $R_s = 5\Omega$

$$\Rightarrow \text{rms Secondary Voltage } V_{S(\text{rms})} = \frac{N_2}{N_1} \times V_{1(\text{rms})}$$

$$= \frac{1}{4} \times 240$$

$$= 60V$$

$$\Rightarrow \therefore V_{S(\max)} = \frac{2}{\sqrt{2}} V_{S(\text{rms})}$$

$$= 60\sqrt{2}$$

$$= 84.8V$$

$$\Rightarrow \text{Peak load current} = \frac{V_m}{R_F + R_S + R_L} = \frac{84.8}{5\Omega + 50\Omega + 1000\Omega}$$

$$I_m = 80.4 \text{ mA}$$

$$① \quad \therefore I_{Ldc} = \frac{I_m}{\pi} = \frac{80.4}{\pi} = 25.6 \text{ mA}$$

$$② \quad V_{Ldc} = I_{Ldc} \times R_L = 25.6 \times 1 \text{ k}\Omega = 25.6V$$

$$③ \quad I_{L(\text{rms})} = \frac{I_m}{2} = \frac{80.4}{2} = 40.2 \text{ mA}$$

$$④ \quad V_{L(\text{rms})} = I_{L(\text{rms})} \times R_L = 40.2 \times 1 \text{ k}\Omega = 40.2V$$

$$⑤ \quad \text{DC Load Power} := P_{Ldc} = V_{Ldc} \times I_{Ldc} = 25.6 \times 25.6$$

$$P_{Ldc} = 655.36 \text{ mWatt}$$

(6) AC Input Power :-

$$P_{ac} = \frac{I^2}{s(\text{rms})} \times (R_s + R_F + R_L)$$

$$= (40.2 \times 10^{-3})^2 \times (5 + 50 + 1000)$$

$$\boxed{P_{ac} = 1.7 \text{ Watt}}$$

(7) Rectification Efficiency :-


$$\eta = \frac{P_{Ldc}}{P_{Lac}} \times 100 = \frac{655.36 \times 10^{-3}}{1.7} \times 100$$

$$\boxed{\eta = 38.5\%}$$

Ans

MP


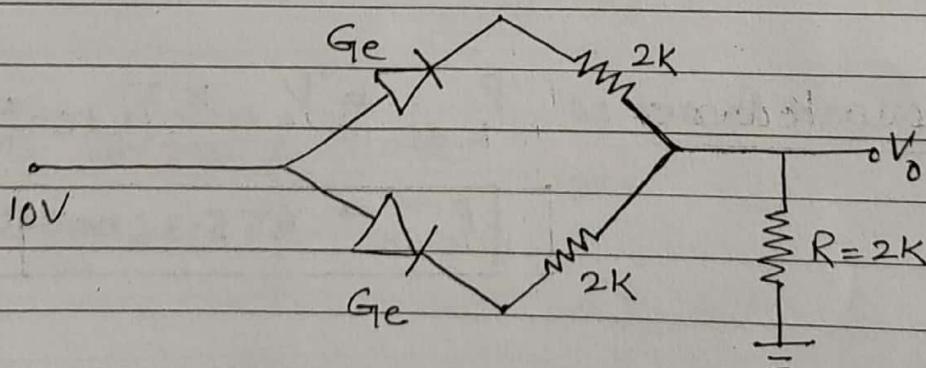
QN08 Determine V_o and I_D for given ckt.



\Rightarrow Diodes are ideal

Q01:

[Page No.
Date: / /]

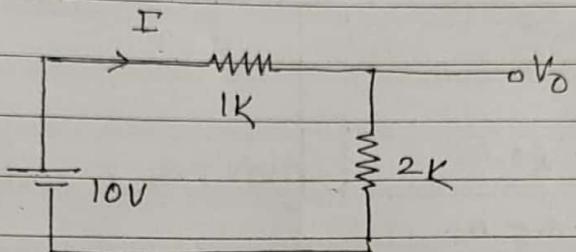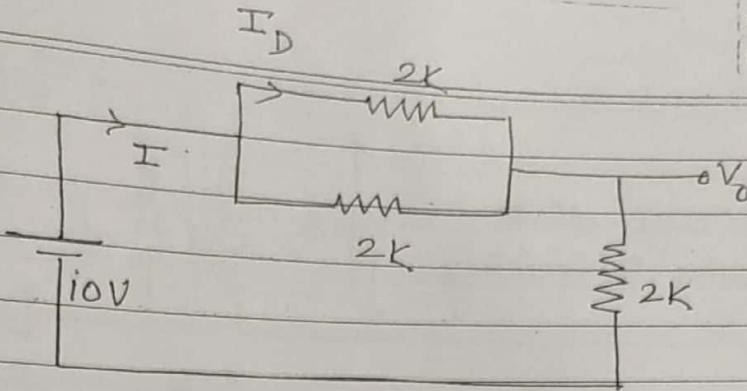

$$I = \frac{V}{R_{\text{Req}}} = \frac{10}{3k}$$

$$I = 3.3 \text{ mA}$$

$$\Rightarrow \therefore I_D = \frac{I}{2} = \frac{3.3}{2} = 1.66 \text{ mA}$$

$$\Rightarrow V_o = 2k \times I = 2k \times 3.3$$


$$V_o = 6.6 \text{ V}$$

Ans

Q09 A Full wave Rectifier with a centre tapped transformer supplies a dc current of 100 mA to a load resistance of $R = 20 \Omega$. The secondary resistance of transformer is 1Ω . Each diode has a forward resistance of 0.5Ω . Determine-

- (1) rms Value of Signal Voltage across each half of Secondary
- (2) DC Power supplied to load
- (3) AC Power Input to rectifier

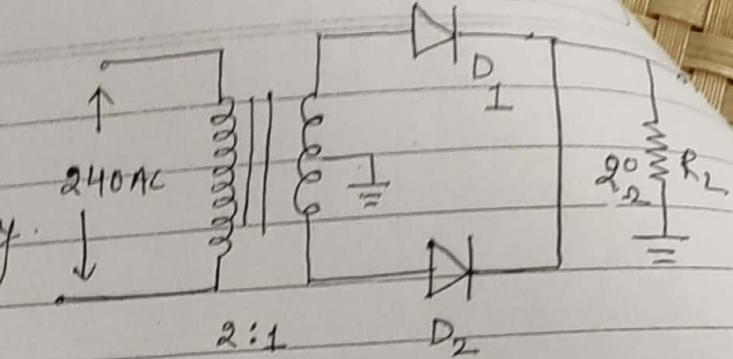4. PIV of each diode 240 AC
 5. Conversion Efficiency.



Given:

$$\frac{N_1}{N_2} = \frac{2}{1}$$

$$R_L = 20 \Omega$$

$$R_F = 0.5 \Omega$$

$$R_S = 1 \Omega$$

$$\therefore I_{Ldc} = 100 \text{ mA}$$

We know

$$\frac{I_{Ldc}}{I_m} = \frac{2}{\pi}$$

$$I_m = \frac{\pi \times I_{Ldc}}{2} = \frac{\pi \times 100 \text{ mA}}{2}$$

$$\boxed{I_m = 157 \text{ mA}}$$

We know

$$I_m = \frac{V_m}{R_S + R_F + R_L}$$

$$R_S + R_F + R_L$$

$$\therefore \frac{V_m}{R_S + R_F + R_L} = \frac{I_m}{0.5 + 1 + 20} = 157$$

$$V_m = I_m (R_S + R_F + R_L)$$

$$V_m = 157 \times (0.5 + 1 + 20)$$

$V_m = 3.3755 V$

$$\Rightarrow \therefore V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{3.3755}{\sqrt{2}}$$

①

$V_{rms} = 2.4 \text{ Volts}$

②

DC Power :- $P_{dc} = I_{dc}^2 \times R_L$

$$= (100 \times 10^{-3})^2 \times 20 \Omega$$

$P_{dc} = 0.2 \text{ Watts}$

③

AC I/P Power :- $P_{ac} = \frac{V_{rms}^2}{R_s + R_f + R_L}$

$$= \left(\frac{V_m}{\sqrt{2}} \right)^2 \times \frac{1}{(R_s + R_f + R_L)}$$

$$= \left(\frac{3.3755}{\sqrt{2}} \right)^2 \times \frac{1}{(20 + 1 + -5)}$$

$P_{ac} = 0.2649 \text{ Watt.}$

(4) PIV of each diode = $2V_m = 2 \times 3.3755$
= $6.75V$

(5) Conversion Efficiency :-

$$\eta = \frac{P_{Ldc}}{P_{Lac}} \times 100 = \frac{0.2}{0.2649} \times 100$$

$$\boxed{\eta = 75.58 \%}$$

Ans