

NUMERICALS (op-amp)

Q1) The two input terminals of an op-amp are connected to voltage signals of strength 745 mV and 740 mV respectively. The gain of op-amp in differential mode is 5×10^5 and its CMRR is 80 db. Calculate :-

- (1) Differential Input
- (2) Common mode Input
- (3) Differential op
- (4) Common mode op
- (5) Output voltage
- (6) % Error due to Common mode

Soln :- Given $V_1 = 745 \text{ mV}$ $CMRR = 80 \text{ db}$
 $V_2 = 740 \text{ mV}$
 $A_d = 5 \times 10^5$

① Differential Input :- $V_d = |V_1 - V_2|$

$$= |745 - 740|$$

$$V_d = 5 \text{ mV}$$

② Common mode Input :- $V_{CM} = \left| \frac{V_1 + V_2}{2} \right| = \left| \frac{745 + 740}{2} \right|$

$$V_{CM} = 742.5 \text{ mV}$$

A_{CM}

We know

$$CMRR \text{ in } dB = 20 \log_{10} \frac{A_d}{A_{CM}}$$

$$80 = 20 \log_{10} \frac{5 \times 10^5}{A_{CM}}$$

$$4 = \log_{10} \frac{5 \times 10^5}{A_{CM}} \Rightarrow 10^4 = \frac{5 \times 10^5}{A_{CM}}$$

$$\Rightarrow \boxed{A_{CM} = 50}$$

③ Differential o/p :- Differential o/p = $A_d V_d$

$$= 5 \times 10^5 \times 5 \mu V$$

$$= 5 \times 10^5 \times 5 \times 10^{-6}$$

$$= 25 \times 10^{-1}$$

$$\boxed{\text{Differential o/p} = 2.5 V}$$

④ Common mode o/p :- Common mode o/p = $A_{CM} V_{CM}$

$$= 50 \times 742.5 \mu V$$

$$= 50 \times 742.5 \times 10^{-6}$$

$$= 37125 \times 10^{-6}$$

$$\boxed{\text{Common mode o/p} = 0.0371 V}$$

⑤ Output Voltage :- $V_o = A_d V_d + A_{CM} V_{CM}$

$$V_o = 2.5V + 0.371V$$

$$V_o = 2.53V$$

⑥ % Error due to Common mode :-

$$\% \text{ Error} = \frac{A_{CM} V_{CM}}{A_d V_d + A_{CM} V_{CM}} \times 100$$

$$= \frac{0.371}{2.53} \times 100$$

$$\% \text{ Error} = 1.466\%$$

Ans

Q2:- Find CMRR if $A_d = 80 \text{ db}$ and $A_{CM} = 2 \times 10^3$.

Soln :- We know $CMRR = \frac{A_d}{A_{CM}}$

but $A_d = 80 \text{ db}$. First we need to convert A_d from db to without db.

$$A_d \text{ in db} = 20 \log_{10} A_d$$

$$80 = 20 \log_{10} A_d$$


$$4 = \log_{10} A_d \Rightarrow A_d = 10^4$$

Now

$$CMRR = \frac{10^4}{2 \times 10^3}$$

$$CMRR = 5 \quad \text{Ans}$$

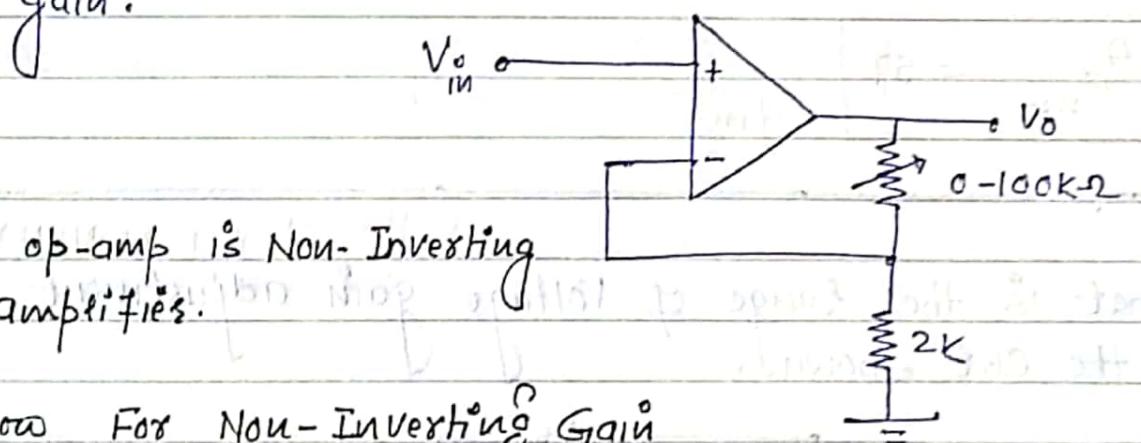Q3: The Variable Resistance varies from zero to $100\text{ k}\Omega$. Find the maximum and minimum closed loop voltage gain.



Given op-amp is Non-Inverting amplifier.

We know For Non-Inverting Gain

$$A_F = 1 + \frac{R_F}{R_I}$$

Here $R_F = 0-100\text{ k}\Omega$ (Variable) & $R_I = 2\text{k}$

① Minimum Gain :-

Ans :-

$$A_{F_{\min}} = 1 + \frac{R_{F_{\min}}}{R_I}$$

$$= 1 + \frac{0}{2k}$$

$$A_{F_{\min}} = 1$$

②

Maximum Gain :-


$$A_{F_{\max}} = 1 + \frac{R_{F_{\max}}}{R_I}$$

$$= 1 + \frac{100k}{2k}$$

$$A_{F_{\max}} = 51$$

Ans

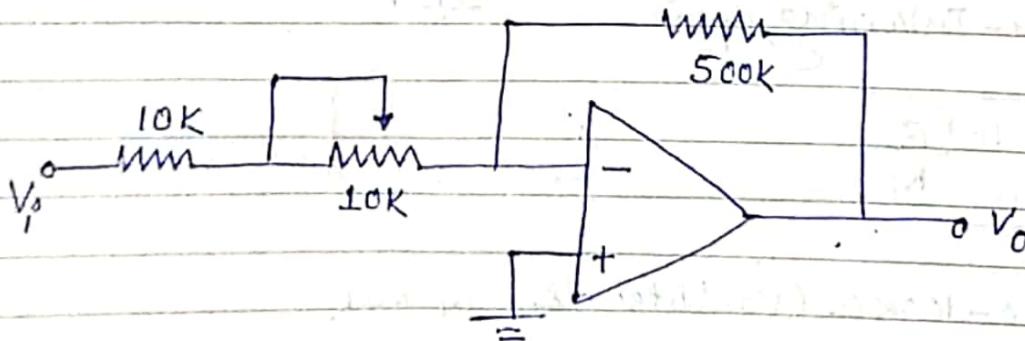Q4) What is the range of Voltage gain adjustment in the ckt shown.



Ques:- This is Inverting op-amp, whose voltage gain is given by :-

$$A_F = -\frac{R_F}{R_I}$$

Here R_F is Fixed in the ckt diagram.

① Minimum Gain

$$A_{F_{\min}} = -\frac{R_F}{R_{I_{\max}}}$$

$$= -\frac{500K}{10+10}$$

$$A_{F_{\min}} = -25$$

② Maximum Gain

$$A_{F_{\max}} = -\frac{R_F}{R_{I_{(\min)}}}$$


$$= -\frac{500K}{10-10}$$

$$A_{F_{(\max)}} = -50$$

\therefore Range of Voltage Gain = -25 to -50

Ans

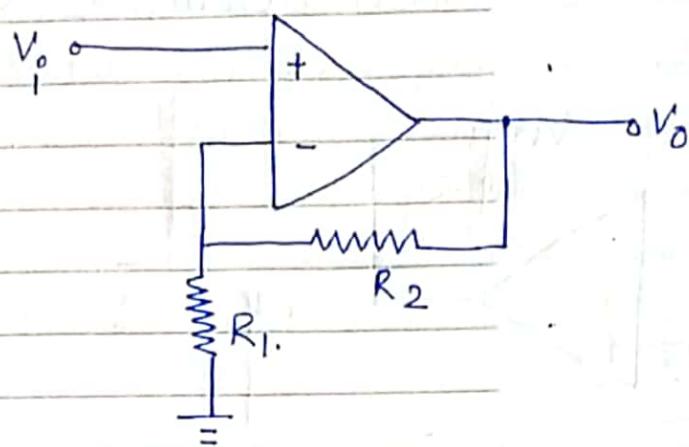Ques) Determine output of the ckt shown below.



Soln:- This is Non-Inverting op-amp. The Gain of Non-Inverting op-amp is given by :-

$$A_F = 1 + \frac{R_F}{R_I}$$

Here $R_F = R_2$
 $R_I = R_1$


$$\therefore A_F = 1 + \frac{R_2}{R_1} \quad \text{but Gain } A_F = \frac{V_o}{V_i}$$

$$\therefore \frac{V_o}{V_i} = 1 + \frac{R_2}{R_1}$$

$$\therefore V_o = \left(1 + \frac{R_2}{R_1}\right) V_i$$

Ans

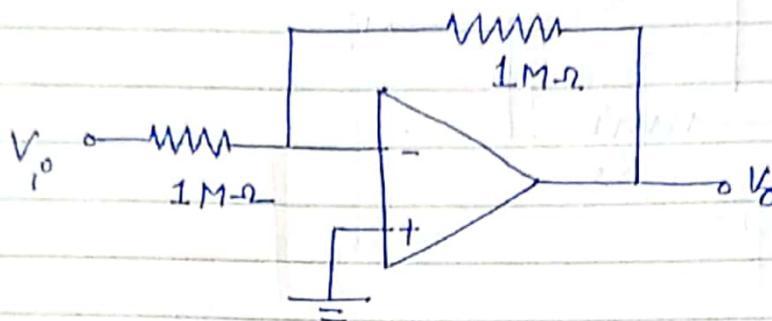Q No 7 Compute Input Impedance and Voltage Gain of the amplifiers CKT shown below:- Op-amp is Ideal.



Sol^u :- This is Inverting op-amp whose gain

$$A_F = -\frac{R_F}{R_I}$$

Where $R_F = 1M\Omega$

$R_I = 1M\Omega$

$$\therefore A_F = -1$$

Input Impedance :- Input Impedance = R_I

$$\boxed{\text{I/P Impedance} = 1M\Omega} \quad \underline{\text{Ans}}$$

Non

Q8 Design an Inverting op-amp with a gain of +15. Assume ideal op-amp and Resistances should not exceed $30\text{ k}\Omega$.

Sol:- Gain of Non-Inverting op-amp is given by :-

$$A_F = 1 + \frac{R_F}{R_I}$$


$$15 = 1 + \frac{R_F}{R_I}$$

Assume $R_F = 20\text{ k}\Omega$

$$15 = 1 + \frac{20}{R_I}$$


$$R_I = 1.4\text{ k}\Omega$$

Design Circuit:-

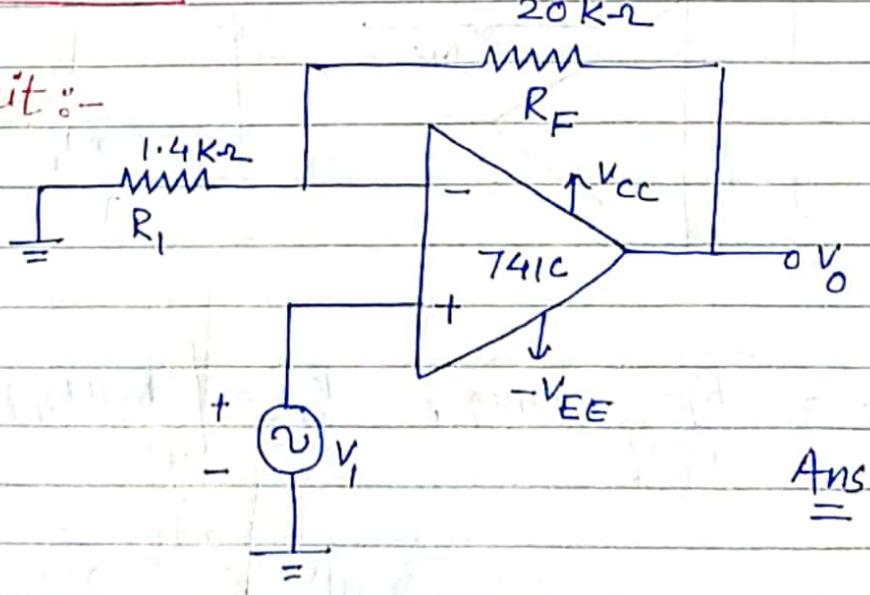


Ans

Q9 For the ckt shown, Find out V_o .

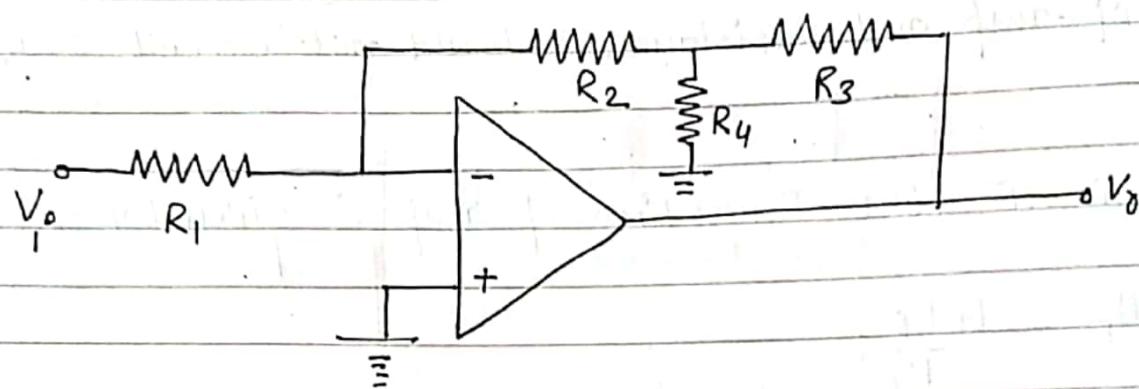

Soln:- Here $(R_2 \parallel R_4)$ which is in series with R_3 .

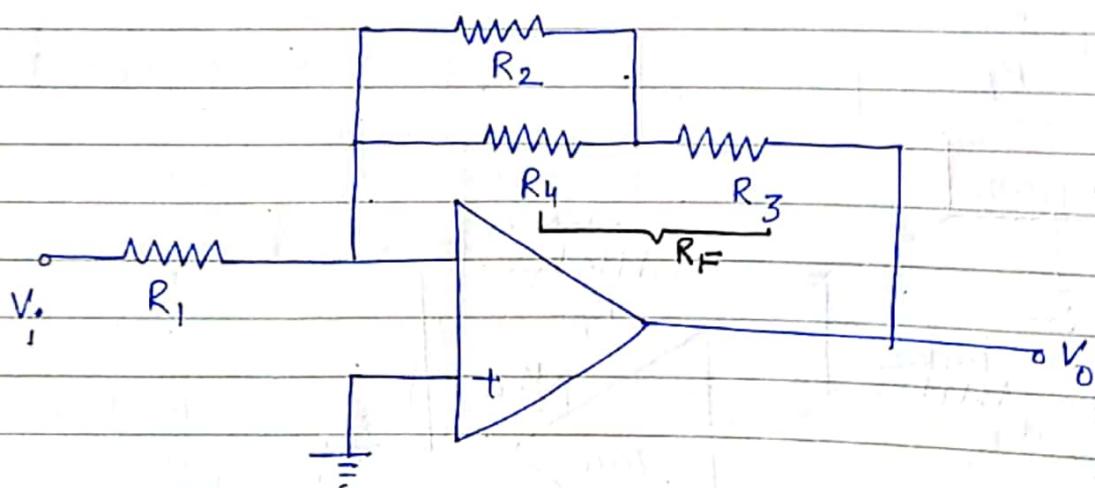→ This is Inverting op-amp, its Simplified ckt is shown below:-



$$\text{Gain } A_F = -\frac{R_F}{R_1} \quad \text{Where } R_F = [(R_2 \parallel R_4) + R_3]$$

$$\therefore \frac{V_o}{V_i} = A_F = - \frac{(R_2 \parallel R_4) + R_3}{R_1}$$

$$V_o = - \frac{(R_2 \parallel R_4) + R_3}{R_1} \times V_i$$

Ans

Q10 For an inverting op-amp, the input voltage is sine wave with a peak voltage of 2V peak and freq. of 1 kHz.

Assume $R_1 = 1\text{ k}\Omega$, $R_F = 10\text{ k}\Omega$ and supply voltage to be $\pm 15\text{V}$. Draw Input and output voltage waveforms and explain them.

Solⁿ :-

This is a Inverting op-amp whose Gain is -

$$A_F = -\frac{R_F}{R_1}$$

Here $R_F = 10\text{ k}\Omega$, $R_1 = 1\text{ k}\Omega$

$$\therefore A_F = \frac{V_o}{V_i} = -\frac{R_F}{R_1}$$

$$V_o = -\frac{R_F}{R_1} \times V_i \quad \text{put all values.}$$

$$V_o = -\frac{10}{1} \times 2V \quad (\text{As Input } V_i = 2V)$$

$$V_o = -20V$$

but As we know, op-amp is restricted to amplify the input voltage to $\pm V_{sat}$ only.

$$\text{Here } +V_{sat} = +V_{cc}$$

$$\text{where } +V_{cc} = +15 \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{ Given}$$


$$\& -V_{ee} = -15$$

$$-V_{sat} = -V_{ee}$$


means o/p voltage is

restricted to $\pm 15V$ only. Hence o/p voltage ($V_o = 20V$)

gets clipped off after $\pm 15V$.

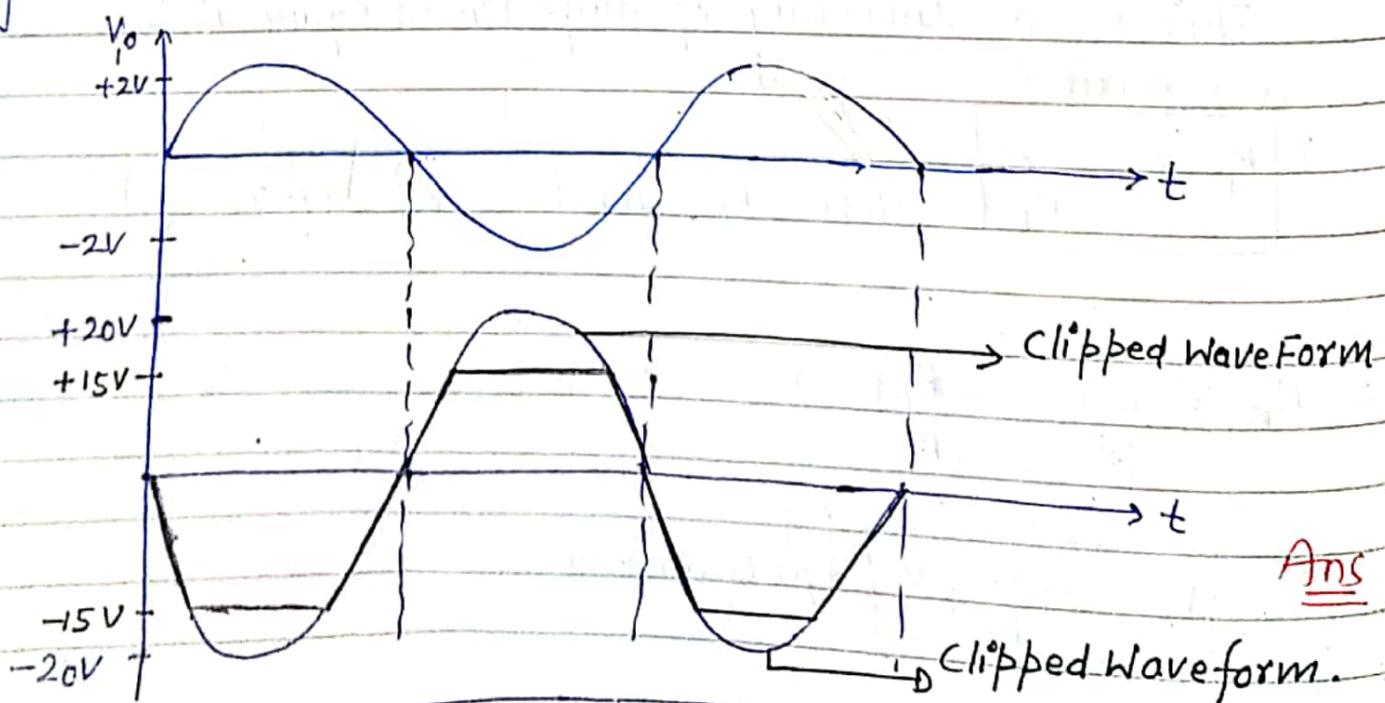

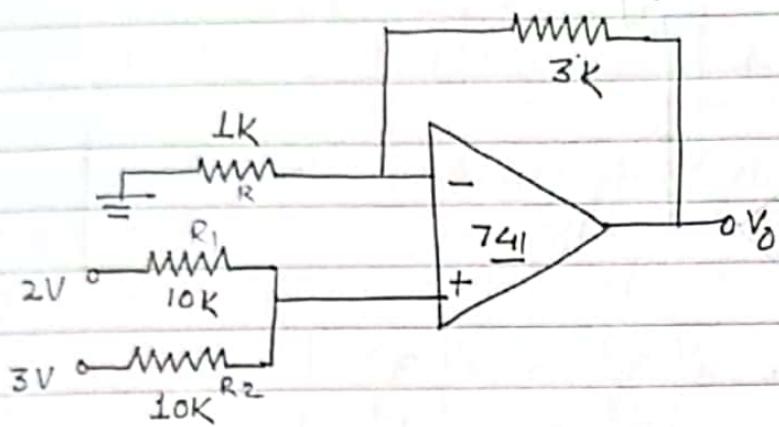Q. No. 11 Find out V_o for the given ckt.



Soln. :- This is Non-Inverting Summing Amp² Whose


$$V_o = \left[\frac{R_2 V_1 + R_1 V_2}{R_1 + R_2} \right] \left[1 + \frac{R_F}{R} \right]$$

$$= \frac{10 \times 2 + 10 \times 3}{10 + 10} \times 1 + \frac{3}{1}$$

$$= \frac{20 + 30}{20} \times 4$$

$$= \frac{50 \times 4}{20} = 10 \text{ Volts} \quad \underline{\text{Ans}}$$

Q1012 Find out V_o for the given ckt.

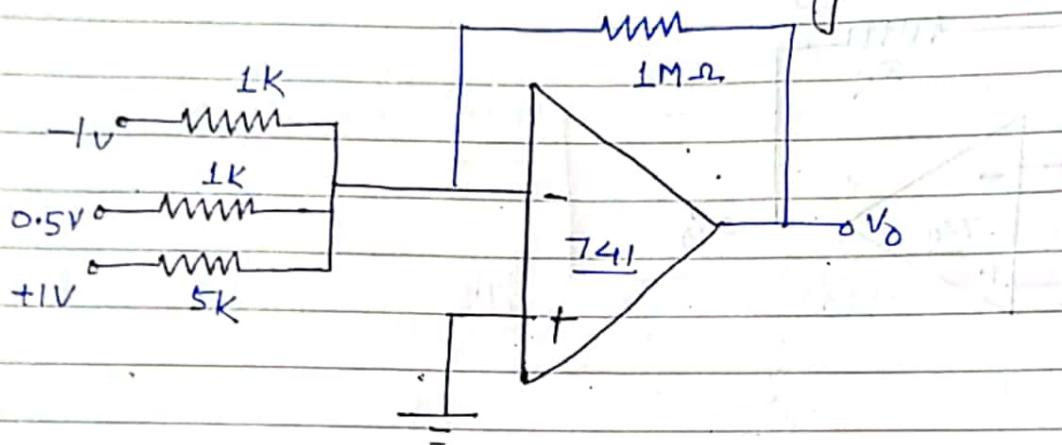

Sol: This is Inverting Summing Amplifier Whose

$$V_o = - \left[\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 \right]$$

$$= - \left[\frac{10k\Omega}{1k\Omega} \times (-1) + \frac{10k\Omega}{1k\Omega} (0.5) + \frac{10k\Omega}{5k\Omega} \times (1V) \right]$$

$$V_o = - (-10 + 5 + 2)$$

$$V_o = 3V$$

Ans

Q1013 Design a summing Amp's whose V_o is given by -

$$V_o = -2V_a + 3V_b - 5V_c$$

Resistances used should not exceed $30k\Omega$.

Soln:- Given $V_o = -2V_a + 3V_b - 5V_c$

$$V_o = -(2V_a - 3V_b + 5V_c) \quad \text{--- (1)}$$

We know

V_o of Inverting Amp Adder is given by :-

$$V_o = - \left[\frac{R_F}{R_1} V_a + \frac{R_F}{R_2} V_b + \frac{R_F}{R_3} V_c \right] \quad \text{--- (2)}$$

By Comparing Equations (1) & (2) :-

$$\frac{R_F}{R_1} = 2$$

$$\frac{R_F}{R_2} = 3$$

Ignore (-ve) sign as R
can't be negative


$$\frac{R_F}{R_3} = 5$$

Assume $R_F = 10 \text{ k}\Omega$

$$R_1 = \frac{10}{2} = 5 \text{ k}\Omega$$


$$R_3 = 2 \text{ k}\Omega$$

$$R_2 = 3.3 \text{ k}\Omega$$

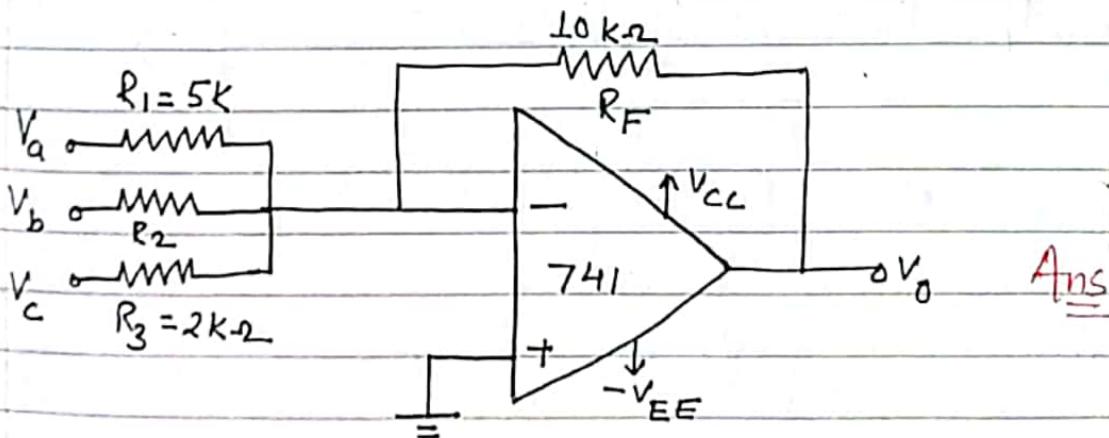

Ans

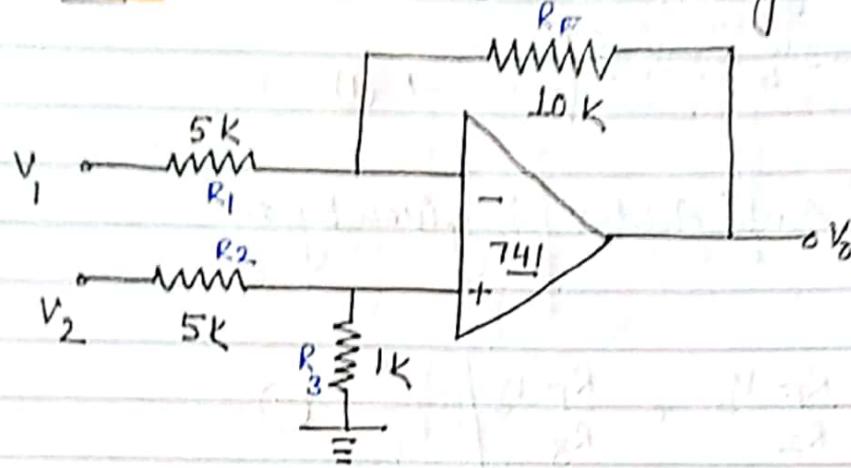Q1014) Find the V_o for the given circuit



Solⁿ: This is op-amp AS subtractor whose V_o can be calculated by applying superposition theorem.

Step 1:- Consider Input V_1 , $V_2 = 0$, o/p is V_{o1} .

$$V_{o1} = -\frac{R_F}{R_1} \times V_1$$

$$= -\frac{10\text{K}}{5\text{K}} \times V_1$$

$$V_{o1} = -2V_1$$

Step 2 :- Consider Input V_2 , $V_1 = 0$

Output due to Input $V_2 = V_{02}$

$$\therefore V_{02} = \left(1 + \frac{R_F}{R_1}\right) V_2 \left(\frac{R_3}{R_2 + R_3}\right)$$

$$= \left(1 + \frac{10k}{5k}\right) V_2 \left(\frac{1}{1+5}\right)$$

$$= 3 V_2 \times \frac{1}{6}$$

$$V_{02} = .5 V_2$$

$$\therefore \text{Total } V_0 = V_{01} + V_{02}$$

$$V_0 = -2V_1 + .5V_2 \quad \underline{\underline{\text{Ans}}}$$

OR (When asked for 2 marks)


We know V_0 For op-amp as Subtractor is given by :-

$$V_0 = \left(-\frac{R_F}{R_1}\right) V_1 + \left[1 + \frac{R_F}{R_1}\right] V_2 \left[\frac{R_3}{R_2 + R_3}\right], \text{ put all values :-}$$

$$V_0 = -\frac{10}{5} \times V_1 + \left[1 + \frac{10}{5}\right] V_2 \left[\frac{1}{1+5}\right] \Rightarrow V_0 = -2V_1 + .5V_2 \quad \underline{\underline{\text{Ans}}}$$

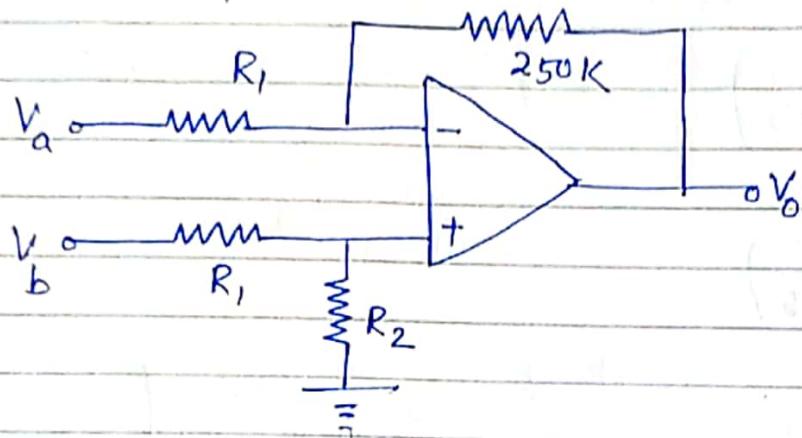Q1015 Find the values of R_1 & R_2 For the o/p

to be $V_o = -5V_a + 3V_b$ for the ckt shown below.



Sol'n :- This is op-amp as subtractor whose V_o is —

$$V_o = -\frac{R_F}{R_1} V_a + \left[1 + \frac{R_F}{R_1} \right] V_b \left[\frac{R_2}{R_1 + R_2} \right] \rightarrow ①$$

Given $V_o = -5V_a + 3V_b \rightarrow ②$

Compare Eq's ① & ② :-

$$\frac{+R_F}{R_1} = 5$$

$$R_1 = \frac{R_F}{5} = \frac{250K}{5} \Rightarrow R_1 = 50K$$

$$2 \left[1 + \frac{R_F}{R_1} \right] \left[\frac{R_2}{R_1 + R_2} \right] = 3$$

$$\left(1 + \frac{250}{50} \right) \left(\frac{R_2}{50 + R_2} \right) = 3$$

$$0.6 \times \frac{R_2}{50 + R_2} = 3$$

$$\frac{R_2}{50 + R_2} = \frac{1}{2} \Rightarrow R_2 = 50 \text{ k}\Omega \quad \underline{\text{Ans}}$$

QNO16 A sinusoidal signal with peak value 6 mV and 2 KHz Freq. is applied to the input of an ideal op-amp integrator with $R_{in} = 100 \text{ k}\Omega$ and $C_f = 1 \mu\text{F}$. Find o/p voltage.

SOLN Given $V_m = 6 \text{ mV}$, $R_{in} = 100 \text{ k}\Omega$, $C_f = 1 \mu\text{F}$, $f = 2 \text{ KHz}$

The o/p voltage of an Integrator is given by -

$$V_o = - \frac{1}{R_{in} C_f} \int A \sin \omega t \, dt \rightarrow \text{for sinusoidal Input}$$

$$= - \frac{1}{R_{in} C_f} \int A \sin(2\pi f) t \, dt \quad \because (\omega = 2\pi f)$$

$$2. \left[1 + \frac{R_F}{R_1} \right] \left[\frac{R_2}{R_1 + R_2} \right] = 3$$

$$\left(1 + \frac{250}{50} \right) \left(\frac{R_2}{50 + R_2} \right) = 3$$

$$0.6 \times \frac{R_2}{50 + R_2} = 3$$

$$\frac{R_2}{50 + R_2} = \frac{1}{2} \Rightarrow \boxed{R_2 = 50 \text{ k}\Omega} \quad \underline{\text{Ans}}$$

QNO16 A sinusoidal signal with peak value 6 mV and 2 kHz Freq. is applied to the input of an ideal op-amp integrator with $R_{in} = 100 \text{ k}\Omega$ and $C_f = 1 \mu\text{F}$. Find opv voltage.

Soln:- Given $V_m = 6 \text{ mV}$, $R_{in} = 100 \text{ k}\Omega$, $C_f = 1 \mu\text{F}$, $f = 2 \text{ kHz}$

The opv voltage of an Integrator is given by -

$$\boxed{V_o = -\frac{1}{R_{in} C_f} \int A \sin \omega t \, dt} \rightarrow \text{for sinusoidal Input}$$

$$= -\frac{1}{R_{in} C_f} \int A \sin(2\pi f t) \, dt \quad \because (\omega = 2\pi f)$$

$$= -\frac{1}{R_{in} C_f} \left[\frac{A}{2\pi f} (-\cos 2\pi f t) \right], \text{ put all values:}$$

$$= \frac{1}{100 \times 10^3 \times 1 \times 10^{-6}} \left[\frac{6 \times 10^{-3}}{2 \times \pi \times 2 \times 10^3} \cos (2\pi \times 2 \times 10^3 t) \right]$$

$$= 10 \left[4.77 \times 10^{-6} \cos (4000\pi t) \right]$$

$$V_o = 4.77 \times 10^{-6} \cos (4000\pi t)$$

Ans

Q No 17 An op-amp has a slew rate of $15V/\mu\text{sec}$. What is the power bandwidth for a peak op. voltage of $10V$.

Soln :- Given S. Rate = $15V/\mu\text{sec}$

$$V_{\text{Peak to Peak}} = 10V$$

$$V_m = \frac{V_{\text{P-P}}}{2}$$

$$V_m = \frac{10}{2} = 5V$$


We know $S\cdot \text{Rate} = 2\pi f V_m$

$$\therefore \text{Power Bandwidth } f = \frac{S\cdot \text{Rate}}{2\pi V_m} = \frac{15 \times 10^{-6}}{2 \times \pi \times 5}$$

$$f = 477.46 \text{ KHz}$$

Ans

Q No 18 :-

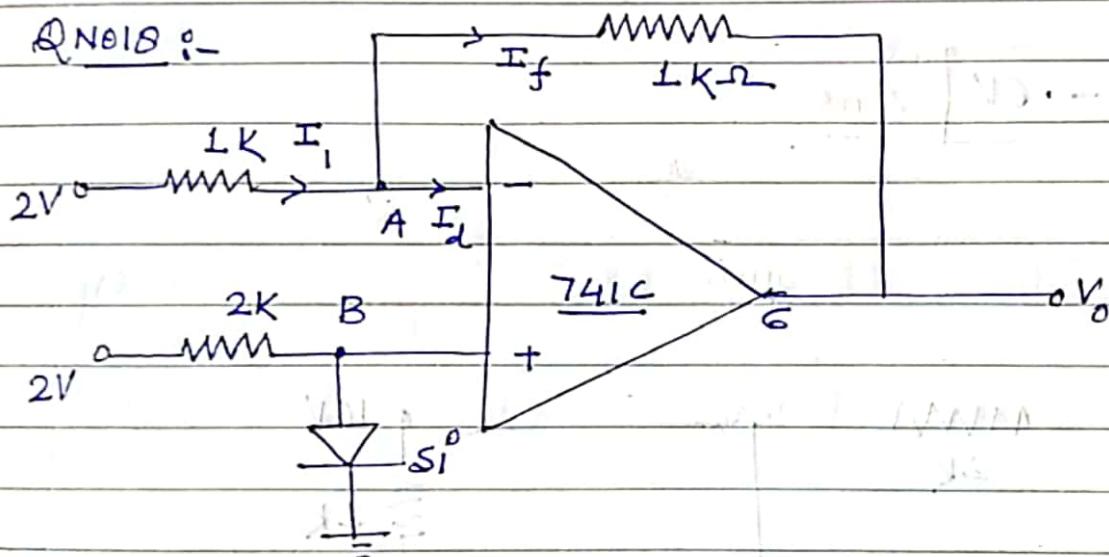

Find V_O .

$$\text{Soln} \therefore \text{KCL at node } A \therefore I_1 = I_d + I_f$$

but $I_d = 0$, As $h_{i0} = \infty$ of an ideal op-amp

$$\therefore I_1 = I_f$$

$$\frac{2 - V_A}{1K} = \frac{V_A - V_O}{1K}$$

$$2 - V_A = V_A - V_0$$


but from Virtual short concept $V_A = V_B$

and here $V_B = 0.7V$ $\therefore V_A = 0.7V$

$$2 - 0.7 = 0.7 - V_0$$

$$V_0 = -0.6V$$

Ans

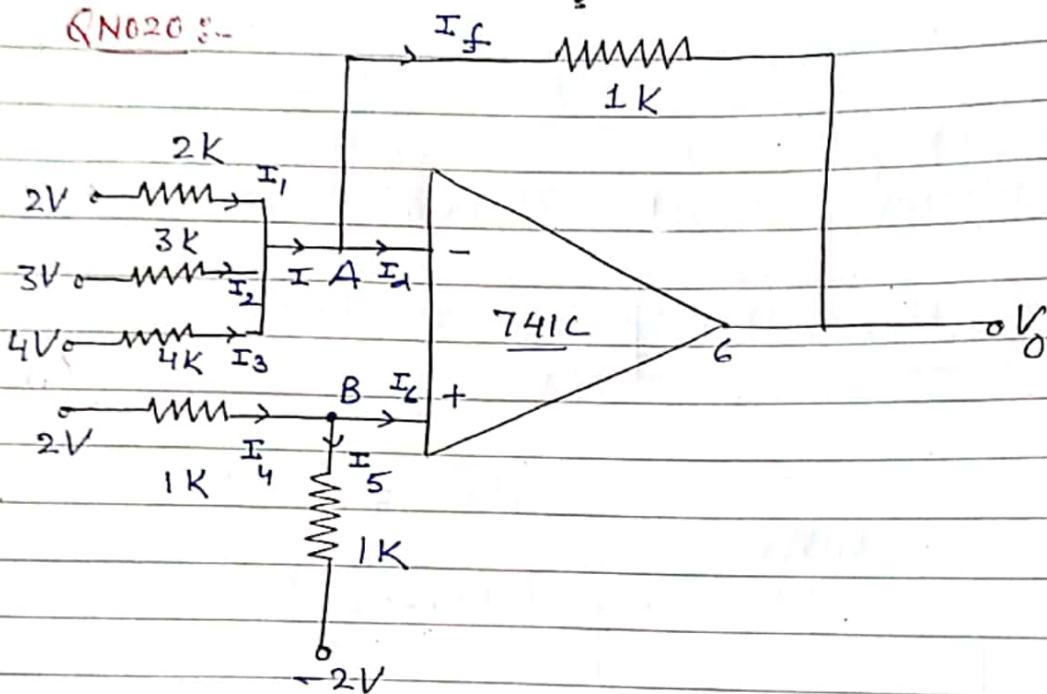

Calculate the o/p of op-amp. ckt.

Q301^u: - Apply KCL at B

$$I_4 = I_5 + I_6$$

but $I_6 = 0$, b'coz $R_o = \infty$ of op-amp.

$$\therefore I_4 = I_5$$

$$\frac{2-v}{1} = \frac{v_3 - (-2)}{1}$$

$$2 - \frac{V_B}{B} = \frac{V_B}{B} + 2 \Rightarrow \underline{\underline{V_B = 0}}$$

From. Virtual Ground Concept $\boxed{V_A = V_B}$

$$\therefore \boxed{V_A = 0}$$

→ Apply KCL at A :-

$$I = I_d + I_f$$

$$\begin{aligned} \text{but } I &= I_1 + I_2 + I_3 \\ &\& I_d = 0, \text{ b'coz } R_d = \infty \end{aligned} \quad \boxed{\quad}$$

$$\therefore I = I_f$$

$$I_1 + I_2 + I_3 = I_f$$

$$\frac{2-V_A}{2} + \frac{3-V_A}{3} + \frac{4-V_A}{4} = \frac{V_A - V_0}{1}$$

$$\text{put } \boxed{V_A = 0} \quad 1+1+1 = -V_0$$


$$\boxed{V_0 = -3V}$$

Ans

Q 21)

Find V_2 and V_3

$R_3 = 20K$

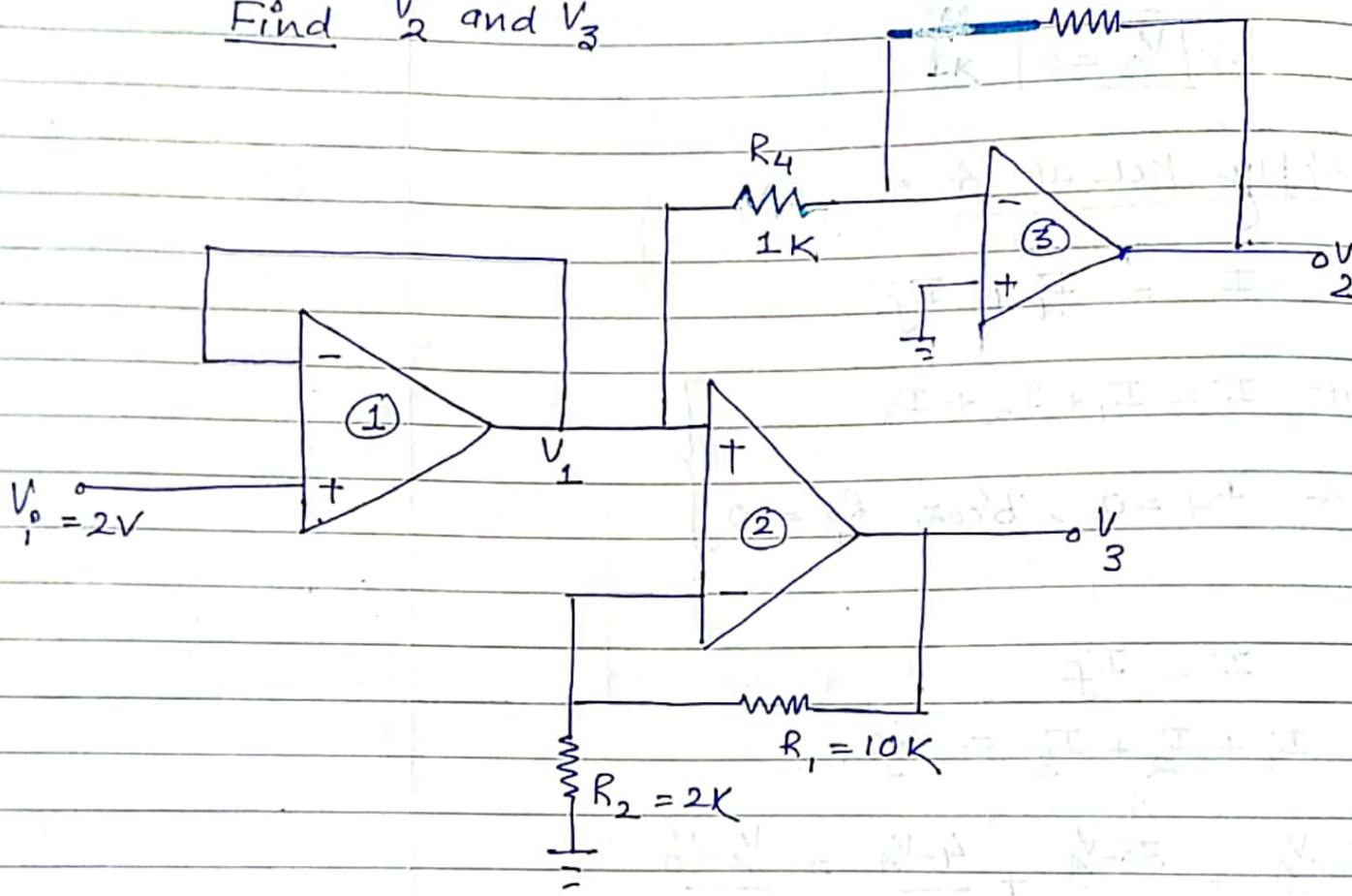

→ Op-amp 1, is voltage follower whose o/p $V_1 = V_i$

$$V_1 = 2V$$

→ Op-amp 2, is Non-inverting op-amp whose o/p is given by —

$$V_3 = \left(1 + \frac{R_f}{R_1}\right) V_1$$

$$= \left(1 + \frac{10}{2}\right) \times 2V$$

$$= (1 + 5) \times 2$$

$$\boxed{V_3 = 12V}$$

→ Op-amp 3, is inverting op-amp, whose output is given by -

$$V_2 = -\frac{R_f}{R_1} \times V_1$$

$$= -\frac{20}{1} \times 2V$$

$$\boxed{V_2 = -40V}$$

Ans