

TRANSFORMER (T/F)

- A transformer is a static device, which transfers electrical energy from one part of a magnetic circuit to another part of a magnetic circuit by mutual induction. During this transformation, frequency is constant. It's also step up and step down the voltage level.

➤ Classification of Transformer

L1

* According to construction	* According to use	* According to winding	* According to cooling
→ Core type	→ Instrument T/F Current T/F, Potential T/F	→ Single phase T/F	→ Natural cooled
→ Shell type	→ Distribution T/F Step UP T/F Step down T/F	→ 3- ^{ph} Transformer	→ Forced air cooled
→ Berry type (circular shell)	→ Power Transformer	→ Auto transformer	→ Water cooled.

➤ Advantages of Transformer

- It's economic to transmit the energy at high voltage
- It's also used for distribution purpose.
- Efficiency of T/F is very high.
- In electronics & control circuit, it matches the ^{device} impedance of a source and its load for max. power transfer.
- Simple in construction & robust.
- No moving part - static in nature.
- Isolate one circuit from another.

Construction in Detail:-

Wdg → Winding


→ There are two basic part of transformer

(i) Magnetic core

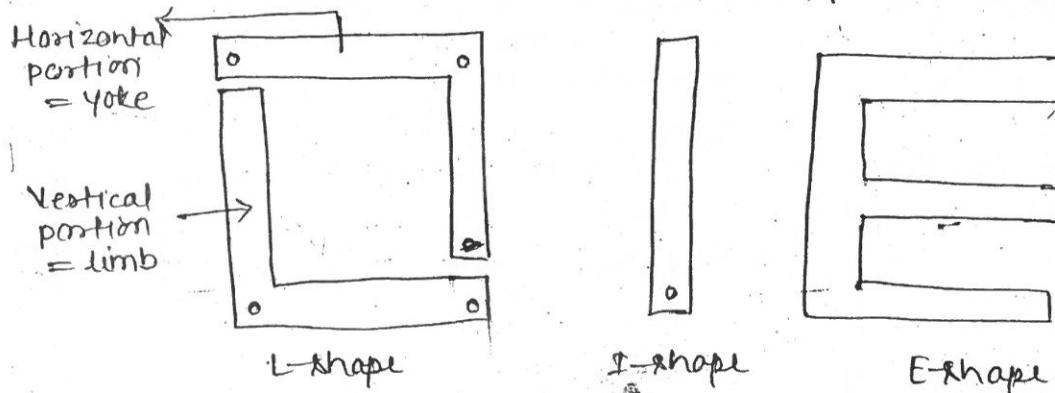(ii) Winding - Primary wdg & sec. wdg (1-Φ T/F)

Primary, secondary, tertiary wdg (3-Φ T/F)

→ To making a core, various type of stamping & laminations are used as L-shape, I-shape or E-shape



→ These laminations are isolated by enamelled Varnish to reduce eddy current losses.

→ To avoid airgap & to increase mechanical strength, overlapped laminations and staggered joints are used.



→ In a transformer, there is only HV & LV winding. And ~~which~~ winding which is connected to a load is ~~secondary~~ wdg & which is connected to excitation is called primary wdg.

→ HV - high voltage wdg

→ LV - low voltage wdg.

➤ Core-type transformer:-

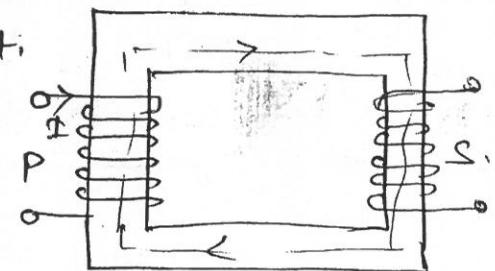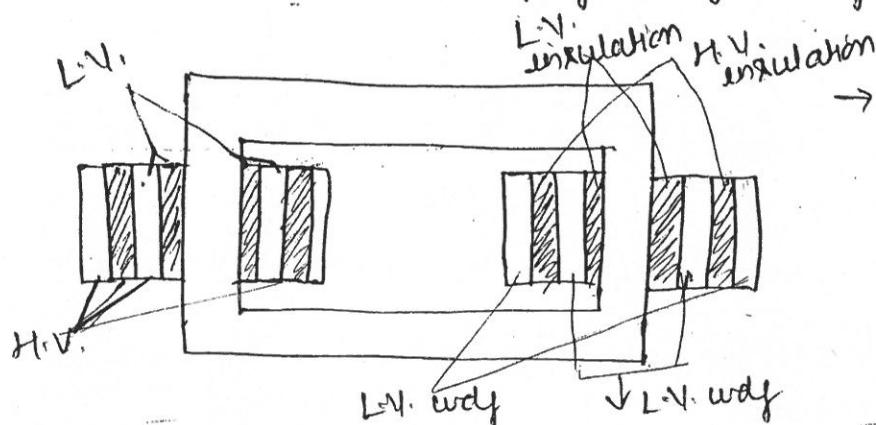- It has single magnetic circuit.
- Magnetic core is rectangular in shape of uniform ~~cross~~ section.
- Both winding are the encircled the both limb as (P) primary & secondary wdg(s).
- Coils are wound the limb in helical layer & coils are cylindrical type.
- Core is made up of large no. of thin laminations.





→ Low voltage coil is placed inside near the core while high voltage coil surrounds the low-voltage coil.

- Edges are uniformly distributed over two limb & natural cooling is more effective.


➤ Shell-type Transformer:-

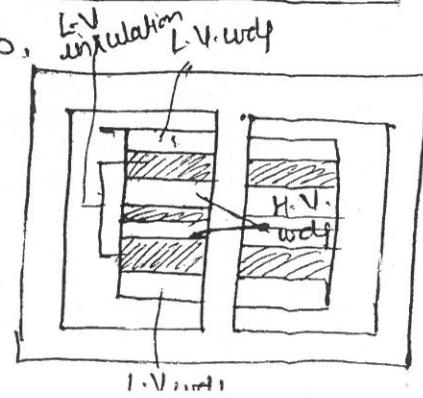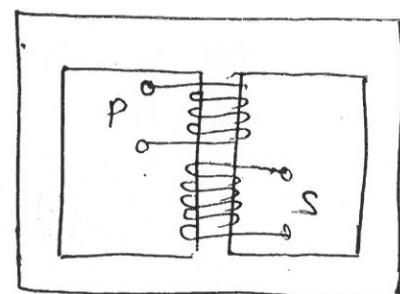- Magnetic circuit are divided into two or more parts.
- Core has three or more limb.
- Both primary & secondary, H.V. & L.V. wdg are placed on central limb.
- L.V. wdg are near to top & bottom of yokes & H.V. wdg are placed b/w L.V. wdg.
- Coils are multilayer dice or sandwich type & wdg are surrounded by core so natural cooling doesn't fails.



➤ Berry-type T/F

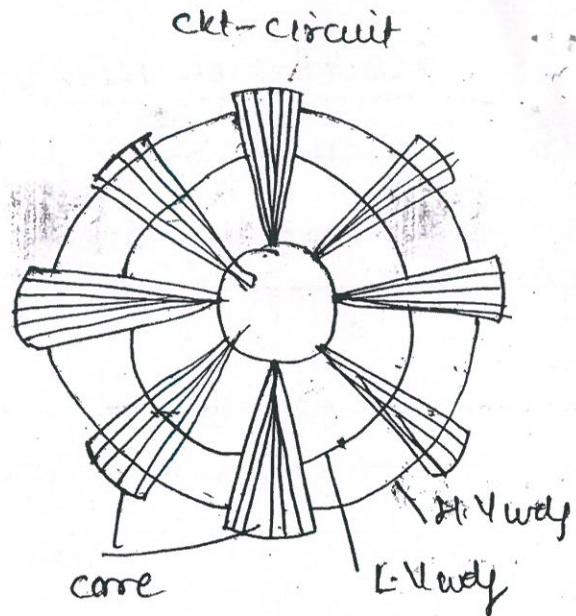- Distributed magnetic ckt
- Core construction is like spokes of a wheel.
- Rugged construction and provide better cooling




⇒ Comparison b/w core-type & shell-type T/F

Core type	Shell-type
① It has only single magnetic ckt.	① It has twice magnetic ckt.
② The core has two limbs.	② The core has three limbs.
③ Both Prim. & Sec. wdg are on different limbs.	③ Both prim. & sec. wdg are placed on central (name) limb.
④ cylindrical coil are used.	④ Multilayer & sandwich type coils are used.
⑤ H.V wdg are ^{surrounds} near the L.V wdg. & L.V.wdg are placed near the core (limb).	⑤ L.V. wdg are surrounds the H.V wdg and L.V. wdg are placed near the yoke
⑥ wdg are uniformly distributed on two diff. limbs than natural cooling is effective. & removed easily for maintenance	⑥ wdg are surrounded by core so natural cooling doesn't exist & coils cannot be removed easily.
⑦ Preferred for Low-voltage transformer	⑦ Preferred for high voltage T/F

3

Working Principle and Emf. equation of TIF

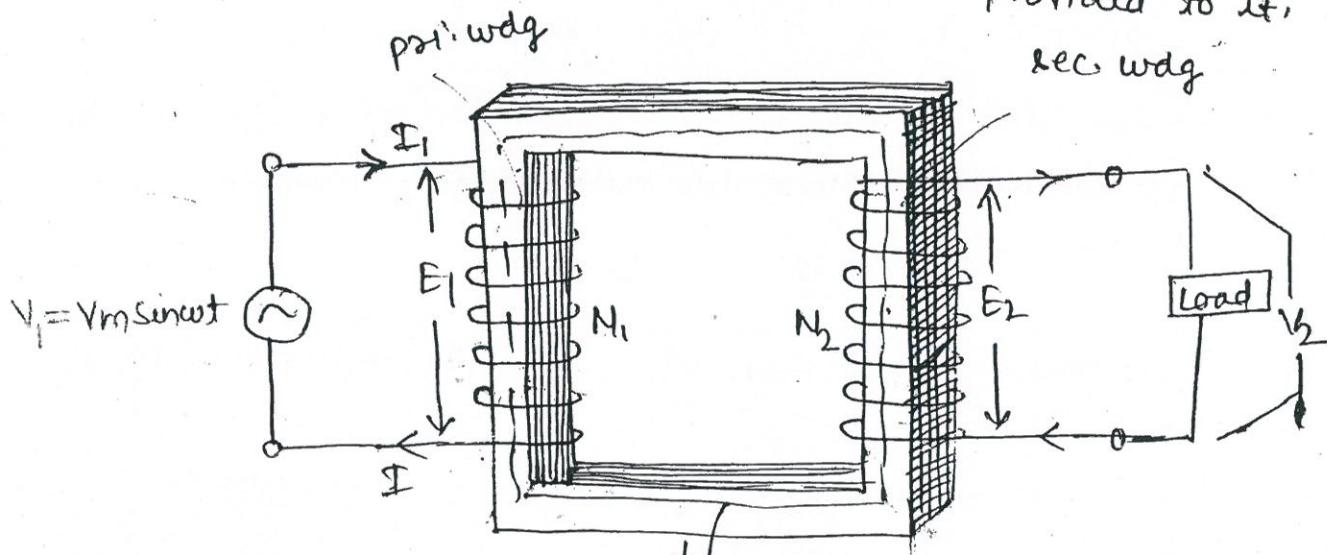- Faraday law of mutual induction ~~with~~ states that when two coils are inductively coupled and if current in one coil is changed uniformly than an emf gets induced in the other coil. This emf can drive a current on sec. wdg when a closed path is provided to it,



- When primary wdg is excited by an alternating voltage, then it circulates an alternating current and produces an alternating flux ϕ which (in common magnetic core) is confined its magnetic path completely via secondary wdg. Thus mag flux which is alternating in nature is linked with secondary wdg.
- As the flux is alternating, according to the Faraday's law of electromagnetic induction, mutually induced emf gets developed in secondary wdg. If now load is connected to the secondary winding, then this emf drives a current through it.
- Thus, there is no electrical contact between two wdg, an electrical energy gets transferred from pri. to secondary.

emf equation \rightarrow

$$V_1 = N_1 \text{ current} \rightarrow \Phi_1 = \text{Flux}$$

\rightarrow An alternating voltage V_1 is confined the primary wdg of N_1 turn ~~thru~~ due to self induction E_1 is developed across pri. wdg.

- \rightarrow The flux established by pri. wdg is linked with sec. wdg through magnetic core & induced mutual emf on sec. wdg which is termed as E_2 across N_2 .
- \rightarrow So, alternating current provided by V_1 establishes alternating flux by alternating mmf ($NI - AT$)

$$\Phi = \Phi_m \sin \omega t$$

$$\rightarrow \text{Then } e_1 = -N_1 \frac{d\Phi}{dt} \quad \& \quad e_2 = -N_2 \frac{d\Phi}{dt}$$

$$e_1 = -N_1 \frac{d}{dt} (\Phi_m \sin \omega t)$$

$$e_2$$


$$= -N_1 \omega \Phi_m \cdot \text{current}$$

$$e_2 = -N_2 \omega \Phi_m \text{ current}$$

$$= -N_1 \omega \Phi_m \sin (\omega t - \pi/2)$$

$$= N_1 2\pi f \Phi_m \sin (\omega t - \pi/2)$$
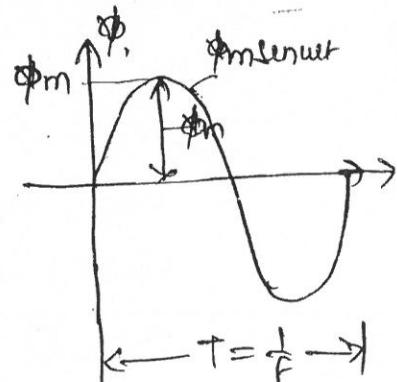
$$e_1 = 2\pi f N_1 \Phi_m \sin (\omega t - \pi/2)$$



$$\begin{aligned} \text{R.M.S value per turn} &= \frac{E_m}{\sqrt{2}} \\ &= \frac{2\pi f \Phi_m}{\sqrt{2}} \\ &= 4.44 f \Phi_m \end{aligned}$$

R.m.s value of primary side
Similarly

$$\boxed{\begin{aligned} E_1 &= 4.44 f \Phi_m N_1 \text{ volts} \\ E_2 &= 4.44 f \Phi_m N_2 \text{ volts} \end{aligned}}$$

→ Voltage Ratio & current Ratio of TIF

$$E_1 = 4.44 f \Phi_m N_1, \quad E_2 = 4.44 f \Phi_m N_2$$

$$\frac{E_1}{E_2} = \frac{N_1 4.44 f \Phi_m}{N_2 4.44 f \Phi_m} \Rightarrow \boxed{\frac{E_1}{E_2} = \frac{N_1}{N_2}}$$

but $\boxed{\frac{E_2}{E_1} = \frac{N_2}{N_1} = K}$ = voltage Transformation Ratio
or turn Ratio

~~$E_2 \propto N_2$~~ $V_2 \propto E_2$ & $N_1 \propto E_1$

then $\boxed{\frac{V_2}{V_1} = \frac{E_2}{E_1} = K}$ → only for Ideal TIF.

Now Ideal TIF has following properties

$\begin{cases} \text{Voltage regulation} = 0 \\ n = 100\% \end{cases}$

- No winding resistance → No winding losses.
- No leakage flux → same flux links with both the windings.
- No iron losses - Eddy current & hysteresis losses in the core.
- High permeability - negligible current is required to establish the flux in it.

∴ Current Ratio in ideal case

$$\text{Input VA} = V_1 I_1 \quad \text{output VA} = V_2 I_2$$

for Ideal TIF $\boxed{\text{Input VA} = \text{output VA}}$

$$V_1 I_1 = V_2 I_2$$

$$\boxed{\frac{V_2}{V_1} = \frac{I_1}{I_2} = K}$$

$$\rightarrow \text{Types of TLF based on } K = K = \frac{V_2}{V_1} = \frac{E_2}{E_1} = \frac{N_2}{N_1}$$

① If $N_2 \geq N_1$ i.e. $K \geq 1$ then

$E_2 \geq E_1 \rightarrow$ step-up transformer

② If $N_1 > N_2$ for $K < 1$ then

$E_1 > E_2 \rightarrow$ step-down transformer

③ $N_1 = N_2$ then $K = 1$

$E_1 = E_2 \rightarrow$ isolation TLF of 1:1

\rightarrow Rating of TLF \rightarrow (VA, kVA, MVA)

Rating of TLF = $V_1 \times I_1$ (VA) input VA

or $V_2 \times I_2$ (VA) output VA

$$\Phi_1 = \frac{VA}{V_1}$$

$$\Phi_2 = \frac{VA}{V_2}$$

Nameplate Rating

4400/440V, 10 kVA, 50Hz
 \uparrow \uparrow \uparrow
 V_1 V_2 KVA rating
 P: voltage S: voltage


VA \rightarrow apparent power [$P + jQ$] Active & Reactive power

\rightarrow Actually output of transformer supply is depends upon the load and load P.f.

\rightarrow Then manufacturer doesn't known about the nature of load at manufacturing time, & load can be changed then output of TLF is also changed. Hence the max. power supplying capacity is given as rating.

Ideal Transformer on No load:-

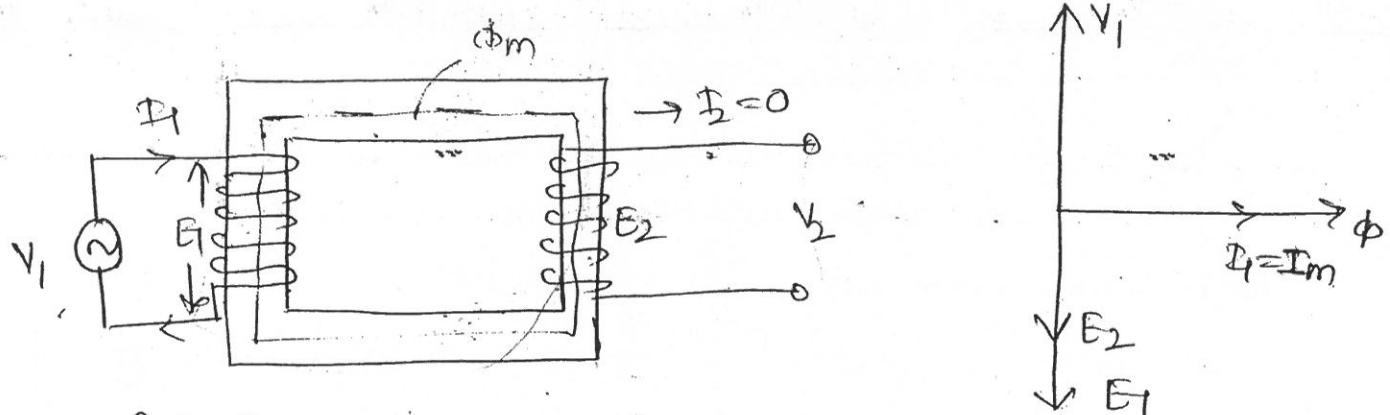No load means secondary has no power loss i.e. sec. is open circuited, $R_L = \infty$



- Actually, primary current $I_1 \neq 0$ ideally but practically a small current called magnetizing current (very small) is required to magnetize the transformer core.
- Assume primary wdg $R_p = 0$ i.e. purely inductive then V_1 is lead by this I_m and the flux ϕ is in time phase with I_m
- Now flux link both the wdg & producing induced emf E_1 & E_2 in primary & sec. wdg respectively. But A/c to Lenz's law, the induced emf opposes the cause i.e. V_1 . Hence $E_1 \propto -V_1$ & its mag. depends upon N_1 .
- E_2 also oppose V_1 & its magnitude depends upon N_2 .

$$\begin{aligned}
 \text{No power input to the T/F} &= V_1 I_1 \cos(90^\circ + \Phi) \\
 &= V_1 I_1 \cos(90^\circ) \\
 &= 0
 \end{aligned}$$

- This is because no load output power is 0 for ideal transformer & there are no power loss bcoz input power is 0.

Practical TIR on No load

→ Same losses are included in practical TIR

* Hysteresis loss and eddy current loss

→ Use high grade material as silicon steel to minimize the hysteresis loss

→ To reduce the eddy current loss, stacks of thin laminations are used.

* Some iron loss is also present


* Some copper loss is also considered due to certain resistance occurred (current) in primary wdg.

Then primary current at no load I_0 has two component

→ I_m - purely reactive component → magnetizing component is required to produce the flux. It is also called wattless component.

→ I_c - active component which supplies total losses at no load, called power component, or wattful component or core loss component

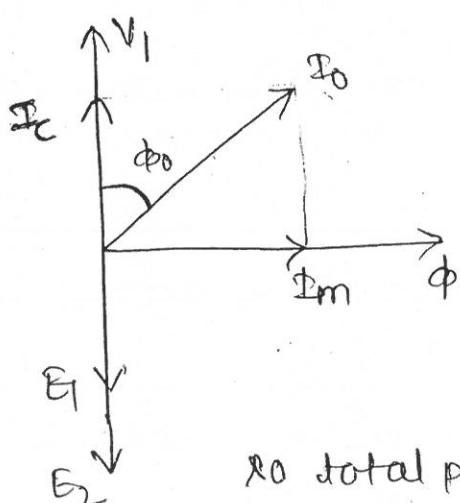∴ I_0 cannot be 90° lag but ~~at~~ leads behind by $\phi_0 < 90^\circ$



$$I_0 = I_m + I_c$$

$$I_m = I_0 \sin \phi_0$$

$$I_c = I_0 \cos \phi_0$$

$$I_0 = \sqrt{I_m^2 + I_c^2}$$

$\cos \phi_0 \rightarrow$ no load p.f.

∴ total power input at no load =

$$P_c = P_w = I_0^2 R = V_1 I_0 \cos \phi_0 = V_1 I_c$$


$$\& \text{ iron loss} = V_1 I_0 \sin \phi_0 = P_e$$

I_0 is very small 3-5% of rated current

Q11 - A 2000/200V, 20kVA transformer has $N_2 = 66$ turns. Calculate the primary current.

(i) N_1 - primary term

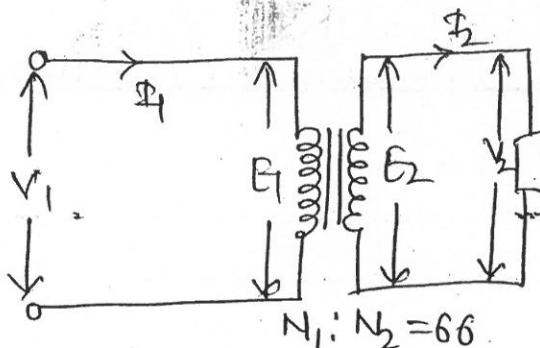(ii) Primary & Secondary full-load ~~voltage~~ Neglect losses.



$$k = \frac{b}{y_1} = \frac{200}{2000} = \frac{1}{10}$$

$$(i) \quad k = \frac{N_2}{N_1} = \frac{N_2}{N_1} \Rightarrow \frac{1}{10} = \frac{N_2}{N_1} \Rightarrow N_1 = 10 \times N_2 = 10 \times 66 = 660 \text{ turns.}$$

$$(ii) \quad V_1 I_1 = V_2 I_2 = 20 \times 10^3 \text{ VA} \quad \text{at neglect losses}$$

$$\begin{aligned}
 I_1 &= \frac{20 \times 10^3}{V_1} & & I_2 = \frac{20 \times 10^3}{V_2} \\
 &= \frac{20 \times 10^3}{2000} & & I_2 = \frac{20 \times 10^3}{200} \\
 &= 10 \text{ Amp} & & = 100 \text{ amp}
 \end{aligned}$$

Q12)- A single phase ~~2000~~ 2200/250 V, 50 Hz T/f has net core area = 36 cm^2 and max. flux density of 6 kG/m^2 . calculate the no. of turns of primary & sec.

$$\text{Sol}^n \leftarrow \Phi_m = B_m a = 6 \times 3.6 \times 10^{-4} = 0.0216 \text{ wb}$$

$$E_1 = 4.44 f\phi_m N_1 \Rightarrow N_1 = \frac{E_1}{4.44 f\phi_m} = \frac{2200}{4.44(50) \times 0.216} = 459$$

$$E_2 = 4.44 \text{ fdom} N_2 \Rightarrow N_2 = \frac{E_2}{4.44 \text{ fdom}} = 52$$

Qn3:- A $200/50$ V, 50 Hz 1ϕ -TIF is connected to a 200 V, 50 Hz supply with sec. open. $N_1 = 400$ turns

(i) $\Phi_m = ?$ if $N_1 = 400$ turns

(ii) $\Phi_m = ?$ if primary voltage is 200 V, 25 Hz.

Soln:- (i) We know: $E_1 = 4.44 f \Phi_m N_1$

$$\Phi_m = \frac{200}{4.44 \times 50 \times 400} = 2.25 \text{ mWb.}$$

$$(ii) \Phi_m = \frac{E_1}{4.44 f N_1} = \frac{200 \text{ V}}{4.44 \times 25 \times 400} = 4.5 \text{ mWb.}$$

Qn4:- 1ϕ TIF, $N_1 = 350$, $N_2 = 1050$, $a = 85 \text{ cm}^2$.

$E_1 = 400$ V, 50 Hz, calculate

(i) Φ_m in the core (ii) voltage induced at sec. & flux density

Soln:- $N_1 = 350$, $N_2 = 1050$, $E_1 = 400$ V

$$(i) \Phi_m = \frac{E_1}{4.44 f N_1} = \frac{400 \text{ V}}{4.44 \times 50 \times 350} = 5.15 \times 10^{-3}$$

$$\Phi_m = B_m a \Rightarrow B_m = \frac{5.15 \times 10^{-3}}{58 \times 10^{-4}} = 936 \text{ Wb/m}^2$$

$$(ii) k = \frac{E_2}{E_1} = \frac{N_2}{N_1} \quad | \quad E_2 = B_1 \times \frac{N_2}{N_1} = 400 \times \frac{1050}{350} = 1200 \text{ V}$$

Qn5:- 1ϕ TIF $N_1 = 400$, $a = 60 \text{ cm}^2$, $l = 1.8 \text{ m}$, $E_1 = 500$ V, 50 Hz
Find Im -magnetizing current if $u_r = 2000$

Ans:- $N \cdot I_m = \text{mmf} \Rightarrow \text{Im} = \frac{\text{mmf}(\text{AT})}{N_1} \frac{\text{flux} \times \text{reluctance}}{N_1}$

$$\text{Im} = N_1 \times \text{Im} = \Phi_m \times \frac{1}{4\pi \times 10^{-7} \times 2000 \times 60 \times a} = \Phi_m \times \frac{1}{4\pi \times 10^{-7} \times 2000 \times 60 \times 60 \times 10^{-4}}$$

$$E_1 = 4.44 f \Phi_m N_1 \Rightarrow \Phi_m = 5.63 \times 10^{-3} \quad \text{--- (1)}$$

$$N_1 \times \text{Im} = 5.63 \times 10^{-3} \times 5.3 \times 10^5 = 2.987 \times 10^2$$

$$\boxed{\text{Im} = 746}$$

$$(\text{Im})_{\text{real}} = \frac{746}{f_2} = 52.8 \text{ A}$$

Qn: 8 A voltage $v = 200 \sin 314t$ is applied to TIF wdg in a load test, resulting $I = 3 \sin(314t - 60^\circ)$. Determine core loss and no load approx. parameter of equivalent det.

Sol:- $V_1 = \frac{200}{\sqrt{2}}$, $I_0 = \frac{3}{\sqrt{2}}$ $\Rightarrow \phi_0 = 60^\circ$

$$\begin{aligned} P_0 &= V_1 I_0 \cos \phi_0 \\ &= \frac{200}{\sqrt{2}} \times \frac{3}{\sqrt{2}} \cos 60^\circ \\ &= 150 \text{W.} \end{aligned}$$

$$\begin{aligned} \text{Component of core loss} \cdot I_{ew} &= I_0 \cos \phi_0 \\ \Phi_e &= \frac{3}{\sqrt{2}} \cos 60^\circ = 1.061 \end{aligned}$$

$$\begin{aligned} \text{magnetizing current } \Phi_m &= \sqrt{I_0^2 - \Phi_e^2} \\ &= \sqrt{(3/\sqrt{2})^2 - 1.061^2} = 1.837 \end{aligned}$$

$$\begin{aligned} \Rightarrow I_0 &= [I_0 \cos \phi_0 - j I_0 \sin \phi_0] \\ &= [1.061 - j 1.837] \end{aligned}$$

$$\begin{aligned} R &= \frac{V_1}{I_0 \cos \phi} = \frac{200/\sqrt{2}}{1.061} = 133.291 \Omega \\ X &= \frac{V_1}{1.837} = \frac{200/\sqrt{2}}{1.837} = 76.98 \Omega \end{aligned}$$

Qⁿ 6 A transformer takes a current of 6A & absorbs 64W when primary is connected to its normal supply 240V, 50Hz, the sec. being an open circuit. Find the magnetizing and iron loss current.

Solⁿ!- Iron loss component or active component

$$\text{No load p.f. power } I_w = V_1 I_0 \cos \phi_0 = 64W$$

$$I_0 = V_1 I_0 \cos \phi_0 \quad \text{& Iron loss component}$$

$$I_0 = V_1 I_w \quad I_w = \Phi_0 \cos \phi_0 = I_c$$

$$I_w = \frac{64}{240} = 0.267 \text{ amp}$$

$$\text{& } \Phi_0 = 0.6 \quad \text{then } I_0 = \sqrt{I_m^2 + I_w^2}$$

$$I_m = \sqrt{I_0^2 - I_w^2} = \sqrt{(0.6)^2 - (0.267)^2} = 0.5375$$

Qⁿ 7!- A 230V / 2300V T/F takes no load current of 6.5A and absorbs 187W. If resistance is 0.6Ω. Find
 (i) Core loss (ii) no load p.f (iii) Active component of current (iv) magnetizing current

Solⁿ!- ~~$I_0 = V_1 I_0 \cos \phi_0$~~

$$(ii) \cos \phi_0 = \frac{187W}{230 \times 6.5} = 0.125 \text{ lagging}$$

$$(iii) \text{ active component of current } I_w = I_0 \cos \phi_0 \\ = 6.5 \times 0.125 = 0.813A$$

$$(iv) I_0^2 = \sqrt{I_m^2 + I_w^2} \Rightarrow I_m^2 = \sqrt{I_0^2 - I_w^2}$$

$$I_m = \sqrt{(6.5)^2 - (0.813)^2} = 6.4W$$

$$(i) \cancel{I_0 = V_1 I_0 \sin \phi_0} \text{ Primary cu loss} = I_0^2 R_1 = (6.5)^2 \times 0.6 \\ = 2.535W$$

$$\text{Core loss} = \text{Iron loss} = 187 - 2.5 = 184.5W$$

→ NO load equivalent circuit


P_W - active component
Supply core losses.

core losses



↳ Hysteresis &
Eddy current losses.

$I_m \rightarrow X_0$ - wattless component

use for magnetizing the core.

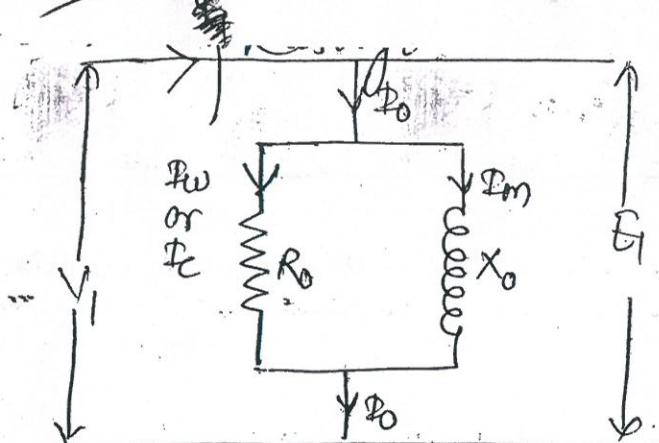

Ideal T/P on Load:-

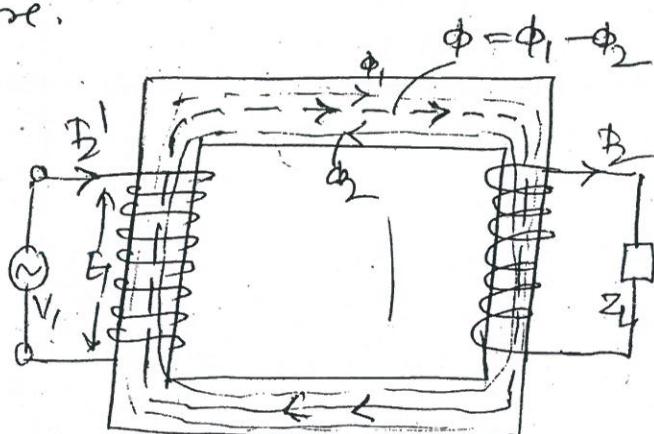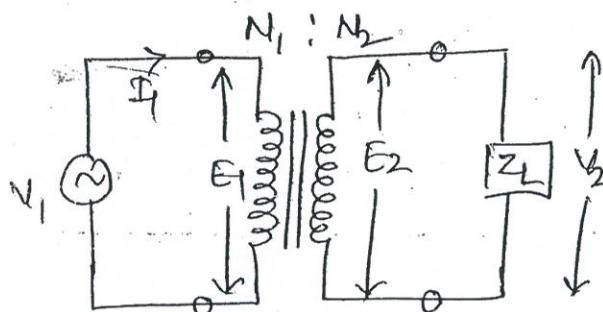

(L type)

- * When a certain load $Z_L = R_L + jX_L$ is connected to the sec. windg. of T/P, a finite I_2 current starts flowing. & due to inductive load I_2 lags behind by 90° by ϕ_2 angle
- * As per lenz's law, the I_2 current will oppose the cause of producing it. Hence it oppose the flux set-up in magnetic core. This is demagnetizing effect of I_2 , and this effect flux weakened the primary wdg setup flux & hence reduced the emf induced at E_1 . Hence vector difference $V_1 - E_1$ increases and corresponding draws more current from current, this additional current drawn due to load, hence it is shown by I_1'
- * Now B' will set up the flux ϕ_2' which help the ϕ_1 but oppose the $\phi_2 \sim B$. Hence I_1' is in antiphase I_2 . Now mmf produced by such change is $N_1 B'$ balance the $N_2 B$ and net flux in the core is again maintained. i.e. Transformer is constant flux machine.


$$N_1 I_2^1 = N_2 I_2$$

$$I_2^1 = \frac{N_2}{N_1} I_2 = K I_2 \quad \& \quad I_2^1 \text{ is } 180^\circ \text{ out of phase with } I_2$$

so net primary current

$$\bar{I}_1 = \bar{I}_2^1 + \bar{I}_m$$

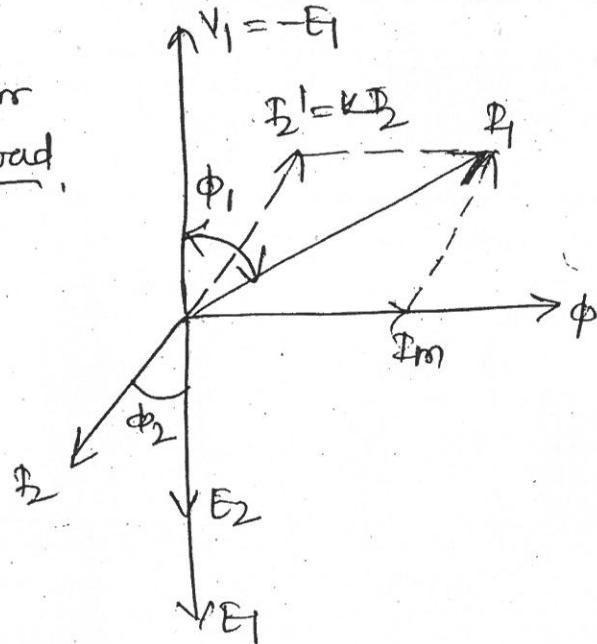Ideal
Transformer phasor
diagram at on load



Numerical :- A 400/200 V T/F takes 1Amp current at p.f=4 on no load if secondary supply a load current 80A at 18 lagging

Practical T/F on Load

S2



Load classification	Load current
Purely Resistive (R)	I_2 in same phase
(R+L) type	I_2 leads with E_2
(R+C) type	I_2 lags with E_2


→ As T/F is loaded, I_2 will start flowing. As load increase, I_2 increases & hence mmf (Amp-turn, NI) $N_2 B_2$ will also increase, and hence flux ~~will~~, setup by $N_2 B_2$, ϕ_2 increases & oppose the main flux ϕ_1 .

→ Now we know that if load is inductive, this I_2 is lag behind E_2 . & due to load current increase ϕ_2 oppose ϕ_1 , & $\bar{V}_1 - \bar{E}_1$ difference increase the additional current flow which is $\bar{I}' = \bar{I}_2' + \bar{I}_0$

Here ~~as~~ $N_2 B_2 = N_1 B_2'$ & $\bar{I}_0 = \bar{I}_m + \bar{I}_w$
 $B_2' = \frac{N_2}{N_1} B_2 = K B_2$ or \bar{I}

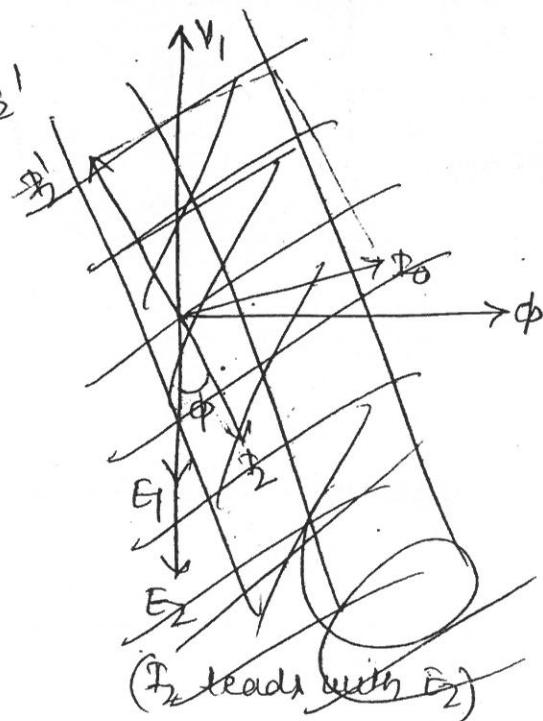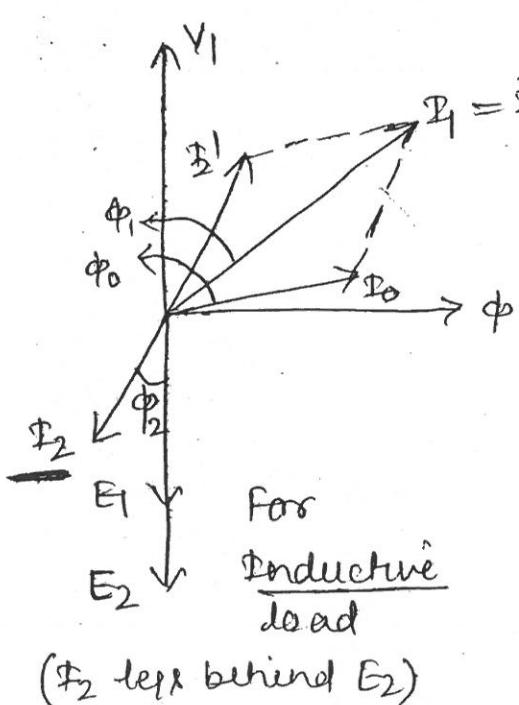
→ Here I_0 is not adjust 90° lags with E_1 but make same angle ϕ_0 due to inductive coil N_1 (per cycle).



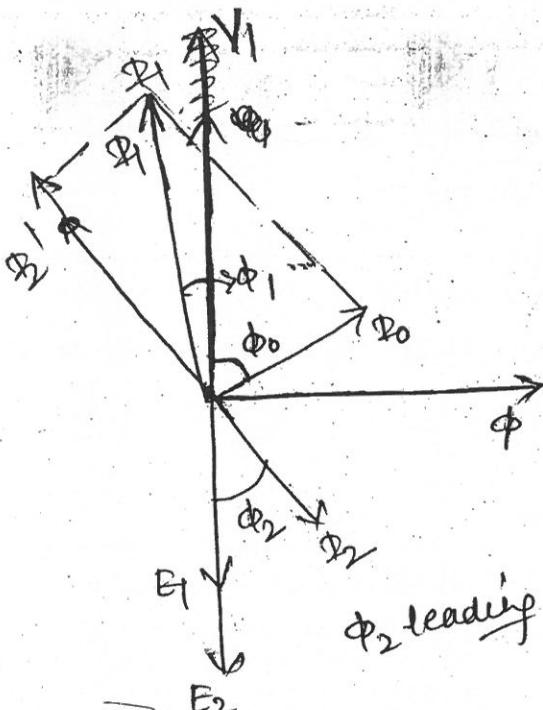

For capacitive load

(Φ_2 leads with E_2)

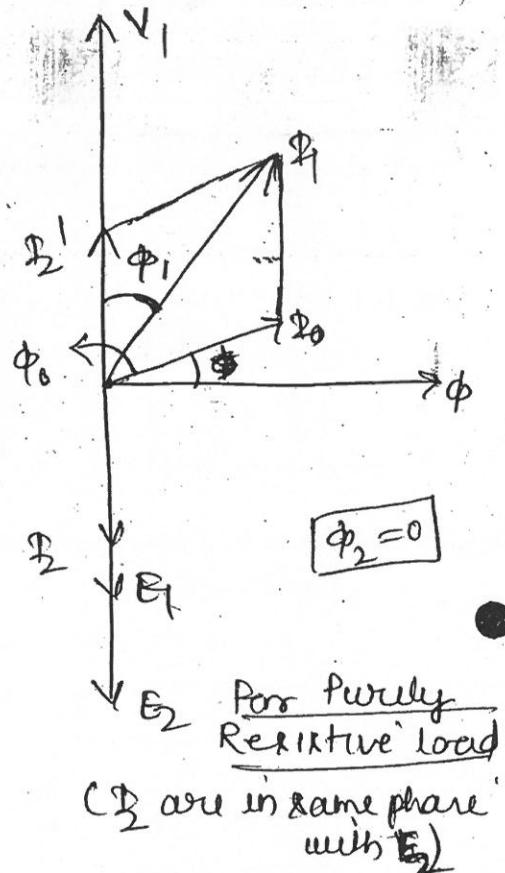

Qn:- A 400/200 V T/F takes 1A at a power factor of .4 on no load if the secondary supplies a load current of 50A at .8 lagging p.f. calculate primary current.

Soln:- $I_0 = 1A$ at $\cos \phi_0 = .4$, $I_2 = 50A$ at $\cos \phi_2 = .8$ lagging
 $\phi_0 = 66.42^\circ$ $\phi_2 = 36.86^\circ$

$$\Phi_0 = I_0 \cos \phi_0 + j I_0 \sin \phi_0$$


$$K = \frac{\Phi_2}{E_1} = \frac{200}{400} = .5 \quad \& \quad \Phi_2' = K \Phi_2 \\ = .5 \times 50 \\ = 25A$$

$$\cancel{(\phi_0 - \phi_2)} = 29.56$$

$$\therefore \Phi_1^2 = \Phi_0^2 + \Phi_2'^2 + 2 I_0 I_2' \cos(\phi_0 - \phi_2)$$

$$\Phi_1^2 = 1 + 625 + 43.5$$

$$\boxed{\Phi_1 = 25.87}$$

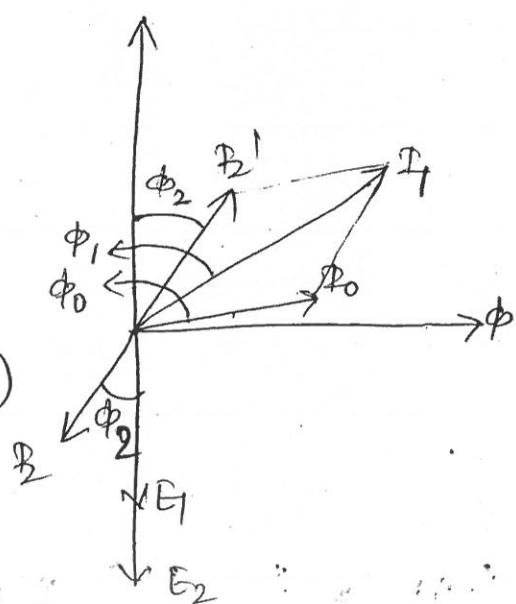

Circuit Impedance

① Equivalent resistance & ~~Reactance~~ & Reactance

Voltage drop of primary wdg = $\Phi_1 R_1$

Voltage drop of secondary wdg = $\Phi_2 R_2$

Total copper loss = $\Phi^2 R$

$$k = \frac{V_2}{V_1} = \frac{\Phi_2}{\Phi_1}$$

$$= \Phi_1^2 R_1 + \Phi_2^2 R_2$$

$$= \Phi_1^2 \left[R_1 + \left(\frac{\Phi_2}{\Phi_1} \right)^2 R_2 \right]$$

$$= \Phi_1^2 \left[R_1 + \left(\frac{R_2}{k^2} \right) \right] = \Phi_1^2 [R_1 + R_2']$$



$$= \Phi_1^2 R_{1e}$$

$R_{1e} \rightarrow$ total resistance referred to primary side

$$R_{1e} = R_1 + R_2'$$

$$\text{where } R_2' = \frac{R_2}{k^2}$$

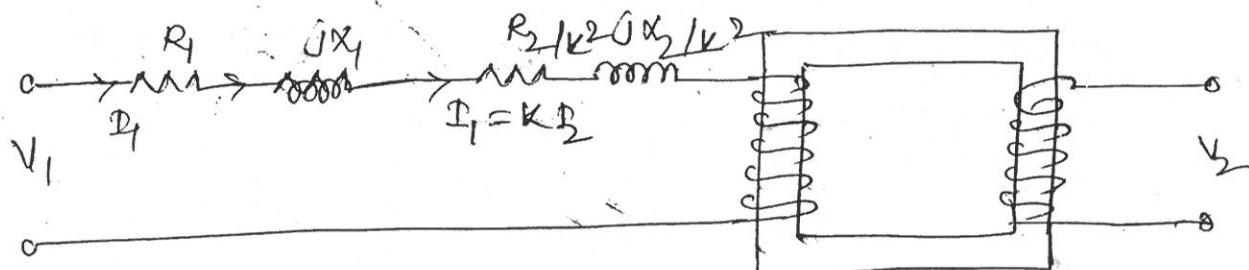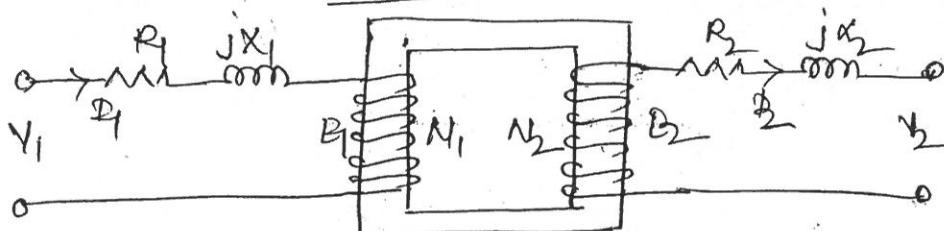Similarly $X_{1e} = X_1 + X_2'$ where $X_2' = \frac{X_2}{k^2}$



Refer to secondary side

$$K = \frac{\psi_2}{\psi_1} = \frac{\Phi_1}{\Phi_2}$$

$$\text{Total copper loss} = \Phi_1^2 R_1 + \Phi_2^2 R_2$$

$$= \Phi_1^2 \left[\left(\frac{\Phi_1}{\Phi_2} \right)^2 R_1 + R_2 \right]$$



$$= \Phi_1^2 \left[K^2 R_1 + R_2 \right]$$

$$= \Phi_1^2 \left[R_2 + R_1' \right] = \Phi_1^2 R_{2e}$$

$R_{2e} \rightarrow$ total resistance referred to sec side


$$R_{2e} = R_2 + R_1' \quad \text{where } R_1' = K^2 R_1$$

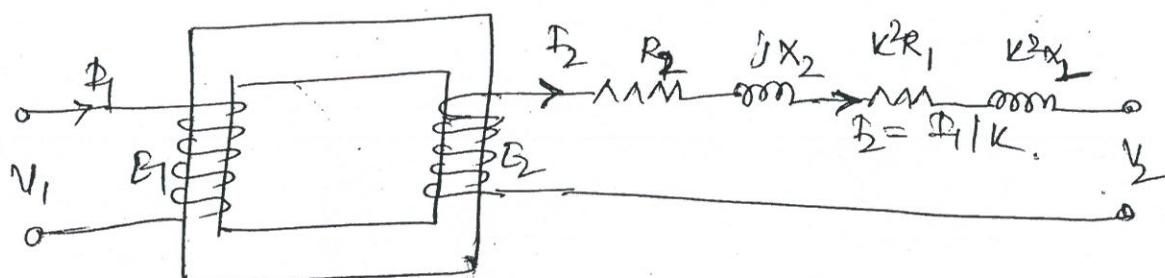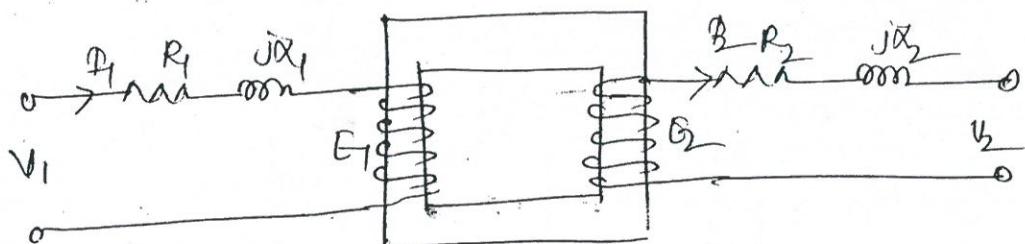similarly reactance $X_{2e} = X_2 + X_1'$ where $X_1' = K^2 X_1$



Equivalent circuit of a TTFI

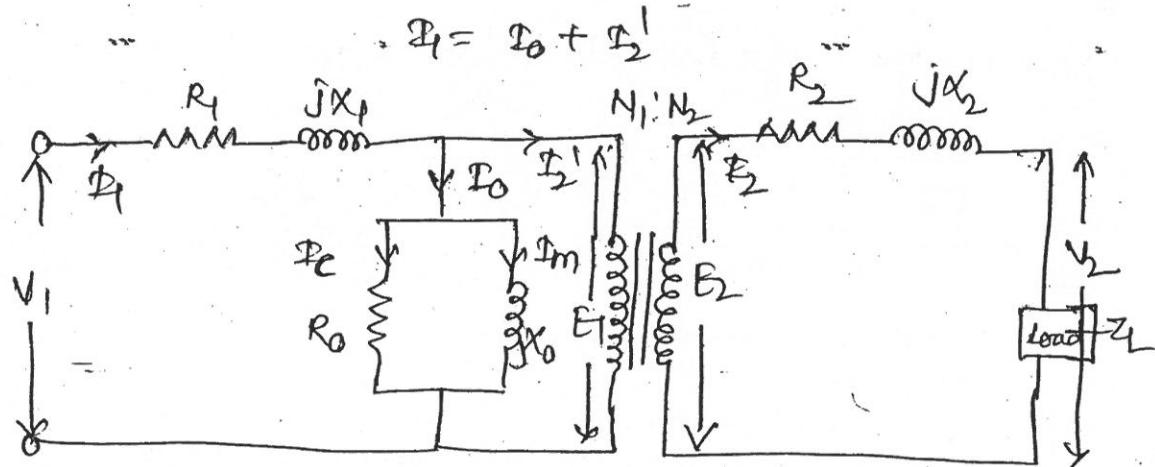
- ① No load primary current I_0
- ② Anticipating or addition current I_2'




Now we referred our parameter

$$\frac{E_2}{E_1} = k$$

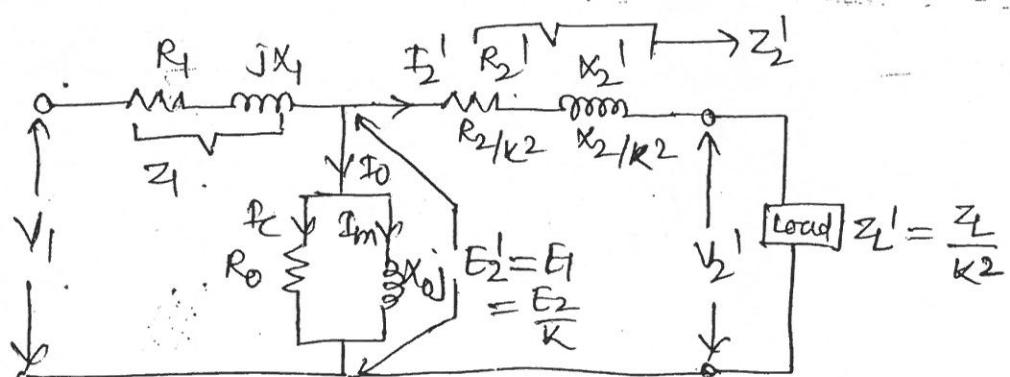- a) Exact Equivalent ckt referred to primary side.
- b) Exact Equivalent ckt referred to sec. side




a) E.E.C. referred to primary side

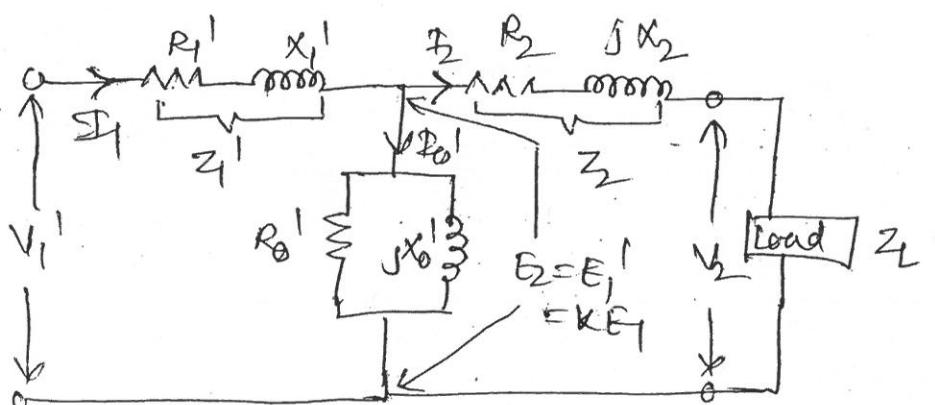


b) Exact Equivalent ckt referred to sec. side

Approximate equivalent circuit:-

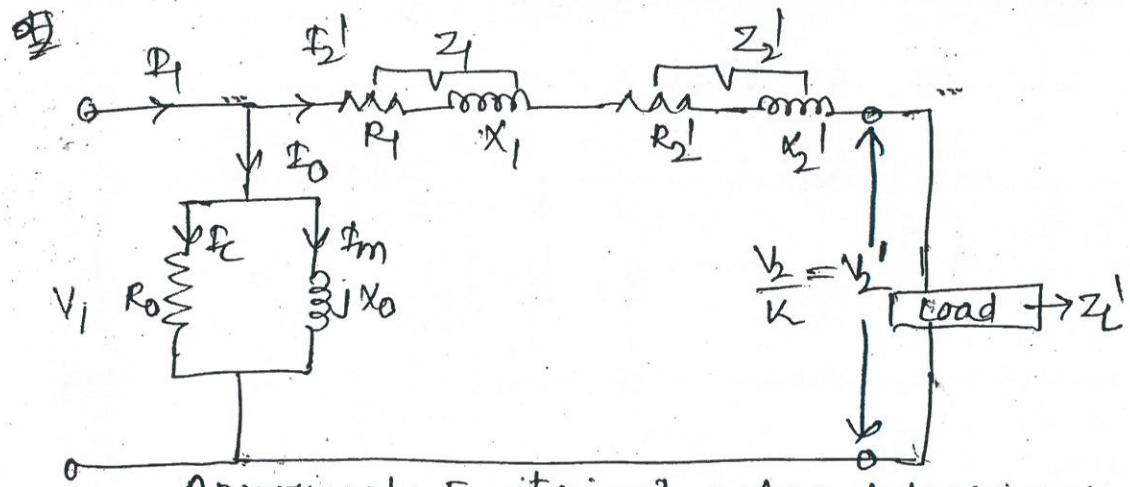
a) Shift No load primary current to the left of Z_1



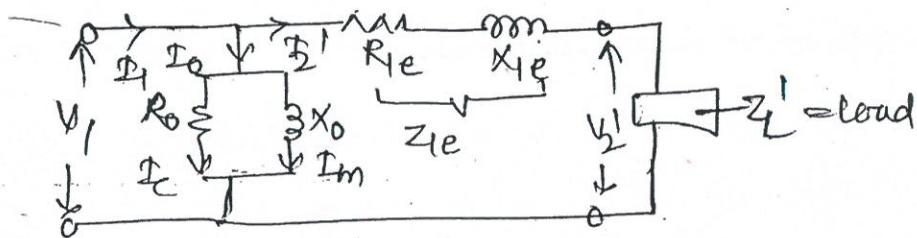Approximate Equi. circuit referred to per. side



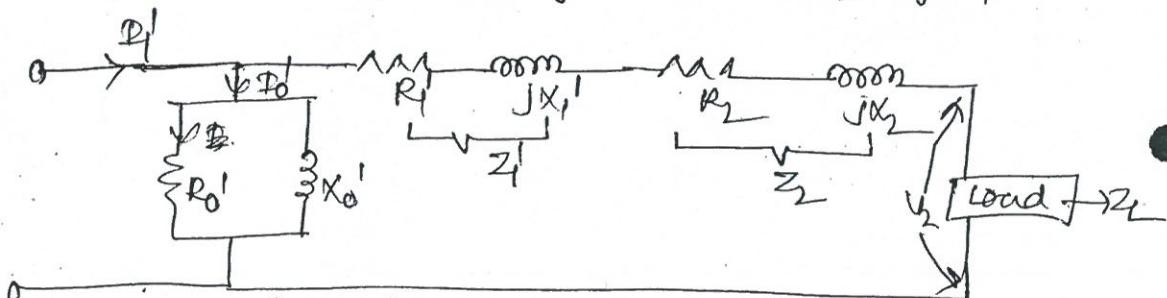
d) Shift No load primary to the left of z_1'




Approximate equivalent circuit referred to terminals

$$R_{2e} = R_3 + R_4^{-1}$$

$$x_{2e} = x_2 + x_1$$

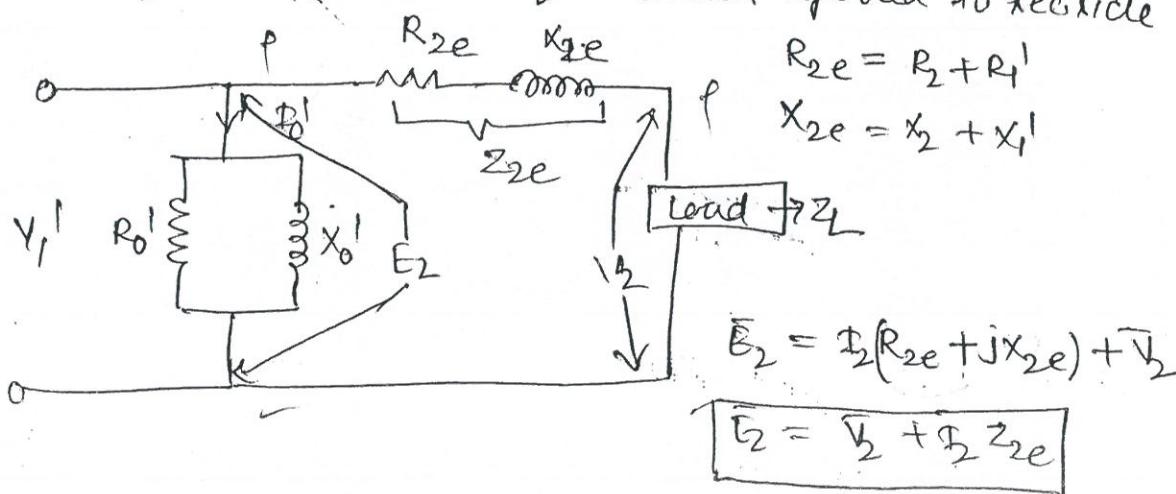


4th term: leading p.f. :-

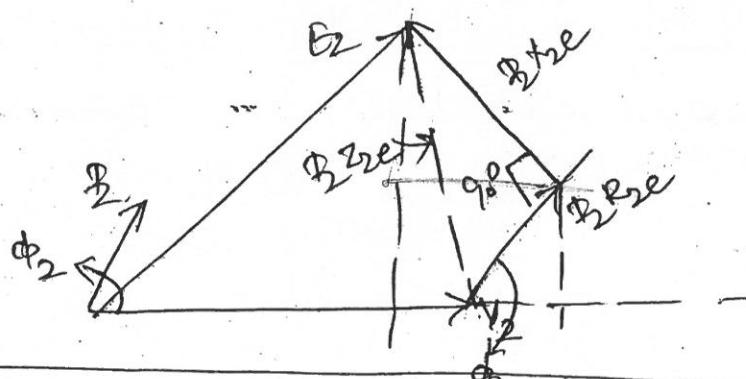

Approximate voltage drop = $I_2 R_{2e} \cos \phi_2 - I_2 X_{2e} \sin \phi_2$ referred to rec.

= $I_2 R_{2e} \cos \phi_2 - I_2 X_{2e} \sin \phi_2$ referred to pri.

3rd term: poor unity p.f. :-

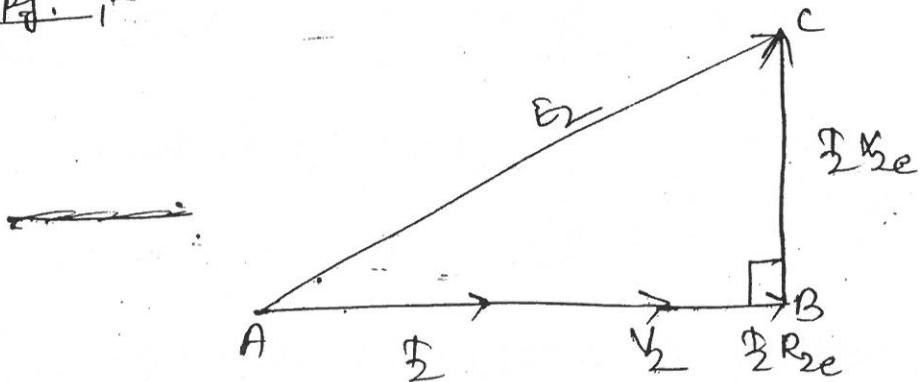

So, Approximate voltage drop = $E_2 - E_{2e} = I_2 R_{2e}$ referred to rec.

= $I_2 R_{2e}$ referred to pri.

General formula for
approx. voltage drop

$$I_2 R_{2e} \cos \phi_2 \pm I_2 X_{2e} \cos \phi_2$$

$$I_2 R_{2e} \cos \phi_2 \pm I_2 X_{2e} \sin \phi_2$$

→ sign for lagging p.f., → sign for leading p.f.


Approximate equivalent phasor diagram

① for
legging pf. $E_2 = V_2 + I_2(R_{2e} + jX_{2e})$

When there is no load ...

$I_2 = 0$ then $E_2 = V_{20}$

= No load
ter. voltage

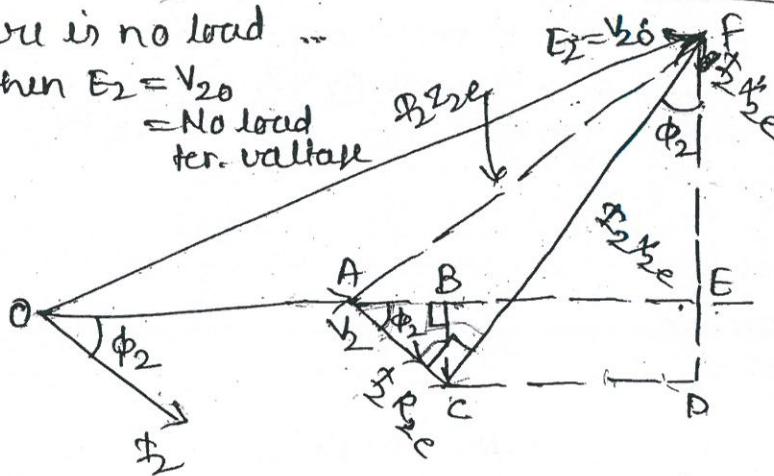

Approximate voltage drop = $\bar{AE} = \bar{AB} + \bar{BE}$ ①

For \bar{AB} , ΔABC : $\cos\phi_2 = \frac{\bar{AB}}{\bar{I}_2 R_{2e}} \Rightarrow \bar{AB} = \bar{I}_2 R_{2e} \cos\phi_2$

For \bar{BE} , ΔCFD : $\cos\phi_2 = \sin\phi_2 = \frac{CD \text{ or } BE}{\bar{I}_2 X_{2e}}$

$\bar{BE} = \bar{I}_2 X_{2e} \sin\phi_2$

so from eqn ① $\bar{AE} = \bar{I}_2 R_{2e} \cos\phi_2 + \bar{I}_2 X_{2e} \sin\phi_2$

Let $\phi_2 = \phi$ (Approx.) $\Rightarrow \bar{AE} = \bar{I}_2 R_{2e} \cos\phi + \bar{I}_2 X_{2e} \sin\phi$

If parameters are

referred to primary side then analogously

Approximate voltage drop = $\bar{A}_1 R_{1e} \cos\phi + \bar{D}_1 X_{1e} \sin\phi$

Voltage Regulation :-

Resistance and leakage Resistance

$$\% \text{ voltage Regulation} = \frac{E_2 - V_2}{V_2} \times 100$$

where $\frac{E_2 - V_2}{V_2}$ is called per unit regulation.

- * Actually, due to presence of pri. & sec. impedance, the sec. terminal voltage drop from its no-load value (E_2) to the load value V_2 .
- * As load current increased, the voltage drops tend to increase means V_2 drops more. This voltage drop should be ~~as much less as~~ as small as possible. Hence less the regulation better is the performance.
- * In case of lagging power factor $E_2 > V_2$ & we get fine voltage regulation, while for leading power factor $E_2 < V_2$ we get negative voltage regulation.
- * Here, sec. terminal voltage also depends upon the nature of the power factor of the load.

$$\% R = \frac{E_2 - V_2}{V_2} \times 100 = \frac{\text{Total voltage drop}}{V_2} \times 100$$

We already derived the approx. voltage drop.

$$\% R = \frac{I_2 R_{2e} \cos \phi \pm I_2 X_{2e} \sin \phi}{V_2} \times 100 \rightarrow \text{Ref. to sec. side}$$

$$\text{or } \frac{I_1 R_{1e} \cos \phi \pm I_1 X_{1e} \sin \phi}{V_1} \times 100 \rightarrow \text{Ref. to pri. side}$$

+ve sign for lagging power factor.

-ve sign for leading power factor.

Zero Voltage Regulation:-

equivalent diagram of $\frac{E_2}{V_2}$

Actually for lagging p.f & unity p.f $V_2 < E_2$ & we get $+ R\%$

But as load becomes capacitive, V_2 starts increasing then there must be a point $E_2 - V_2 = 0$, at this point the regulation becomes zero & $\% R = 0$

$$i.e. \Rightarrow E_2 = V_2$$

$$\Rightarrow E_2 - V_2 = 0 \Rightarrow \text{voltage drop} = 0$$

$$\Rightarrow I_1 R_{2e} \cos \phi - I_1 X_{2e} \sin \phi = 0$$

$$\Rightarrow V_R \cos \phi - V_x \sin \phi = 0$$

$$\Rightarrow \tan \phi = \frac{V_R}{V_x}$$

$$\Rightarrow \boxed{\cos \phi = \cos \left[\tan^{-1} \left(\frac{V_R}{V_x} \right) \right]}$$

This is leading p.f at which voltage regulation becomes zero while supplying the load.

Sol For 250/125V, 5 KVA, 1Ø TIF has $R_1 = 0.2 \Omega$, $X_1 = 0.75$
 $R_2 = 0.5 \Omega$, $X_2 = 1.2 \Omega$

(i) Determine its regulation while supplying full load on 1.8 leading p.f.

(ii) The secondary terminal voltage on full load & 1.8 leading p.f.

$$\text{Sol} \quad K = \frac{125}{250} = 0.5 \quad I_2 (\text{FL}) = \frac{5 \times 10^3}{125} \text{ A} = 40 \text{ A}$$

$$R_{2e} = R_2 + K^2 R_1 \\ = 0.5 + 0.25 \times 0.2 = 0.15 \Omega$$

$$X_{2e} = X_2 + K^2 X_1 \\ = 0.2 + (0.5)^2 \times 0.75 = 0.3875 \Omega$$

(i) $\cos \phi = 1.8$ leading $\sin \phi = 0.6$

$$\% R = \frac{I_2 R_{2e} \cos \phi - I_2 X_{2e} \sin \phi}{V_2} = \frac{40 \left[0.15 \times 1.8 - 0.3875 \times 0.6 \right]}{125} \\ = -4.88\%$$

(ii)

$$\% R = \frac{E_2 - V_2}{V_2} \times 100 \Rightarrow -4.88 = \frac{125 - V_2}{V_2} \times 100$$

$$V_2 = ?$$

$$E_2 \neq V_2$$

$R_2 = 0.015 \Omega$ & $X_2 = 0.02 \Omega$ respectively. The no load current of T/F is 10A at 0.2 pf. Determine

- Equivalent Resistance, Reactance & Impedance referred to pri.
- Supply current (ii) Total copper loss.

Soln:- $K = \frac{V_2}{V_1} = \frac{200V}{2000V} = 0.1$

(i) $R_{1e} = R_1 + R_2' = R_1 + \frac{R_2}{K^2} = 1.5 + \frac{0.015}{(0.1)^2} = 3 \Omega$

$X_{1e} = X_1 + X_2' = 2 + \frac{0.02}{(0.1)^2} = 4 \Omega$

Answer

$Z_{1e} = R_{1e} + jX_{1e} = 3 + j4 \Rightarrow |Z_{1e}| = \sqrt{3^2 + 4^2} = 5 \Omega$

(ii) Supply current $I_{1e} = \frac{KVA (V_1, \Phi_1)}{V_1} = \frac{20 \times 10^3}{2000} = 10A$

on loaded T/F. $I_1 = \frac{V_1}{Z_1} = \frac{2000}{5} = 400A$


(iii) Total cu. loss

$$P_{cu\text{ (loss)}} = I_1^2 R_{1e} = (400)^2 \times 3 = 480 \text{ kW}$$


$$Z_0 = \frac{V_1}{I_1} = \frac{2000}{1} = 2000 \Omega \quad \cos \phi_0 = 0.2$$

$$Z_0 = 2000 \Omega \quad R_0 = Z_0 \cos \phi_0 = 2000 \times 0.2 = 400 \Omega$$

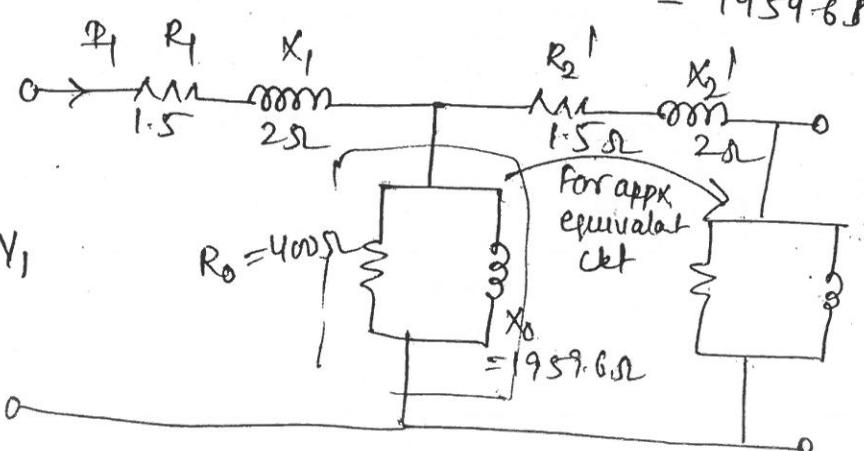
$$X_0 = Z_0 \sin \phi_0 = 2000 \times \sin(78.46^\circ) = 1959.6 \Omega$$




(Actual transformer on load)

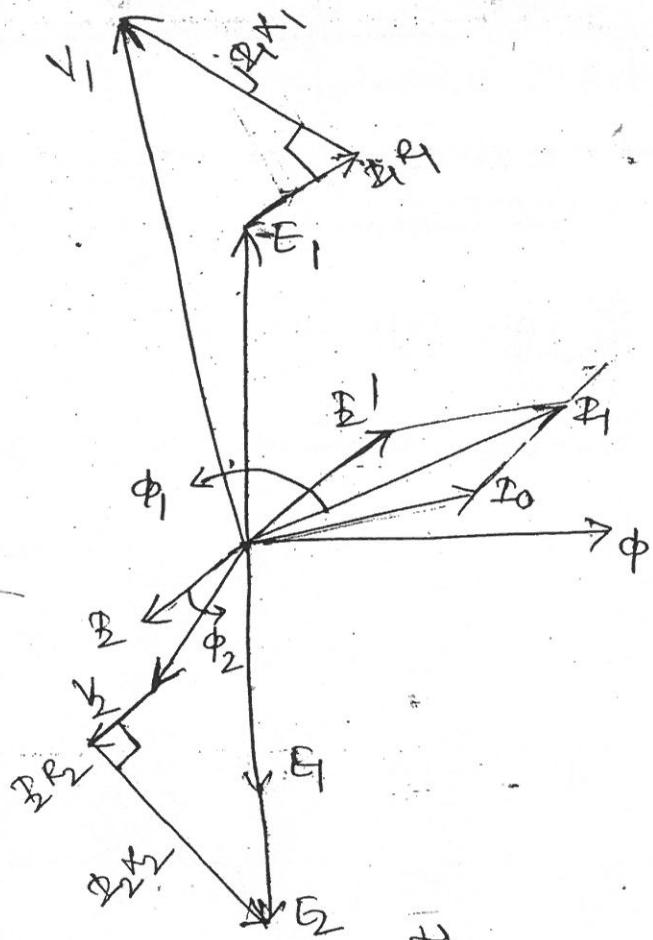

Phasor diagram at leading power factor:-

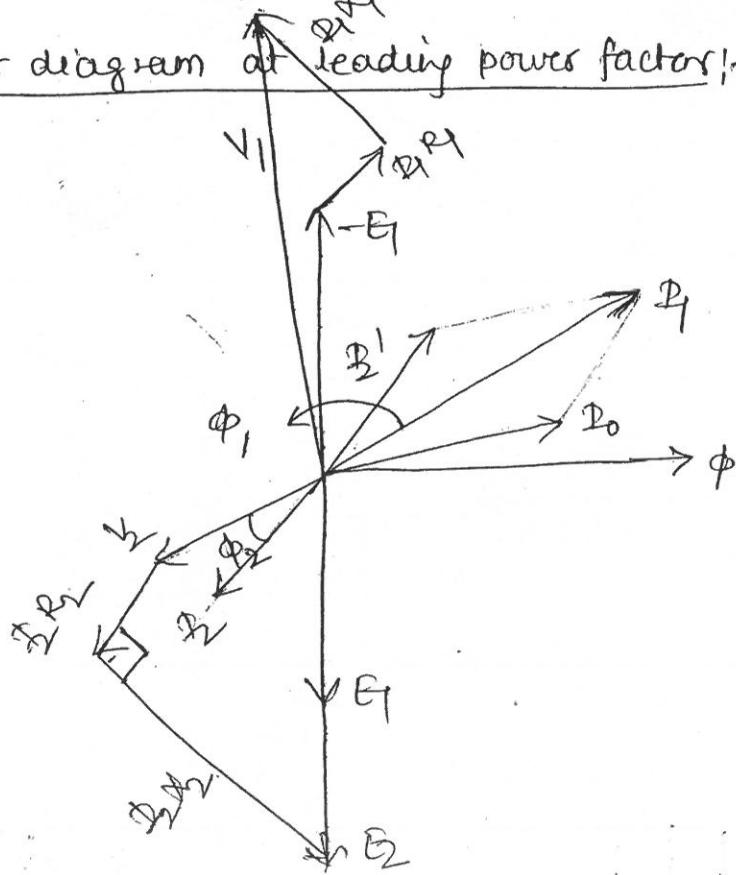


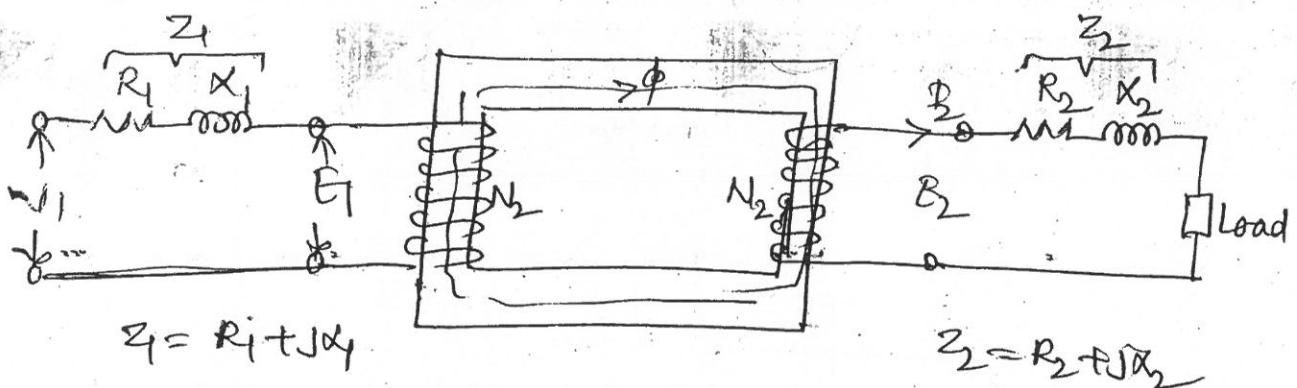

Phasor diagram on different load with leakage R & X

① Inductive load Purely Resistive load i.e. $\phi_2 = 0$

For Unity Power factor

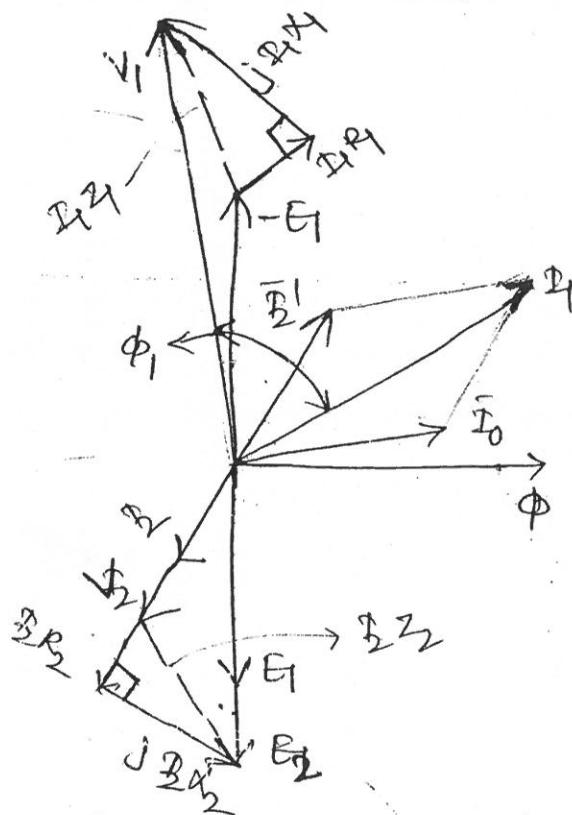


$$V_1 = -E_1 + I_1(R_1 + jX_1)$$

$$V_2 = E_2 + I_2(R_2 + jX_2)$$

Resistance & leakage Reactance

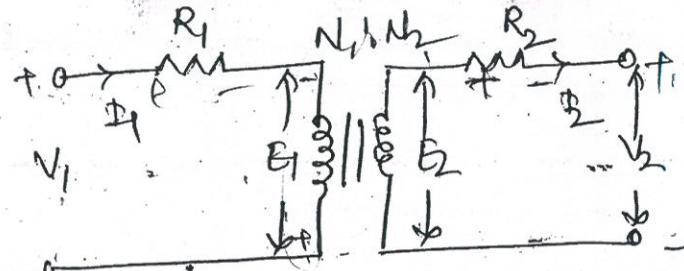- * In actual, both primary and secondary wdg have certain resistances R_1 & R_2 which causes copper losses and voltage drop.



we already know $E_1 \propto -V_1$ [Lenz's Law]

KVL at primary side

$$V_1 + E_1 - I_1 R_1 = 0$$


$$E_1 = V_1 - I_1 R_1$$

KVL at secondary side

$$E_2 - V_2 - I_2 R_2 = 0$$

$$V_2 = E_2 - I_2 R_2$$

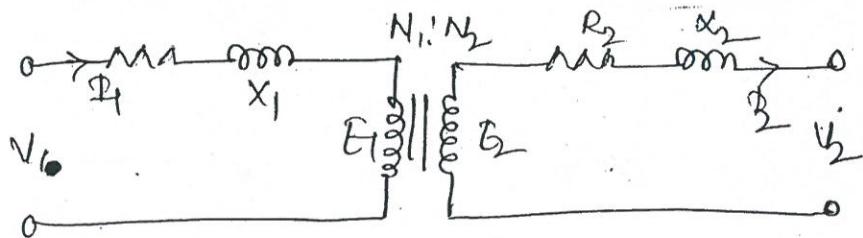- * Similarly, both primary and secondary wdg also have same leakage reactance X_1 & X_2 respectively which produces same flux leak out in both pri. & sec. wdg.



KVL at primary side

$$V_1 + E_1 - I_1 R_1 - j I_1 X_1 = 0$$

$$V_1 = -E_1 + I_1 Z_1$$


$$\text{where } Z_1 = R_1 + j X_1$$

KVL at sec side

$$E_2 - V_2 - I_2 R_2 - j I_2 X_2 = 0$$

$$V_2 = E_2 - I_2 Z_2$$

$$\text{where } Z_2 = R_2 + j X_2$$

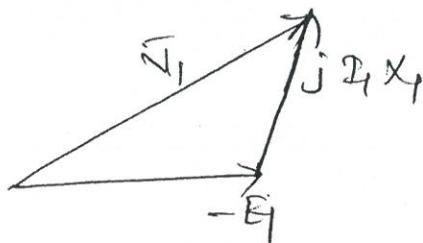


Condition for maximum efficiency:-

FB T3 Page No. 17

Transformer works on constant input voltage & hence the efficiency varies with the load.

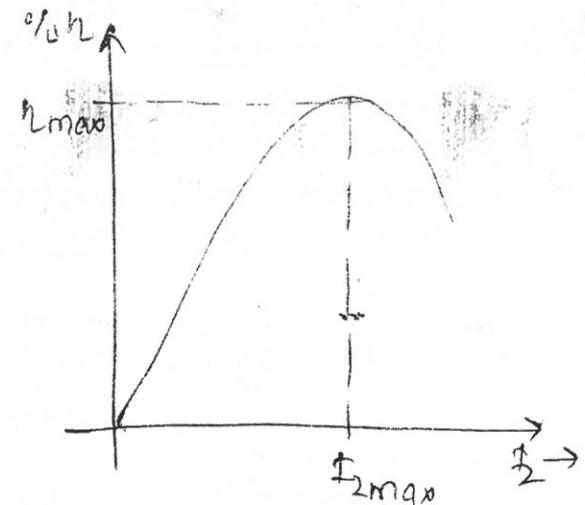As load increases, η increases. And at certain load current, it attains max. value. & further increment in load draws more load current hence η decreases.



$$\frac{d\eta}{dI_2} = 0 = \frac{d}{dI_2} \left[\frac{V_2 I_2 \cos \phi_2}{V_2 I_2 \cos \phi_2 + P_e + I_2^2 R_{2e}} \right]$$

$$= \frac{[V_2 I_2 \cos \phi_2 + P_e + I_2^2 R_{2e}] \cdot V_2 \cos \phi_2 - V_2^2 \cos^2 \phi_2 [V_2 \cos \phi_2 + I_2^2 R_{2e}]}{[V_2 \cos \phi_2 + P_e + I_2^2 R_{2e}]^2} = 0$$

$$= V_2^2 I_2^2 \cos^2 \phi_2 + P_e V_2 \cos \phi_2 + I_2^2 R_{2e} V_2 \cos \phi_2 - V_2^2 \cos^2 \phi_2 - V_2 I_2^2 R_{2e} \cos \phi_2 = 0$$

$$\Rightarrow V_2 \cos \phi_2 [P_e - I_2^2 R_{2e}] = 0$$

$$\Rightarrow P_e = I_2^2 R_{2e} = P_{CU}$$

means condition for achieving max. efficiency is

$$P_{CU \text{ max}} = P_{iron \text{ loss}}$$

Lead current I_2m at maximum efficiency:-

$$I_2^2 \max R_{2e} = P_e \Rightarrow I_2m = \sqrt{\frac{P_e}{R_{2e}}}$$

$$\frac{I_2m}{I_2(\text{FL})} = \frac{1}{I_2(\text{FL})} \sqrt{\frac{P_e}{R_{2e}}} = \sqrt{\frac{P_e}{I_2^2(\text{FL}) R_{2e}}}$$

$$I_2m = I_2(\text{FL}) \sqrt{\frac{P_e}{P_{CU}(\text{FL})}}$$

KVA supply at max. efficiency:-

$$(\text{KVA})_m = V_2 I_2m = V_2 I_2(\text{FL}) \sqrt{\frac{P_e}{P_{CU}(\text{FL})}} = \text{KVA max} \sqrt{\frac{P_e}{P_{CU}(\text{FL})}}$$

$$\text{Ans. } \% n = \frac{\frac{V_2}{V_1} I_{2m} \cos \phi_2}{\frac{V_2}{V_1} I_2 \cos \phi_2 + 2P_i} \times 100$$

$$\boxed{\% n = \frac{(kVA)_{n \text{ max}} \cos \phi_2}{(kVA)_{n \text{ max}} \cos \phi_2 + 2P_i} \times 100}$$

Qⁿi:- A 500 kVA TIF has an iron loss 500W & full load copper loss of 600W. calculate η at $3/4$ th full load & 0.8 pf. Also calculate the n_{max} at that pf.

Solⁿi:-

$$\begin{aligned} \% n &= \frac{n (kVA \text{ rating}) \cos \phi}{n (kVA \text{ rating}) \cos \phi + P_i + n^2 P_{\text{cu}} (\text{FL})} \times 100 \\ &= \frac{.75 \times 500 \times .8 \times 10^3}{.75 \times 500 \times 10^3 \times .8 + 500 + (.75)^2 \times 600} \times 100 \\ &= 99.7216\% \end{aligned}$$

$$\begin{aligned} (kVA)_{\text{for } n_{\text{max}}} &= (kVA)_{\text{FL}} \times \sqrt{\frac{P_i}{P_{\text{cu}} (\text{FL})}} = 500 \sqrt{\frac{500}{600}} \\ &= 456.435 \text{ kVA} \end{aligned}$$

$$\begin{aligned} \% n &= \frac{456.435 \times 10^3 \times .8}{456.435 \times 10^3 \times .8 + 500 + 500} = 99.7268\% \end{aligned}$$

Qⁿi:- A 1kW TIF on full load has an impedance drop of 20V and resistance drop of 10V. calculate the pf when its regulation will be zero.

Solⁿi:- $E_2 = V_2$ at zero voltage regulation

$$I_2 Z_{re} = 20, \quad I_2 R_{re} = 10 \quad \text{then}$$

$$I_2 X_{re} = \sqrt{(20)^2 - (10)^2} = 17.32$$

$$\phi = \tan^{-1} \left[\frac{I_2 R_{re}}{I_2 X_{re}} \right] = \tan^{-1} \left[\frac{10}{17.32} \right]$$

$$\phi = 30^\circ$$

$$\boxed{\cos 30^\circ = .866 \text{ leading}}$$

$\eta = 98.77\%$ of 400 KVA TIF, when delivering full load of 1.8 p.f and $\eta = 99.13$ at half load unity p.f.

Calculate ① Iron loss, ② full load cu loss

Soln:- At full load
at 1.8 p.f.

$$\eta = \frac{(\text{KVA rating}) \text{ cos}\phi}{(\text{KVA rating}) \text{ cos}\phi + P_i + P_{cu}} \times 100$$

$$\frac{98.77}{100} = \frac{400 \times 10^3 \times 1.8}{400 \times 10^3 \times 1.8 + (P_i + P_{cu})}$$

$$P_i + P_{cu}(\text{ff}) = 3985 \text{W} \quad \text{--- (1)}$$

At half power
unity p.f

$$\eta = 99.13 = \frac{400 \times 10^3 \times 1 \times \frac{1}{2} \times 100}{\frac{1}{2} \times 400 \times 10^3 + P_i + \left(\frac{1}{2}\right)^2 P_{cu}(\text{ff})}$$

$$P_i + \frac{P_{cu}(\text{ff})}{4} = 1755.2 \text{W} \quad \text{--- (2)}$$

Solve (1) & (2) $\therefore P_{cu} = 2973 \text{W}$ & $P_i = 1012 \text{W}$ Answer.

Qn:- A 40KVA TIF has a core loss of ~~400~~ ⁴⁰⁰ watts and full load cu loss of 800 watts, if load p.f is 1.9 lagging

- ① The full load efficiency &
- ② % of full load at which max. efficiency occurs.

Answer:- KVA = 40, $P_i = 40$, $P_{cu} = 800 \text{W}$, $\text{cos}\phi = 1.9$,

$$\eta = \frac{(\text{KVA rating}) \times 10^3 \text{ cos}\phi}{(\text{KVA rating}) \times 10^3 \text{ cos}\phi + P_i + P_{cu}}$$

$$= \frac{40 \times 10^3 \times 1.9}{40 \times 10^3 \times 1.9 + 400 + 800} = 96.77\%$$

Calculate load at max. efficiency

KVA for max. efficiency = Full load KVA $\times \sqrt{\frac{P_i}{P_{cu}}}$

$$= 40 \times \sqrt{\frac{400}{800}} = 28.28 \text{ KVA}$$

Q1:- calculate the Regulation of a TIF in which ohmic drop is 1% and reactance drop is 5% of the voltage of p.f are
 (i) \angle lagging pf (ii) \angle leading pf.

Soln:- $\% R = \frac{I_2 R_{2e} \cos \phi \pm I_2 X_{2e} \sin \phi}{V_2} \times 100$

$\cos \phi = .8$
 then
 $\sin \phi = .6$

$$= \left[\frac{I_2 R_{2e} \cos \phi \pm I_2 X_{2e} \sin \phi}{V_2} \right] \times 100$$

$$= [pu \text{ resistance} (\cos \phi) \pm pu \text{ reactance} (\sin \phi)] \times 100$$

$$= \left[\frac{1}{100} \cos \phi \pm \frac{5}{100} \sin \phi \right] \times 100$$

(i) when $\cos \phi = .8$ lagging \rightarrow Assume +ve sign

$$\% R = [1 \times .8 + 5 \times .6] = 3.8\%$$

(ii) when $\cos \phi = .8$ leading \rightarrow Take -ve sign

$$\% R = [1 \times .8 - 5 \times .6] = -2.2\% \text{ Answer}$$

Q2:- A 1 ϕ TIF delivers 10A, 220V to a resistive load while the primary draws 6A at \angle lagging pf from 450V, 50Hz supply,
 $K = 15$. Calculate efficiency & voltage regulation $\% R = ?$

Soln:- (i) $\eta = \frac{\frac{V_2 I_2 \cos \phi_2}{V_1 I_1 \cos \phi_1}}{1}$

$\cos \phi_2 = 1$
 $\cos \phi_1 = .9$

$$= \frac{220 \times 10 \times 1}{450 \times 6 \times .9}$$

$$= \frac{2200}{2430} = .9053 \text{ or } 90.53\%$$

(ii) $\% R = \frac{E_2 - V_2}{V_2} \times 100$

$\frac{E_2}{E_1} = \frac{N_2}{N_1} = 2$
 $E_2 = .5 \times 450 = 225$

$$= \frac{225 - 220}{220} \times 100$$

$$= 2.27\%$$

$$\boxed{\% R = 2.27\%}$$

Qn1 - A 20kVA, 440/220V, 1φ T/F, 50Hz has $P_e = 324W$, $P_{cu} = 100W$ at half load current, determine -

- η at full load current & 8 lagging pf
- % full load load kVA when η will be max.

Soln1 - (i) Output at 8 lagging pf = $20 \times 10^3 \times 0.8$
 $= 16 \text{ kW}$

$$(P_{cu})_{1/2 \text{ load}} = (n)^2 (P_{cu})_{FL} \quad n = \frac{1}{2}$$

$$100 \times 4 = (P_{cu})_{FL} = 400W = 0.4 \text{ kW}$$

$$\frac{P_e}{\text{Total losses}} = \frac{324W}{= 0.724 \text{ kW}}$$

$$\eta \text{ at full load } 8 \text{ lagging pf} = \frac{\text{output} \times 100}{0.1T + T \cdot \text{losses}} = \frac{16}{16 + 0.724} \times 100 = 95.67\%$$

$$\text{(ii) KVA at max } \eta = (kVA)_{FL} \sqrt{\frac{P_e}{P_{cu}(FL)}} \\ = (20 \text{ kVA})_{FL} \sqrt{\frac{324}{400}} = (kVA)_{FL} \times 0.9$$

Efficiency max. at 90% full load KVA

Qn1 - A 25kVA, 2200/220V, 1φ T/F has primary resistance & secondary resistance are 1Ω & 0.01Ω respectively. Find full load efficiency at 8 pf if iron losses in T/F is 200W.

$$(I_2)_{FL} = \frac{25 \times 10^3}{220} = 133.6A$$

$$R_{2e} = R_2 + k^2 R_1 = 0.01 + \left(\frac{220}{2200}\right)^2 \times 1 = 0.025\Omega$$

$$\frac{K_u}{1000} (P_{cu} \text{ FL}) = (I_2^2 \text{ FL}) R_{2e} = (133.6)^2 \times 0.02 = 2.56 \text{ kW}$$

$$\text{Total losses} = 2.56 + 200 = 2.756 \text{ kW}$$

$$\text{Full load efficiency} = \frac{2.5 \times 0.8}{2.5 \times 0.8 + 2.756} \times 100 = 97.6\%$$

Qn :- A 600 kVA, 1φ TIF when works at unity pf has 92% efficiency at full load & also at half full-load. Determine n at unity pf and 60% of full load.

Soln :- There is same efficiency at two different loading condition, so we calculate P_{cu} & P_i

$$\text{output} = 600 \times 1 = 600 \text{ kW}$$

$$\rightarrow n = \frac{\text{output}}{\text{input}} \quad \text{then input} = \frac{600}{.92} = 652.2 \text{ kW}$$

At full load \rightarrow Total FL loss = $652.2 - 600 = 52.2 \text{ kW}$

$$P_i + P_{cu,FL} = 52.2 \text{ kW} \quad \text{--- (1)}$$

At half load output = 300 kW

$$\text{input} = 300/.92 = 326.1$$

$$P_i + \left(\frac{1}{2}\right)^2 P_{cu} = 326.1 - 300 = 26.1 \text{ kW} \quad \text{--- (2)}$$

By (1) & (2) $P_c = 34.8 \text{ kW}, P_i = 17.4 \text{ kW}$

Efficiency at 60% full-load = $\frac{.6 \times 600 \times 1}{.6 \times 600 \times 1 + 17.4 + (.6)^2 \times 34.8} \times 100$

n at 60% full load = 96.3%

Qn :- A 400 kVA TIF has $P_i = 2 \text{ kW}$ & max. efficiency occurred at .8 pf when load is 240 kW. calculate

- max efficiency at unity pf
- efficiency on full-load at .71 pf lagging.

Soln :- KVA at max. efficiency = $\frac{240 \text{ kW}}{.8} = 300 \text{ kVA}$

& at max. efficiency $P_i = P_{cu}$

(i) then n at unity pf = $\frac{300 \times 1}{300 \times 1 + 2 + 2} \times 100 = 98.6\%$

(ii) $P_i = 2 \text{ kW}, P_{cu} = \left(\frac{400}{300}\right)^2 \times 2 = 3.55 \text{ kW}$

n at .71 pf = $\frac{400 \times .71}{400 \times .71 + 2 + 3.55} \times 100 = 98\%$


Indirect Loading Test of T/F T.3 + E.Sem.

AIM:- To calculate efficiency and regulation on any given load condition and at any power factor can be predetermined by such tests w/o actual load testing. That's why we can save power losses during actual load tests & results are effective in Indirect loading Tests which are -

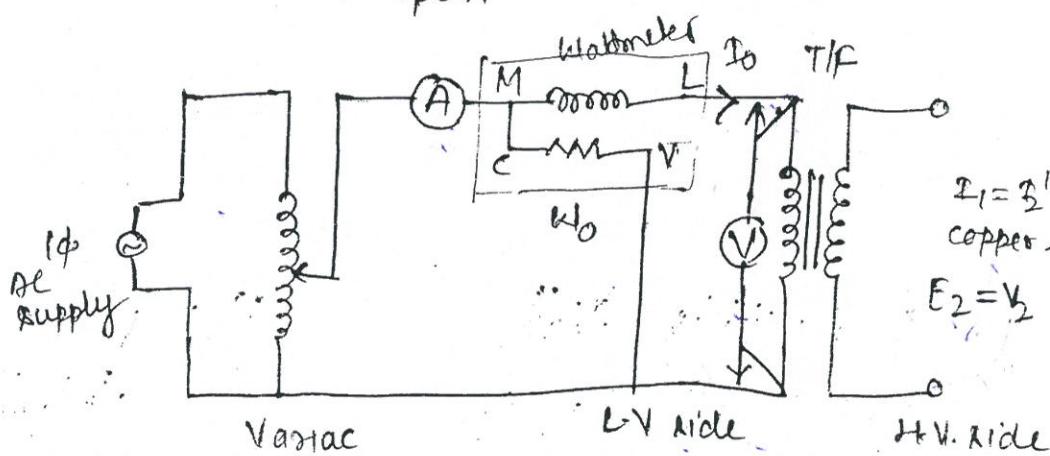- (i) Open circuit Test (O.C. test)
- (ii) Short circuit Test (S.C. test)

Open Circuit Test :- (From loss determination) (constant for all loads)

- Transformer primary side (L.V. side) is connected to a a.c. supply through ammeter, wattmeter and variac.
- Transformer secondary side (H.V. side) is kept open. \rightarrow input power
 \rightarrow input current
 \rightarrow rated pri. voltage
Sometime very high resistance is applied at rec., here secondary is treated as open.



$I_2 = 0$ hence
 $I_2' = 0$ &
 $I_1 = I_1' + I_0 = I_0$ hence
 copper loss are very low
 $E_2 = V_2$ (open)

* By Primary side, we observed pri. side rated values

V_0 (Volt)	I_0 (amp)	W_0 (watts)
Rated		


* When Rec. is open, T/F is on no load

$$I_m = I_0 \sin \phi_0, \quad I_c = I_0 \cos \phi_0$$

$$W_0 = V_0 I_0 \cos \phi_0 = P_i = \text{iron loss}$$

* Now we can calculate

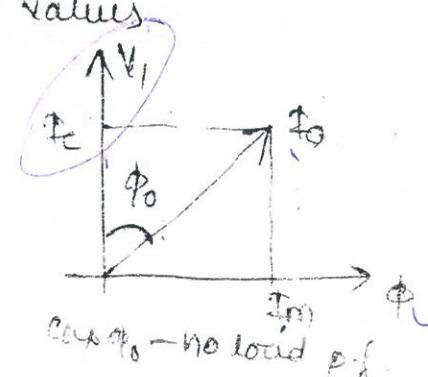
$$R_0 = \frac{V_0}{I_0} \quad \& \quad X_0 = \frac{V_0}{I_0}$$



$$I_c = I_0 \cos \phi_0$$

$$I_m = I_0 \sin \phi_0$$

② Short circuit Test (Sc. Test)

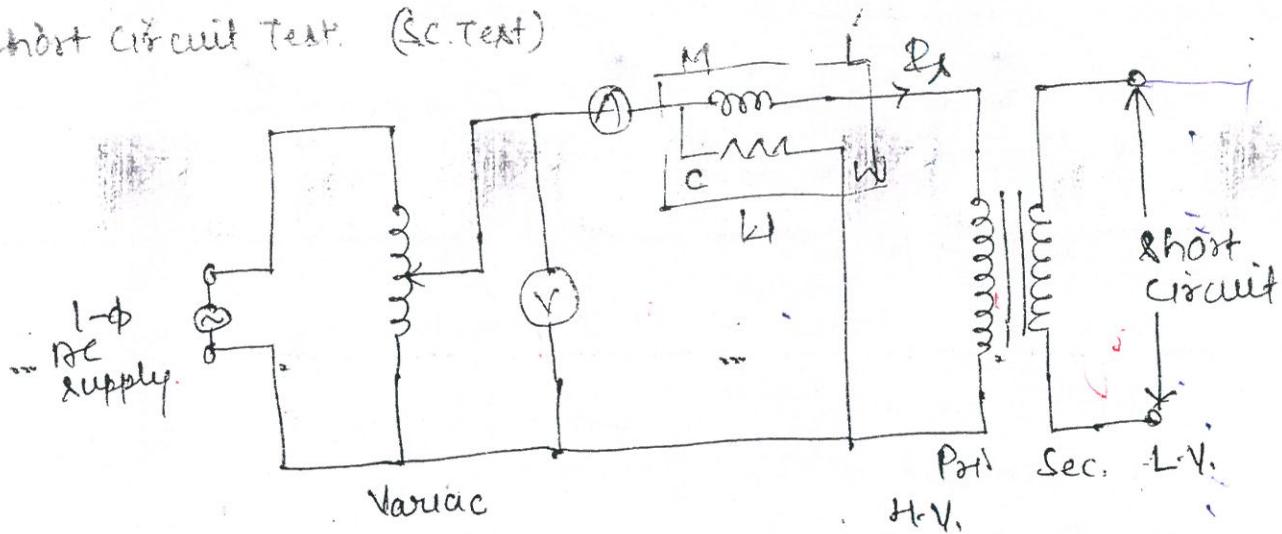

- Primary is connected to ac supply 1-φ through variac, voltmeter, ammeter, and wattmeter.
- The sec. is short circuited by thick copper wire. We know high voltage side is always low current side.
- ~~Then~~ why →? ~~H.V.~~ side - pri. side (Supply side)
 Then ~~H.V.~~ side - sec side (shorted side)
 L.V.
- For shorting sec. side, very \approx low resistance connect which draw very large current. Due to very large current, overheating and burning of TLF may happen. To limit this large short circuit current, primary is supplied to very low voltage ~~side~~ & adjusted by variac. Hence it's also termed as low voltage test.

V _{AC} (volt)	I _{SC} (A)	W _{AC} (Watts)
	Rated	

- Pri. side - applied voltage is low & iron losses are \propto of applied voltage. i.e. iron losses are very \approx small.

- Sec. side experienced rated current i.e. we get total full load copper losses.

$$W_{AC} = (P_{cu})_{losses} + L = V_{AC} I_{SC} \cos \phi_{AC} = I_{SC}^2 R_{le}$$

$$cos \phi_{AC} = \frac{W_{AC}}{V_{AC} I_{SC}}$$

$$R_{le} = \frac{W_{AC}}{I_{SC}^2}$$

$$Z_{le} = \frac{V_{AC}}{I_{SC}} = \sqrt{R_{le}^2 + X_{le}^2} \Rightarrow X_{le} = \sqrt{Z_{le}^2 - R_{le}^2}$$

Efficiency Calculation from O.C. & S.C. tests /

2

① From O.C. $U_o = P_i$

From S.C. $U_{sc} = P_{sc} (F.L)$

& we know

$$\eta \% = \frac{V_2(I_2)_{F.L} \text{ cas} \phi}{V_2(I_2)_{F.L} \text{ cas} \phi + U_o + U_{sc}} \times 100$$

means for any given P.F. $\text{cas} \phi$, we determined the efficiency.

② for fractional load

$$\eta \% = \frac{n V_2 I_2 \text{ cas} \phi}{n V_2 I_2 \text{ cas} \phi + U_o + n^2 U_{sc}} \times 100$$

⇒ Regulation Calculation is determined as before

$$\% R = \frac{I_1 R_{1e} \text{ cas} \phi \pm I_2 X_{1e} \text{ sin} \phi}{V_1} \times 100$$

referred to pri. side

I_1, I_2 are rated current at full load &

V_1, V_2 are rated voltage.

$$\% R = \frac{I_2 R_{2e} \text{ cas} \phi \pm I_1 X_{2e} \text{ sin} \phi}{V_2} \times 100$$

referred to rec. side

If load is in fraction then

$$I_1 = n(I_1)_{F.L}$$

$$I_2 = n(I_2)_{F.L}$$

$$P_{cu} = 1800.69 \text{ watt}$$

$$P_e = 2000.18 \text{ watt}$$

8

Ques ① & ②

$$P_e + (5) P_{cu} = 2300.74$$

$$P_e + n^2 P_{cu} = 2300.74$$

$$\text{Total loss} = \text{Input - Output} = \frac{100 \times 10^3}{100 \times 10^3} = 977.51$$

$$\text{Input power} = \frac{\text{Input loss}}{100 \times 10^3} = \frac{977.51}{100 \times 10^3}$$

$$= 100 \times 10^3 \text{ watt}$$

$$= 100 \times 200 \times 10^3$$

$$\text{Total output power at half load} = n \times 200 \times 10^3$$

$$\text{Similarly, Total output power at full load} \Rightarrow P_e + P_{cu} = 3800.88$$

$$= 3800.88 \text{ W}$$

$$\text{Total loss} = \text{Input - Output} = \frac{981.35}{200 \times 10^3} = 200 \times 10^3 \text{ watt}$$

$$\text{Input power} = \frac{981.35}{200 \times 10^3}$$

$$\text{Input power}$$

$$n \% = \frac{\text{Output power}}{\text{Input power}} \times 100$$

Full load
Efficiency

$$= 200 \times 10^3 \text{ watt}$$

$$\text{Total output power at full load} = 250 \times 10^3 \times 0.8$$

8 cu watt

Efficiency

Q. If the efficiency is 87.75%, calculate the load

Q. If the efficiency is 87.75%, calculate the load

Q. 35 KW, if the load is 75%, calculate the efficiency at full load

Q2:- A 5KVA, ~~500/200V~~, 50Hz, 1Ø TIF give the following readings.

O.C. Test:- 500V, 1A, 50W (L.N. side)

S.C. Test:- 25V, 10A, 60W (L.N. side shorted)

- Determine → (i) η at full load & leading p.f.
(ii) η at 60% of full load & leading p.f.
(iii) % Voltage Regulation on full load & leading p.f.
(iv) Draw equivalent circuit referred to pri. side with all elements.

Solⁿ:- From O.C. Test
(Iron losses) no. load.

$$I_1 = I_0 = 1A, \quad U_0 = 50W$$

$$U_0 = 500V$$

$$\Rightarrow \text{Core} \phi_0 = \frac{U_0}{U_0 I_0} = \frac{50}{500 \times 1} = 0.1$$

$$\Rightarrow I_c = I_0 \text{Core} \phi_0 = 1 \times 0.1$$

$$I_c = 0.1$$

$$\Rightarrow I_m = I_0 \sin \phi_0 = 1 \times 0.9949$$

$$I_m = 0.9949$$

$$\Rightarrow P_e = U_0 = 50W$$

~~Core~~

$$(i) \eta \% = \frac{(\text{VA rating}) \text{Core} \phi_2}{[(\text{VA})_{\text{rating}} \text{Core} \phi_2 + P_e] + P_{\text{cu}}(\text{F.L.})} \times 100$$

$$= \frac{5 \times 10^3 \times 0.8}{5 \times 10^3 \times 0.8 + 50 + 60} \times 100$$

$$= 97.32\%$$

$$(ii) \eta \% = \frac{n (\text{VA rating}) \text{Core} \phi_2}{n (\text{VA})_{\text{rating}} + P_e + n^2 P_{\text{cu}}} \times 100 = \frac{6 \times 5 \times 10^3 \times 0.8}{6 \times 5 \times 10^3 + 50 + (0.09) \times 6} \times 100$$

$$= 97.103\%$$

From S.C. Test
(Pu (F.L.) losses)

$$U_{AC} = 25V, \quad I_{AC} (\text{Coated}) = 10A$$

$$U_{AC} = 60W \quad \Rightarrow P_{\text{cu}}(\text{F.L.})$$

$$R_{le} = \frac{U_{AC}}{I_{AC}} = \frac{25}{10} = 2.5\Omega$$

$$R_{le} = 2.5\Omega$$

$$R_{le} = \frac{U_{AC}}{I_{AC}^2} = \frac{60}{(10)^2}$$

$$R_{le} = 6\Omega$$

$$X_{le} = \sqrt{(2.5)^2 - (6)^2}$$

$$X_{le} = 2.4269\Omega$$

$$(ii) I_{FL} = I_{AC} = 10A$$

$$\text{or } I_{(FL)} = \frac{\text{VA rating}}{V} = \frac{5 \times 10^3}{500} = 10A$$


(iii) $\% R = ?$ leading

$$\% R = \frac{(A_{FL} R_{ie} \cos \phi_2 - A_{IF} X_{ie} \sin \phi_2) \times 100}{V_1}$$

$$= \frac{10 \times 6 \times 8 - 10 \times 2.4269 \times 6}{500} \times 100$$

$$= -1.95\%$$

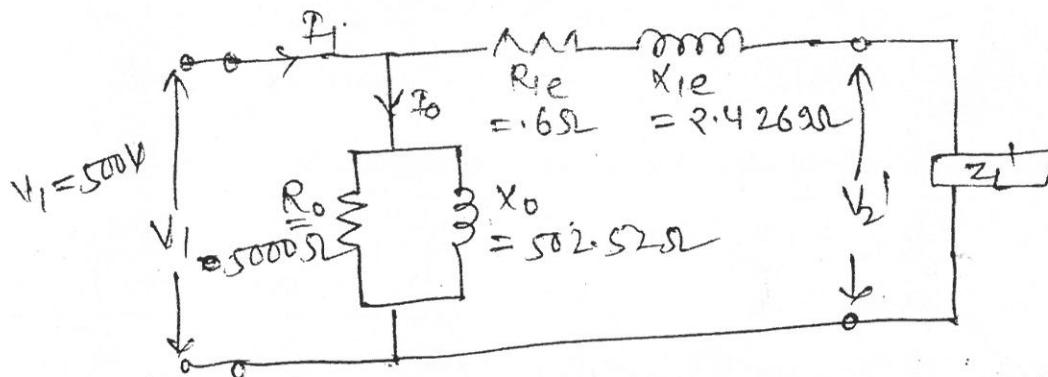(iv) Equivalent circuit referred to primary



$$R_0 = \frac{V_1}{I_1} = \frac{500}{0.1} = 5000 \Omega, \quad X_0 = \frac{V_1}{I_m} = \frac{500}{0.9948} = 502.52 \Omega$$

Soln:- In no-load test 1- ϕ TIF, the following data were obtained:-

Pr. voltage : 200V, sec. voltage : 110V

Pr. current : 0.5A, Power input : 30W, Resistance (Pr.) = 0.6

Find:- (i) Turn ratio (ii) I_m magnetizing ~~constant~~ component of no-load

(iii) Iron loss (iv) Iron loss component of no-load current

$$\text{Soln:- (i) Turn ratio} = \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{200}{110} = 2$$

$$\begin{aligned} \text{(ii) } I_m &= I_0 \sin \phi_0 \\ &= 0.5 \times 0.962 \\ &= 0.48 A \end{aligned}$$

$$\begin{aligned} &\text{& } V_0 = V_1 \sin \phi_0 \\ \cos \phi_0 &= \frac{30}{200 \times 0.5} = 0.273 \\ \sin \phi_0 &= 0.962 \end{aligned}$$

$$\begin{aligned} \text{(iv) } I_0 &= I_0 \cos \phi_0 \\ &= 0.5 \times 0.273 = 0.1365 A \end{aligned}$$

$$\text{(iii) Iron loss} = I_0^2 R_0 = (0.5)^2 \times 0.6 = 0.15 W$$

$$\text{Iron loss} = 0.15 \times 0.9948 = 0.14923 W$$

A 10KV, 200/400V, 50Hz 1φ-TIF give the following test results!

O.C. Test: - 200V, 1.3A, 120W, on L.V. side

S.C. Test: - 22V, 30A, 200W, on H.V. side

calculate:- (i) I_m , I_w , (ii) R_0 , X_0 , (iii) %R at 8pf leadup under supply f.L.

Soln:- O.C. Test: LV side (ptt. side)

$$V_1 = 200V, I_0 = 1.3A, W_0 = 120W$$

$$(i) I_m = I_0 \sin \phi_0 \quad \text{--- (1)}$$

$$I_w = I_0 \cos \phi_0 \quad \text{--- (2)}$$

$$W_0 = V_1 I_0 \cos \phi_0$$

$$\cos \phi_0 = \frac{120}{200 \times 1.3} = 0.462$$

$$\text{from eqn (2)} \quad I_w = 1.3 \times 0.462 = 0.6A \quad \text{--- (3)}$$

$$\text{from eqn (1)} \quad I_m = 1.3 \times 0.886 = 1.15A \quad \text{--- (4)}$$

$$(ii) R_0 = \frac{V_1}{I_w} = \frac{200}{0.6} = 333\Omega$$

$$X_0 = \frac{V_1}{I_m} = \frac{200}{1.15} = 174\Omega$$

$$(iii) Z_{2e} = \frac{22}{30} = 0.733\Omega \quad \left(\frac{V_{AC}}{I_{AC}} \right)$$

$$R_{2e} = \frac{V_{AC}}{I_{AC}^2} = \frac{200}{(30)^2} = 0.222 \quad \text{--- (5)}$$

$$X_{2e} = \sqrt{(0.733)^2 - (0.222)^2} = 0.698\Omega \quad \text{--- (6)}$$

$$F.L \text{ on H.V. side} = \text{we know} = 25A = \frac{1}{2} f.L$$

$$\begin{aligned} \text{referred to rec. side} &= I_2 [R_{2e} \cos \phi_2 - X_{2e} \sin \phi_2] / V_2 \times 100 \\ \text{at leadup pf} &= 25 [0.222 \times 0.8 - 0.698 \times 0.6] / 400 \times 100 \\ &= -1.5\% \quad \text{--- (7)} \end{aligned}$$

S.C. Test: H.V. side (rec. side)

$$I_{AC} = 30A \quad (\text{rec. current})$$

$$I_2 (f.L) = \frac{10 \times 10^3}{400} = 25A$$

Qn:- A 10KVA, 200/400V, 50Hz, 1-φ T/F gave the following test results:-

O.C test : 200V, 1.3A, 120W — on L.V. side

S.C. test : 22V, 30A, 200W — on H.V. side

calculate : ① Efficiency and rec. terminal voltage when supplying full load at .8 leading power factor.

② calculate the load at unity p.f corresponding to max. efficiency.

Soln:- ① We calculate $\eta\% = \frac{\text{output}}{\text{input}} \times 100$ & Voltage drop V_2
 $V_2 = I_2 [R_{2e} \cos \phi - X_{2e} \sin \phi]$

$$\text{Input} = \text{output} + \text{losses}$$

$$\text{then output power (F.L)} = 10 \times 10^3 \cos \phi \text{ (kWatt)} \\ = 10 \times 10^3 \times 0.8 = 8 \text{ kW}$$

→ We'll find cu losses, iron losses

O.C. test gives Iron loss = 120W = .12 kW = P_i

S.C. test gives cu losses but not full load $P_{ac} = 200W$

$$I_2 \text{ FL} = \frac{10 \times 10^3}{400} = 25A \quad I_{ac} = 30$$

$$\frac{I_2 \text{ FL}}{I_{ac}} = n = \frac{25}{30} = \frac{5}{6}$$

$$\text{Full load cu loss} P_{cu,FL} = n^2 P_{ac} = \left(\frac{5}{6}\right)^2 \times 200 \\ = 140W = .14 \text{ kW}$$

$$(\text{Total losses})_{F.L} = P_i + P_{cu,FL} = .12 + .14 = .26$$

$$\eta\% = \frac{\text{output}}{\text{output} + \text{losses}} = \frac{8}{8 + .26} \times 100 = 96.85\%$$

$$\text{Voltage drop} = I_2 [R_{2e} \cos \phi - X_{2e} \sin \phi] = -6V \quad \left. \begin{array}{l} \text{mean voltage} \\ \text{side due to leading p.f.} \end{array} \right.$$

$$\text{Rec. voltage} = 400 + 6 = 406V$$

$$(ii) \text{ KVA for max. efficiency} = \text{F.L KVA}$$


$$= 10 \sqrt{\frac{120}{140}} = 9.25 \text{ KVA}$$

$$\text{Load at unity p.f} = 9.25 \times 1 = 9.25 \text{ KVA}$$


Auto Transformer:-

- * It's a special type of TIF which has only one winding only, wound over a closed magnetic circuit of low permeability i.e. Auto TIF is a single winding TIF of an iron core and a part of winding is common to both primary and secondary circuit.

*

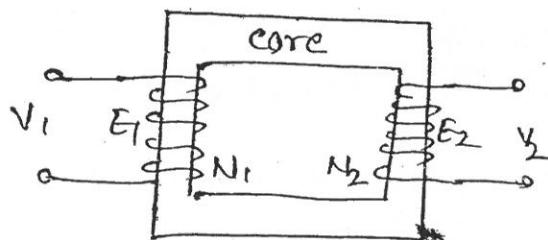


a) Two-winding transformer

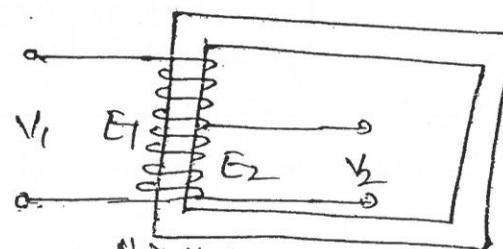


constructional view

b) Auto transformer

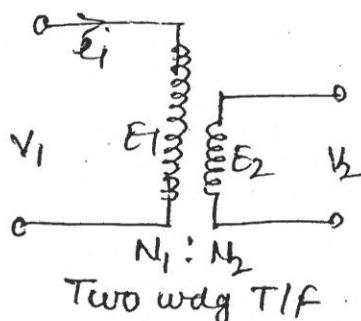

Two wdg TIF

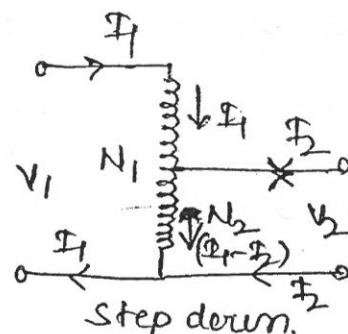

Step down.



Step Up

- * Operating principle and construction of an auto TIF is same, but in 2-wdg TIF, pri. wdg are completely insulated to rec. wdg & magnetically coupled with a common core.


While, in auto TIF pri. & rec. wdg are inter-related to each other.

- * Neglect the losses, leakage reactance & I_m then for ideal TIF,


Transformation Ratio $k = \frac{V_2}{V_1} = \frac{I_1}{I_2} = \frac{N_2}{N_1}$

> Theory of Auto-transformer:-

→ Assume an ideal step-down TIF on load

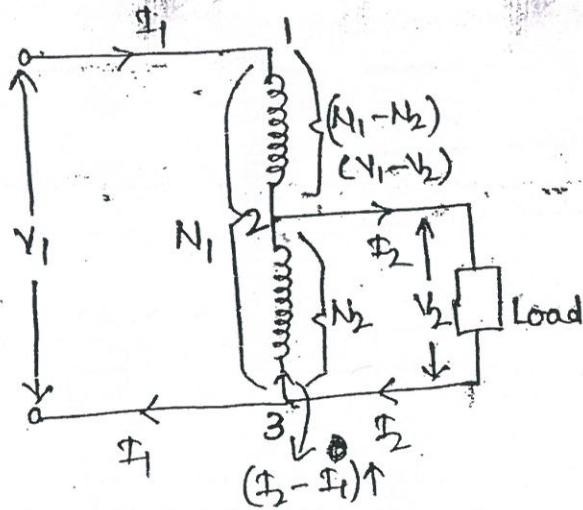
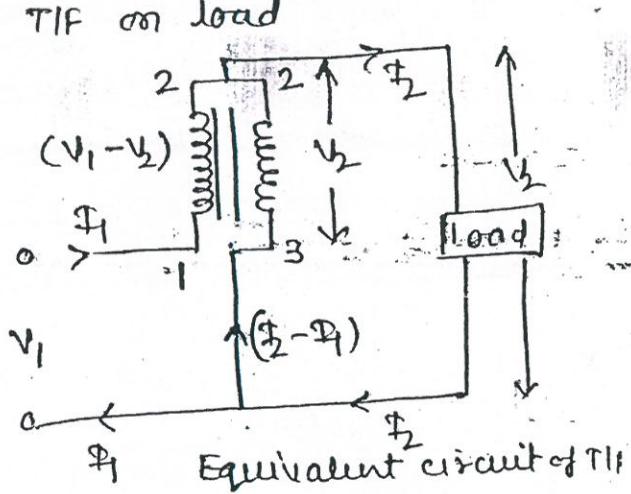
$$\begin{aligned}
 (V_1 - V_2) \Phi_1 &= (\Phi_2 - \Phi_1) V_2 \\
 \Rightarrow V_1 \Phi_1 - V_2 \Phi_1 &= \Phi_2 V_2 - \Phi_1 V_2 \\
 \Rightarrow \boxed{\frac{V_2}{V_1} = \frac{\Phi_1}{\Phi_2}} &= K
 \end{aligned}$$



$$\frac{V_2}{V_1 - V_2} = \frac{N_2}{N_1 - N_2}$$

$$\Rightarrow V_2 (N_1 - N_2) = N_2 (V_1 - V_2)$$

$$\Rightarrow V_2 N_1 - V_2 N_2 = N_2 V_1 - N_2 V_2$$

$$\Rightarrow \boxed{\frac{V_2}{V_1} = \frac{N_2}{N_1} = K}$$

> Copper Saving:-

* Weight of Cu required in wdg of current \propto turns

→ 2-winding TIF : $W_{Cu, 2w} \propto (\Phi_1 N_1 + \Phi_2 N_2)$

→ Auto 1-wdg TIF : W_{Cu}

$$\begin{aligned}
 &\text{for section 1-2 of } \Phi_1 (N_1 - N_2) \\
 &\text{for section 2-3 of } (\Phi_2 - \Phi_1) N_2
 \end{aligned}
 \left. \begin{array}{l} \text{Total } W_{Cu, \text{autoTif}} \propto \\ \Phi_1 (N_1 - N_2) + N_2 (\Phi_2 - \Phi_1) \\ = \Phi_1 N_1 - \Phi_1 N_2 + N_2 \Phi_2 - \Phi_1 N_2 \\ = \Phi_1 N_1 + \Phi_2 N_2 - 2 \Phi_1 N_2 \end{array} \right.$$

* Now Ratio $\frac{\text{Weight of Cu in autoTif} (W_a)}{\text{Weight of Cu in 2-wdg TIF} (W_0)} =$

$$\frac{\Phi_1 N_1 + \Phi_2 N_2 - 2 \Phi_1 N_2}{(\Phi_1 N_1 + \Phi_2 N_2)}$$

$$= 1 - \frac{2 \Phi_1 N_2}{(\Phi_1 N_1 + \Phi_2 N_2)} = 1 - \frac{2 \frac{\Phi_1 N_2}{\Phi_1 N_1}}{2 + \frac{\Phi_2 N_2}{\Phi_1 N_1}} \quad \left. \begin{array}{l} \therefore \Phi_1 N_1 = \Phi_2 N_2 \\ \therefore \frac{\Phi_2 N_2}{\Phi_1 N_1} = 1 \end{array} \right.$$

$$= 1 - \frac{N_2}{N_1} = 1 - K$$

$$\frac{W_a}{W_0} = (1-K) \Rightarrow W_a = (1-K)W_0$$

* Saving in cu = Copper used in 2wdg TIF - Copper used in auto TIF

$$= W_0 - (1-K)W_0 = KW_0$$

Saving in cu = $K \times$ wdg of cu in 2wdg TIF

➤ Output:- In Auto TIF, pri. & sec. are connected magnetically & electrically.

Magnetically connected \rightarrow Transformer action

Electrically connected \rightarrow conductively (Directly cause to load)

$$\text{Output Apparent Power} = V_2 I_2$$

$$\begin{aligned} \text{Inductively Apparent Power transferred} &= V_2 (I_2 - I_1) \\ &= V_2 I_2 (1 - \frac{I_1}{I_2}) = V_2 I_2 (1-K) \\ &\text{or } V_1 I_1 (1-K) \end{aligned}$$

* Power transferred inductively = Input $\times (1-K)$

* Power transferred conductively = Input - Input $(1-K)$

$$= K \text{ Input. or } K \times \text{ output}$$

➤ Note:- Advantage of auto TIF decreases as ratio of transformation increases. Therefore, an auto TIF has more advantages at relative transformation ratio (near to 1).

Comparison between SWDG TIF & AUTO TIF

S.N.	Parameter	SWDG TIF	AUTO TIF
①	Winding	Pri. & Sec.	A part of wdg is common.
②	Movable contact	Not	Yes
③	Type	Step-UP & Step-Down.	Step-UP & Step-Down.
④	Copper Saving	None	Yes
⑤	Size	Large	Small
⑥	Cost	High	Low
⑦	Efficiency	Low	High.
⑧	Regulation	Poor	Better.
⑨	Application	Power supply, welding, isolation, Main TIF.	Variac, starting of ac motor, dimmerstat
⑩	Maintenance - cost	Low	High

➤ Summary of Auto TIF

→ I.M. Induction Machine
→ M/c - machine

Advantages	Disadvantages	Applications
① Higher efficiency (losses reduced)	① No isolation b/w pri. & sec. wdg. Dangerous for H.V. application.	① Starting for I.M & Syn. M/c by using tapping
② Better Voltage Regulation (Resistance Reduced)	② If common part of the wdg lost → O.Circuited then TIF action lost. Pri. voltage appear across the sec.	② Used as balance coil to give 3-wire neutral.
③ Small size & weight	→ S.C. then large current will appear to sec. side.	③ Used as boosters in ac feeders.
④ Easy Transportation	③ High maintenance due to movable part.	④ Variac for lab.
⑤ Less Cu required		⑤ Biggest Application - Regulating TIF
⑥ Low cost		⑥ D/A dimmerstat in cinema hall to reduce the intensity of bulb
⑦ Required small exciting current.		

an auto.TIF supplies a load of 2.5kW at 110V & at a power factor of unity. If the primary applied voltage is 220V. calculate Power supplied to load - (i) Inductively (ii) conductively. [Neglect losses]

Solⁿ:-

$$k = \frac{110}{220} = 0.5$$

Neglect losses, then output = Input

$$\begin{aligned} \text{(i) Power transferred inductively} &= \text{input} \times (1-k) \\ &= 2.5 \times (1-0.5) = 1.25 \text{ kW} \end{aligned}$$

$$\begin{aligned} \text{(ii) Power transferred conductively} &= k \times \text{input} = 0.5 \times 2.5 \\ &= 1.25 \text{ kW} \end{aligned}$$

* Qⁿ 1:- An auto TIF is used to transform from 500V to 440V. The load is 20kW at unity power factor. Neglecting losses and magnetizing current, find the currents in various part of wdg.


Solⁿ:- Step up auto TIF

$$\begin{aligned} I_2 &= \frac{20 \times 10^3}{440} \\ &= 45.45 \text{ Amp} \end{aligned}$$

$$V_1 I_1 = V_2 I_2$$

$$I_1 = \frac{440}{500} \times 45.45 = 40 \text{ A}$$

$$(I_2 - I_1) = 45.45 - 40 = 5.45 \text{ A}$$

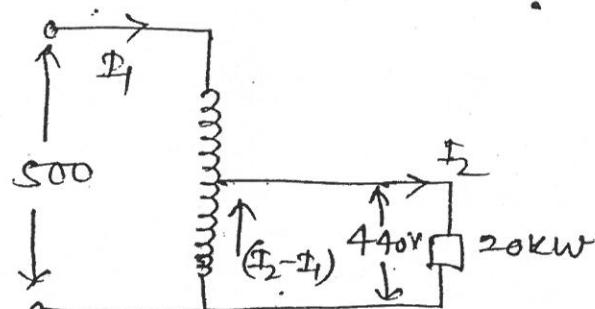

Qⁿ 1:- An auto TIF supplies a load of 5kW at 125V unity p.f. & pri. voltage is 250V, determine -


$$\text{(i) Transformer ratio } k = \frac{125}{250} = 0.5$$

$$\text{(ii) Sec. current } I_2 = \frac{5 \times 10^3}{125} = 40 \text{ A}$$

$$\text{(iii) Pri. current } I_1 = k I_2 = 0.5 \times 40 = 20 \text{ A}$$

$$\text{(iv) Power delivered inductively} = (1-k) P_T = \frac{(1-0.5) \times 5}{0.5} = 2.5 \text{ kW}$$
 
$$\text{(v) Power conductively} = k P_T = 0.5 \times 2.5 = 1.25 \text{ kW}$$



H.C. of D.C. Compound motor:-

(5)


Compound Motor

- capable of large torque (torque) at low speeds, basically torque increases as load increases.

- * Shunt field produce definite torque and series field help the main field to increase the total flux level.

Actually exact shape of below characteristic depends upon shunt & series field wdg contribution.

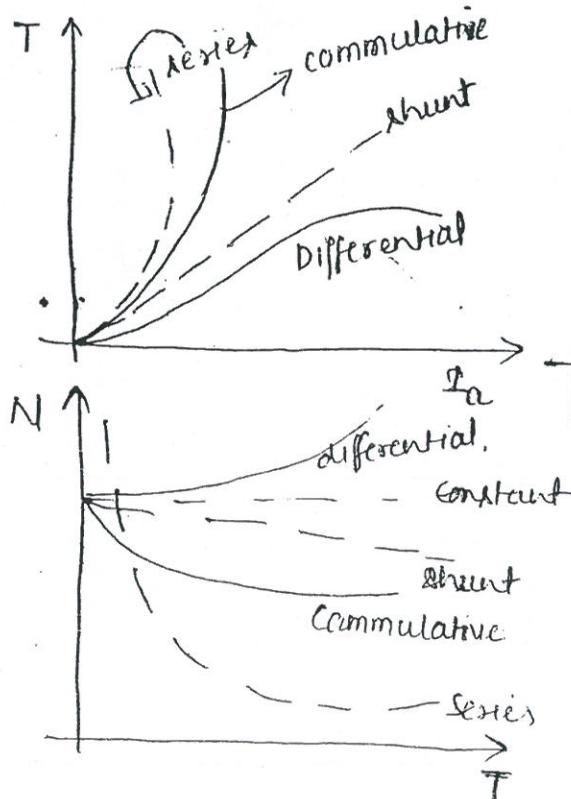
- * Which wdg dominant, characteristic turns the corresponding wdg (series / shunt) machine curve.




Differential Compound motor

- * This motor is not capable to generate large torque at low speeds, basically torque increases as load increases.

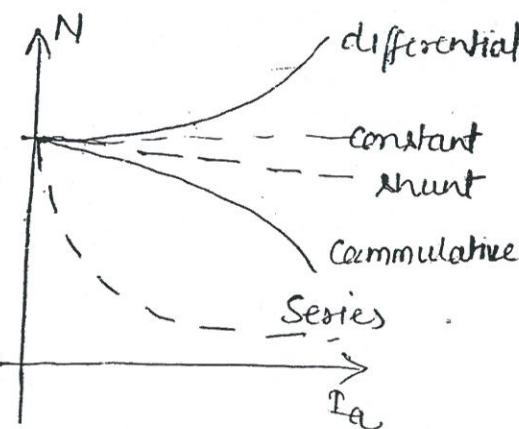- * Two fluxes (shunt & series field wdg) opposes each other, then the resultant flux decreases as load increase, & $N \propto \frac{1}{\phi}$, i.e. m/c runs at higher speed as load increase, which will be dangerous at high speed full load. so this type of m/c practically is not used.



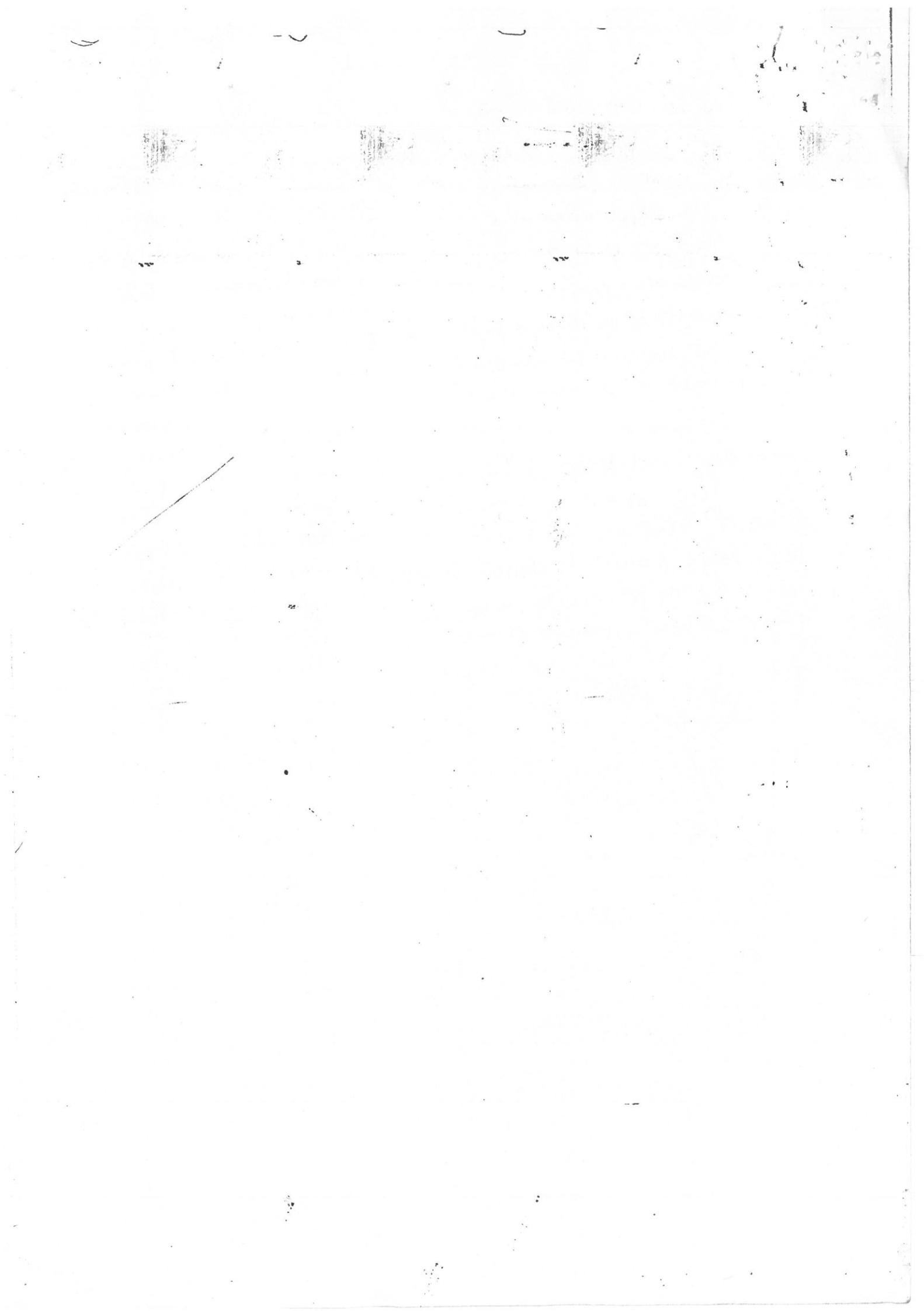

→ 10KVA, 200/400V, 50Hz 1φ-T/F give the following test result

O.C. :- 200V, 1.3A, 120W, on L.V. side

S.C. test :- 22V, 30A, 200W, on H.V. side

Calculate :- (i) Φ_m , Φ_w , (ii) R_o , X_o , (iii) %R at 8pf lead under supply F.L.

(i) O.C. Test: LV side (prim. side)

$$V_1 = 200V, I_0 = 1.3A, W_0 = 120W$$

$$(i) \Phi_m = \Phi_0 \sin \phi_0 \quad \text{--- (1)}$$

$$\Phi_w = \Phi_0 \cos \phi_0 \quad \text{--- (2)}$$

$$W_0 = V_1 I_0 \cos \phi_0$$

$$\cos \phi_0 = \frac{120}{200 \times 1.3} = 0.462$$

$$\text{From eqn (2)} \quad \Phi_w = 1.3 \times 0.462 = 0.6A$$

$$\text{From eqn (1)} \quad \Phi_m = 1.3 \times 0.886 = 1.15A \quad \boxed{8}$$

S.C. Test: H.V. side (sec. side)

$$I_{sc} = 30A \quad (\text{sec current})$$

$$I_2(\text{F.L.}) = \frac{10 \times 10^3}{400} = 25A$$

$$(ii) R_o = \frac{V_1}{\Phi_w} = \frac{200}{0.6} = 333\Omega$$

$$X_o = \frac{V_1}{\Phi_m} = \frac{200}{1.15} = 174\Omega$$

$$(iii) Z_{2e} = \frac{22}{30} = 0.733\Omega \quad \left(\frac{V_{sc}}{I_{sc}} \right)$$

$$R_{2e} = \frac{V_{sc}}{I_{sc}^2} = \frac{200}{(30)^2} = 0.222 \quad \text{Ω}$$

$$X_{2e} = \sqrt{(0.733)^2 - (0.222)^2} = 0.698\Omega \quad \text{Ω}$$

$$\text{F.L. on H.V. side} = \text{we know} = 25A = I_2 \text{ f.l.}$$

%R

$$\begin{aligned} \text{referred to sec. side} &= I_2 [R_{2e} \cos \phi_2 - X_{2e} \sin \phi_2] / V_2 \times 100 \\ \text{at leading pf.} &= 25 [0.222 \times 0.8 - 0.698 \times 0.6] / 400 \times 100 \\ &= -1.5\% \quad \text{Ω} \end{aligned}$$

Qn:- A 10 kVA, 200/400 V, 50Hz, 1-φ T/F gave the following test results:-

O.C test: 200V, 1.3A, 120W — on L.V. side

S.C. test: 22V, 30A, 200W — on H.V. side

Calculate: (1) Efficiency and sec. terminal voltage when supplying full load at .8. leading power factor.

(2) Calculate the load at unity p.f. corresponding to max. efficiency.

Soln:- (1) We calculate $\eta_n = \frac{\text{output}}{\text{input}} \times 100$ & Voltage drop V_2 for leading p.f.

$$V_2 = I_2 [R_{2e} \cos \phi - X_{2e} \sin \phi]$$

$$\text{Input} = \text{output} + \text{losses}$$

$$\text{then output power (F.L)} = 10 \times 10^3 \text{ cos} \phi \text{ (kWatt)} \\ = 10 \times 10^3 \times 0.8 = 8 \text{ kW}$$

→ We'll find cu losses, iron losses

O.C. test gives Iron loss $= 120W = 12 \text{ kW} = P_i$

S.C. test gives cu loss but not full load $I_{2e} = 200W$

$$I_2 = \frac{10 \times 10^3}{400} = 25A \quad I_{2e} = 30$$

$$\frac{I_2}{I_{2e}} = n = \frac{25}{30} = \frac{5}{6}$$

$$\text{Full load cu loss } P_{cu, F.L} = n^2 P_{cu, O.C.} = \left(\frac{5}{6}\right)^2 \times 200 \\ = 140W = 0.14 \text{ kW}$$

$$(\text{Total Losses})_{F.L} = P_i + P_{cu, F.L} = 12 + 0.14 = 12.14$$

$$\eta \% = \frac{\text{output}}{\text{output} + \text{losses}} = \frac{8}{8 + 12.14} \times 100 = 96.85\%$$

$$\text{Voltage drop} = I_2 [R_{2e} \cos \phi - X_{2e} \sin \phi] = -6V \quad \begin{array}{l} \text{means voltage} \\ \text{drop due to leading} \\ \text{p.f.} \end{array}$$

$$\text{sec. voltage} = 400 + 6 = 406V$$

$$(ii) \text{ KVA for max. efficiency} = F.L \text{ kVA} \sqrt{\frac{P_i}{P_{cu, F.L}}} \\ = 10 \sqrt{\frac{120}{140}} = 9.25 \text{ kVA}$$

$$\text{Load at unity p.f.} = 9.25 \times 1 = 9.25 \text{ kW}$$