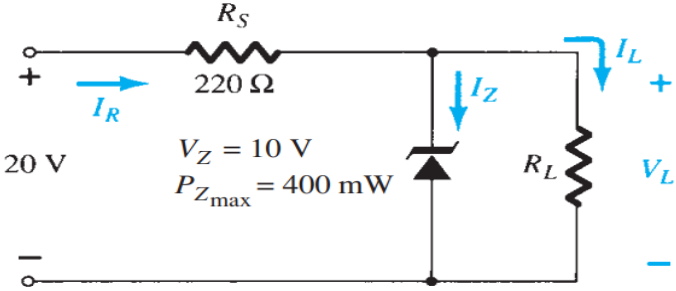
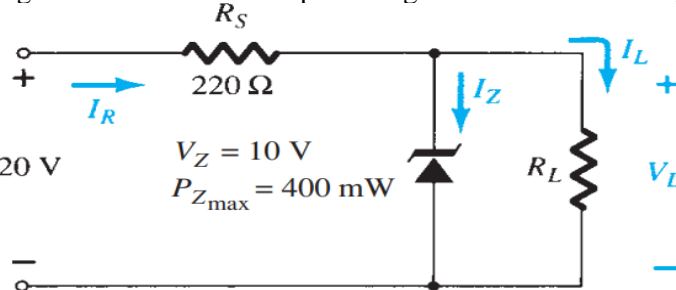
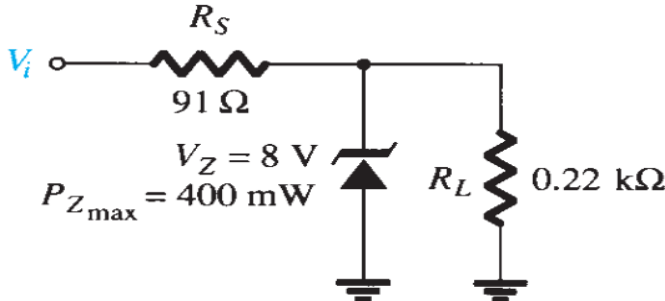




Assignment 3

S.No.	KL, CO	Question	Marks
1	K2, CO5	Describe briefly Satellite Communication with an appropriate block diagram.	5
2	K2, CO5	Describe briefly radar Communication with an appropriate block diagram.	5
3	K2, CO5	Describe the evolution of wireless communication in detail. OR Discuss the comparisons among 1G, 2G, 3G, 4G & 5G communication Technologies.	5
4	K2, CO1	(i) Draw and explain the GSM architecture. (ii) Write five differences between GSM and CDMA.	5
5	K2, CO1	Explain the working of Zener diode as a voltage regulator against: i. variable load resistance and fixed load resistor ii. variable input voltage and fixed load resistance	5
6	K3, CO1	<p>Determine V_L, I_L, I_Z and I_R for the network given below for $R_L = 180 \Omega$.</p> 	5
7	K3, CO1	<p>Determine the Range of R_L to maintain output voltage 10V of the network given below.</p> 	5

8	K3, CO1	<p>For the network given below, determine the range of V_I that will maintain V_L at 8 V and not exceed the maximum power rating of the Zener diode.</p> 	5
9	K3, CO1	<p>Design a voltage regulator that will maintain an output voltage of 20 V across a 1-kΩ load with an input that will vary between 30 V and 50 V. That is, determine the proper value of R_S and the maximum Zener current I_{ZM}</p>	5
10	K3, CO2	<p>Write short notes on the following</p> <ul style="list-style-type: none"> (i) LED (ii) Tunnel Diode (iii) Photodiode (iv) Varactor Diode 	5

CO-Course Outcomes mapped with respective question

KL- Bloom's Knowledge Level (K₁,K₂,K₃,K₄,K₅,K₆)

K₁ – Remember K₂ – Understand K₃ – Apply K₄ – Analyze K₅ – Evaluate K₆ – Create