

## Important Questions

- ① Difference between BJT & FET
- ② Difference between D-MOS & E-MOS
- ③ Define transconductance. How JFET can be used as VVR & Constant Current source.
- ④ Explain Virtual ground Concept.
- ⑤ Input & output characteristics of Common base configuration along with Circuit diagram.
- ⑥ Input & output characteristics of Common emitter configuration.
- ⑦ Relation between  $\alpha$ ,  $\beta$ ,  $\gamma$  & its numerical
- ⑧ Numericals based on transconductance & Shockley's equation.
- ⑨ Working of NPN transistor in Common base config.
- ⑩ Construction, Working & characteristics of :-
  - (a) JFET
  - (b) D-MOS
  - (c) E-MOS

- ✓ 11 Ideal characteristics of op-amp.
- ✓ 12 Ideal voltage transfer curve of op-amp.
- ✓ 13 Derive expression for o/p voltage or closed loop Gain for —
  - (a) Inverting op-amp
  - (b) Non-Inverting op-amp
- ✓ 14 Derive  $V_o$  for inverting & Non-inverting summing amplifiers.
- ✓ 15 op-amp as subtractor
- ✓ 16 op-amp as Integrator & Differentiator
- ✓ 17 op-amp as Comparator
- ✓ 18 Voltage follower/unity gain amplifiers.
- ✓ 19 Different modes of op-amp
- ✓ 20 Numericals based on CMRR | (covered in PDF of op-amp)
- ✓ 21 Why CE is preferred for amplification in BJT