



**ABES Engineering College, Ghaziabad**

**Session: 2023-24**

**Semester: I**

**Course Code: BEC-101**

**Course Name: Fundamental of Electronics Engineering**

**Assignment - 4**

- ✓ Q1. Derive the relation of current gains between CB, CE & CC configuration. A transistor having  $\alpha = 0.975$  and reverse saturation current  $I_{CBO} = 10\mu A$  is operated in CE mode. If the base current is  $250\mu A$ . Calculate  $I_E$  and  $I_C$ .
- ✓ Q2. Explain the working of NPN transistor in CE Configuration with suitable input and output characteristics and mention the regions of operation.
- Q3. Explain the construction, working and characteristics of n channel DMOS.
- Q4. Explain the construction, working and characteristics of n channel EMOS.
- ✓ Q5. Compare FET and BJT.
- Q6. Describe the input and output characteristics of CB configuration.
- ✓ Q7. Mention the difference between DMOS and EMOS.
- Q8. Draw the drain and transfer characteristics of P channel DMOS and EMOS.
- ✓ Q9. Explain the construction, working and characteristics of n channel of JFET.
- ✓ Q10. (a) Why is CE configuration preferred in amplifier circuits?  
(b) Explain how JFET can be used as a VVR and a constant current source.