



Assignment 2

S.N o.	KL, CO	Question	Marks
1	K3, CO1	The reverse saturation current of a Si diode at room temperature is 5nA. Calculate the diode current at room temperature when the voltage across diode is 0.7V.	5
2	K3, CO1	<p>Determine <math>V_o</math> &amp; <math>I_D</math> of the following networks, (voltage drop across red LED in ON state=1.8v)</p>	5
3	K3, CO1	<p><b>Determine <math>V_o</math>, <math>I_1</math>, <math>I_D</math>, and <math>I_{D2}</math> for the networks given below..</b></p>	5
4	K3, CO1	<p>Determine the output waveform for the networks given below and calculate the output dc level and the required PIV of each diode.</p>	5
5	K2, CO1	Explain the working of P-N junction diode in Unbiased and Biased conditions.	5
6	K2, CO3	Explain the working of Bridge type full wave rectifier with proper circuit diagram and waveforms.	5
7	K2, CO1	Draw and explain the full wave voltage doubler with proper circuit diagram.	5
8	K2, CO1	Draw and explain the Voltage Tripler/Quadrupler with proper circuit diagram.	5

9	K3, CO1	<p>Determine and draw the output voltage of the following networks.</p>	5
10	K3, CO1	<p>Determine and draw the output voltage of the following networks.</p>	5

CO-Course Outcomes mapped with respective question

KL- Bloom's Knowledge Level (K<sub>1</sub>,K<sub>2</sub>,K<sub>3</sub>,K<sub>4</sub>,K<sub>5</sub>,K<sub>6</sub>)

K<sub>1</sub> – Remember K<sub>2</sub> – Understand K<sub>3</sub> – Apply K<sub>4</sub> – Analyze K<sub>5</sub> – Evaluate K<sub>6</sub>– Create